

PRACTICAL

ELECTRONICS

MARCH 1975

30p

...in this issue

FREE

I.C. IDENTICHART

**for VALUABLE
PROTECTION**



The diagram illustrates an ultrasonic intruder alarm system within a room. Two black rectangular sensors are mounted on the left wall and floor. Red lines represent the ultrasonic waves emanating from these sensors, reflecting off the walls and floor to create a protective zone. A white outline of a person is shown entering this zone from the right. The room is depicted with green walls and a yellow floor, all enclosed within a blue border.

**Fit the DOPPLER SHIFT
ULTRASONIC INTRUDER ALARM**

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN
- PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31" Loudspeaker ● Earpiece ● Mica Baseboard
- 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 55p (free with parts)

TOTAL BUILDING COSTS

£7-23 P.P. & Ins. 44p
(Overseas Seamail P. & P. £2-35)
(+ 8% VAT 57p)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and 8W. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wave change controls. Attractive all white case with red grille and carrying strap. Size 9½in x 7in x 2½in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-95** P.P. & Ins. 44p
(Overseas Seamail P. & P. £2-35)
(+ 8% VAT 55p)

POCKET FIVE

NOW WITH 3" LOUDSPEAKER

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages. 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½in x 1½in x 3½in approx. Plans and parts price list free with parts. (Overseas Seamail P. & P. £1-70)



Total Building Costs **£2-75** P.P. & Ins. 36p
(+ 8% VAT 21p) (Overseas Seamail P. & P. £1-70)

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list free with parts.

£2-50 P.P. & Ins. 36p
(+ 8% VAT 20p)

TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

ROAMER SIX CASE AND LOOKS AS TRANS EIGHT

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Plans and parts price list free with parts.

TOTAL BUILDING COSTS **£4-48** P.P. & Ins. 40p
(Overseas Seamail P. & P. £1-25)
(+ 8% VAT 36p)

TOTAL BUILDING COSTS **£3-98** P.P. & Ins. 40p
(Overseas Seamail P. & P. £2-00)
(+ 8% VAT 32p)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9in x 5½in x 2½in approx. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£2-95** P.P. & Ins. 36p
(Overseas Seamail P. & P. £1-70)
(+ 8% VAT 23p)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial. 3" Loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£3-60** P.P. & Ins. 36p
(Overseas Seamail P. & P. £1-70)
(+ 8% VAT 29p)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£4-08** P.P. & Ins. 38p
(Overseas Seamail P. & P. £2-00)
(+ 8% VAT 32p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-98** P.P. & Ins. 47p
(Overseas Seamail P. & P. £2-50)
(+ 8% VAT 56p)

ROAMER TEN Mk. II

WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft. Volume/on/off, wave change and tone control. Attractive case in black with silver lining. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

TOTAL BUILDING COSTS **£9-50** P.P. & Ins. 52p
(Overseas Seamail P. & P. £2-50)
(+ 8% VAT 76p)



EDU-KIT

Build Radios Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 4in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£5-50** P.P. & Ins. 40p
(Overseas Seamail P. & P. £2-35)
(+ 8% VAT 44p)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £..... for.....

Name.....

Address.....

PE3

PRACTICAL ELECTRONICS

VOLUME 11 No. 3 MARCH 1975

CONSTRUCTIONAL PROJECTS

- ULTRASONIC DOPPLER SHIFT INTRUDER ALARM** *by J. B. Dance.* 206
Protect your home with this easy to construct security system
- P.E. MINISONIC—5** *by G. D. Shaw* 212
This concluding article deals with making the most of the Minisonic
- IN-CIRCUIT OHMMETER** *by O. N. Bishop* 228
For measuring the resistance of a component without having to remove it from the circuit
- ELECTRONIC THERMOSTAT** *by R. A. Penfold* 236
An accurate temperature controller particularly suitable for photographic work
- GEIGER COUNTER** *by M. Plant* 242
Detect radioactive minerals with this portable pocket radiation monitor

GENERAL FEATURES

- SWITCHING POWER SUPPLIES** 223
- INGENUITY UNLIMITED** 219
Touch-Switch—Two-way Morse Trainer—Transistor Tester—Lighting Control Circuit

NEWS AND COMMENT

- EDITORIAL—On Guard** 205
- SPACEWATCH** *by Frank W. Hyde* 216
Pioneer 11—Red Spot—Radio Waves from Earth
- POINTS ARISING** 220
P.E. Orion—P.E. Minisonic 3—Digital Leaf—Marine Speedometer
- NEWS BRIEFS** 233
New Loudspeaker—New Year Award—Ipswich News
- MARKET PLACE** 234
Loudspeaker Kit, P.E. Orion, Digital Leaf and New Transistors
- BOAT SHOW '75** 239
Electronics for the mariner at this year's show
- ELECTROMUSE** *by Malcolm Pointon* 241
Setting-up and composing electronic music
- INDUSTRY NOTEBOOK** *by Nexus* 245
What's happening inside industry
- PATENT REVIEW** 248
Thought provoking ideas on file at the British Patents Office
- READOUT** 249
More on Boolean breakfast

SPECIAL FREE DATA SHEET INSIDE THIS ISSUE I.C. IDENTICHART

An easy-to-read directory of over 450 integrated circuits

CEEFAX and ORACLE
Part 2 of this article will appear next month

Our April issued will be published on Friday, March 14, 1975

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3.85, Overseas £4.70. USA and Canada \$13.00. International Giro facilities Account No. 5122007. State reason for payment, "message to payee".

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* +VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £10.85 inc. VAT and p & p.
Ready Made Unit £13.65 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES



The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel: Sheffield (0742) 668888



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/
volt High Sensitivity Meter
£14.40. 20p P. & P.

**TAPE
RECORDER
LEVEL
METER**

500µA, 70p. 5p P. & P.



**CARDIODE
DYNAMIC
MICROPHONE**

del UD-130. Fre-
quency response 50-
000c/s. Impedance
at 50K and 600 ohms,
55. 11p P. & P.



4½in x 3½in **METER.** 30µA,
50µA or 100µA, £3.85. 11p P. & P.

**MULTI-
METER**

Model D62
20,000 ohm/
volt, £7.65.
15p P. & P.



**3 WATT STEREO
AMPLIFIER**
£4.30. 10p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11.
Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

ENGINEERS

FREE

**YOURSELF FOR A
BETTER JOB WITH MORE PAY!**

Do you want promotion, a better job, higher pay? 'New Opportunities' shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This guide to success should be read by any ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!
Tick or state subject of interest. Post to the address below.

☐ Practical Radio and Electronics (Technician)	☐ C. & G. Radio, TV Electronics, Mechanics	☐ C. & G. LI Installations and Wiring
☐ Electronic Engineering	☐ Radio Amateurs	☐ General Electrical Engineering
☐ Television Maintenance and Servicing	☐ Practical TV	☐ Society of Engineers (Electrical Engineering)
☐ General Radio and TV Engineering	☐ Colour Television	☐ Electrical Installations and Wiring
☐ Radio Servicing, Maintenance and Repairs	☐ Computer Electronics	☐ C. & G. Electrical Technicians (Primary)
	☐ C. & G. LI Radio-TV Servicing cert.	☐ C. & G. Telecommunications
	☐ Post Master General 1st & 2nd class cens.	
	☐ C. & G. Electrical Engineering Practise	

TO ALDERMASTON COLLEGE
Dept. EPE03, Reading RG7

NAME (Block Capitals Please) _____
ADDRESS _____
POSTCODE _____ Age _____
Other subjects Accredited by C.A.C.C. _____ Member of A.B.C.C. _____

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Includes dozens of useful and interesting circuits you can build: data: hundreds of pictures: transistor equivalents list and hundreds of new lines. Packed with information. **ONLY 35p.**

187

R T V C

FOR AUDIO AT A BUDGET

COMPLETE STEREO SYSTEM

*



System 1. £51-00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System 1 includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K, equalised within -1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2".

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 1/2" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

Complete System £51-00

System 2. £69-00

Viscount III amplifier (As System 1)

Garrard SP 25 Mk III deck (As System 1)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2" Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69-00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only: **£51-00**
+ £3.50 p & p

PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

Available complete for only: **£69-00**
+ £4.00 p & p

STEREO 21* QUALITY SOUND FOR LESS THAN £20-00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes:- BSR 3 speed deck, automatic, manual facilities together with stereo cartridge. Two speakers with cabinets.


Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications: For the technically minded:-

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only **£19-95** + £1.60 p & p. Extras if required. Optional Diamond Styli **£1-37**.

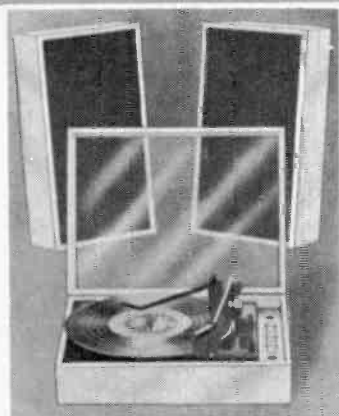Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85**.



BUILD YOUR OWN * STEREO AMPLIFIER

For the man who wants to design his own stereo - here's your chance to start with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7-64+55p p & p Also available with 2 speakers (7" x 4") £9-00 + 75p p. & p.

8 TRACK HOME CARTRIDGE PLAYER

*



Elegant self selector push button player for use with your stereo system.

Compatible with Viscount III system, Unisound module and the Stereo 21.


Technical specification Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at

£24.00 approx. Yours for only

£11.95 + 90p p & p.

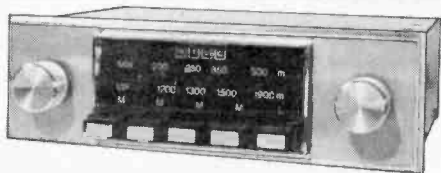PUSH BUTTON CAR RADIO KIT ~ The Tourist II



NO SOLDERING REQUIRED!

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

TECHNICAL SPECIFICATION: (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) **Integrated circuit** output stage, pre-built three stage IF Module. **Controls** volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4½" deep approx £7.70 + 55p. p & p.

Speaker including baffle and fixing strip £1.65 + 23p. p & p.

Car Aerial Recommended—fully retractable £1.37 + 20p. p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model.

Same technical specification as Tourist II. **Price £6.60 + 55p p & p.**

EMI SPEAKERS AT FANTASTIC REDUCTIONS

20 WATT SPEAKER SYSTEM *

System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components. Circuit diagram.

Technical Specification:

Bass Unit

Flux density—100 K. speech coil—1½". Cone. Triple laminated paper with P.V.C. surround.

Mid Range Unit

Flux density—33K. speech coil—1" with parasitic tweeter.

Power Handling

20 watts R.M.S. impedance—8 ohms, frequency response—20 Hz to 18,000 Hz.

**OUR PRICE
£6.60. Complete
+ 90p p & p.**




15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS. and is treated to give a smooth frequency response. Resonance 30 Hz. Flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70

+ £1.50 p & p

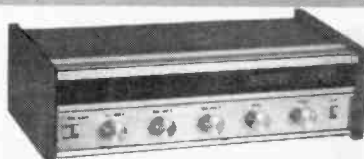

DISCO AMPLIFIER *

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls.

*Separate bass and treble controls common to all 4 inputs.


*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry.

*Attractive styling.

INPUT SENSITIVITIES —Input — 1.) Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity).

—Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12½" x 6" x 3½". **£15.00 + 60p. p & p**

PORTABLE DISCO CONSOLE *

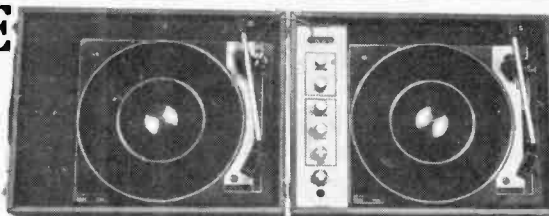

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV.

Auxiliary inputs — 200mV and 750mV into 1 meg.

Mic input — 6mV into 100K. 240 volt operation.

Turntables capacity — 7", 10" or 12" records.

Rumble, wow and flutter

Rumble Better than -35dB. **Wow** Better than 0.2%.

Flutter Better than 0.06% (Gaumont kalee meter).

Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17½" x 13½" x 8½" (approx.)

Unit Open — 35½" x 13½" x 4½" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.



DO NOT SEND CARD

Just write your order giving your credit card number



Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Jan. 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.

Personal Shoppers Edgware Road: 9a.m.—5.30p.m. Half day Thurs. Acton: 9.30a.m.—5p.m. Closed all day Wed.



Radio and TV
Components
(Acton) Ltd.

21d High Street, Acton, London W3 6NG
323 Edgware Road, London W2

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY

The famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed matt and brushed aluminium trim, and the Perspex cover has an easy "hinged-on, hinged-off" movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth, as above.



S.A.U.2 PICK-UP ARM

Recognised as one of today's most advanced pick-up arms it features

- * Auto-bias Compensator
- * Hydraulic Lowering Device
- * Precision Balance
- * Adjustable Head Shell



S.C.U.1 STEREO CARTRIDGE

A quality cartridge designed specifically for the person who appreciates his equipment.



Contact your dealer for information or send stamp for a brochure.

A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoisseur, Brighouse

ERSIN



for fast easy reliable soldering EASY TO USE DISPENSERS AND REELS IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5
32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



For soldering fine joints



Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 71t. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B.80p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited,


Sole U.K. Sales Concessionaires. P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Prices and specifications subject to change without notice.





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

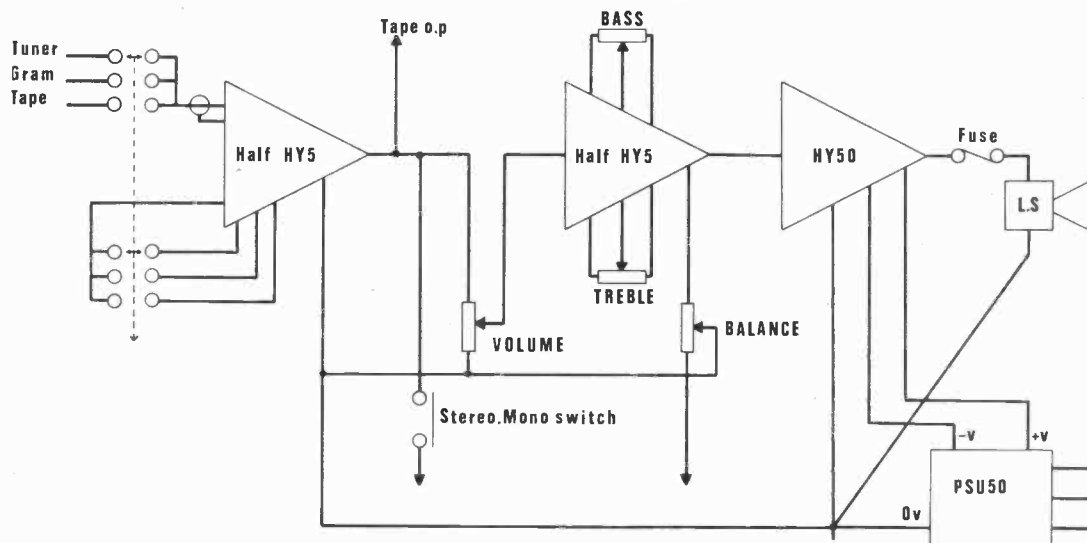

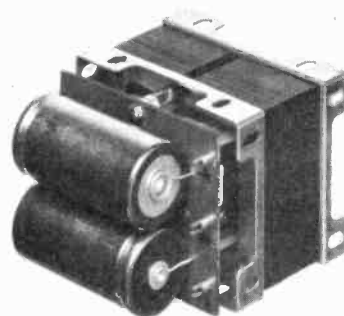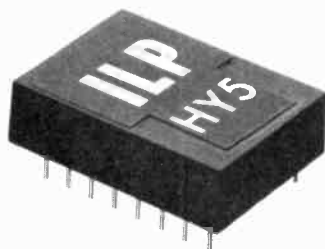MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input/impedance 47k Ω at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble $\pm$ 12db at 10kHz; Bass $\pm$ 12db at 100Hz; Distortion: 0.5% at 1kHz; Signal/Noise Ratio: 68db; Overload Capability: 40db on most sensitive input. Supply Voltage: $\pm$ 16-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8 Ω . Load Impedance: 4-16 Ω . Input Sensitivity: 0db (0.775V RMS). Input Impedance: 47k Ω . Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz $\pm$ 3db. Supply Voltage: $\pm$ 25V. Size: 105 x 50 x 25mm.

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: $\pm$ 25V. Input voltage: 210-240V. Size: L 70, D 90, H 60mm.

PRICE £4.50

+ 36p VAT
P. & P. free

PRICE £5.98

+ 48p VAT
P. & P. free

PRICE £6

+ 48p VAT
P. & P. FREE

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply
Total Purchase Price
I Enclose Cheque ☐ Postal Orders ☐ Money Order ☐
Please debit my Access account ☐ Barclaycard account ☐
Account number
Name and Address
Signature

If you're interested in electronics You'll like the NEW LITESOLD SUPER IRONS

We've been supplying the electronics industry with soldering irons for many years and we have now put all our experience into an iron for the electronics enthusiast.

The new LITESOLD SUPER IRONS have all the features you have been looking for; a neon indicator which glows only when the supply is connected correctly and the iron is safely earthed, an unbreakable nylon handle, a burn-proof mains lead, a special oxydised binding, a long life element, a range of bit shapes to suit every job and a special bench stand.

There are three SUPER IRONS

the S90

12 watts for miniature jobs

at £4.77

the S142

20 watts for medium jobs

at £4.85

the S187

24 watts for heavy jobs

at £4.89

and the special spring stand at £2.24.

Get your LITESOLD SUPER IRON
direct from

**Light Soldering
Developments Limited**
97-99 Gloucester Road
Croydon Surrey
Telephone 01-689 0574

All prices include postage, packing and VAT
but not the diamond ring.



RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 5p for first transistor, 1p thereafter, over
ten post free. INTEGRATED CIRCUITS 6p + 1p each added

1N21	0-17	AFZ11	1-15	BY213	0-25	OAZ205	0-45	Z8170	0-10
1N23	0-35	AFZ12	2-00	BYZ10	0-45	OAZ206	0-45	Z8271	0-18
1N85	0-88	ASY26	0-25	BYZ11	0-40	OAZ207	0-45	ZT21	0-25
1N253	0-50	ASY27	0-33	BYZ12	0-40	OAZ208	0-40	ZT43	0-25
1N256	0-50	ASY28	0-25	BYZ13	0-42	OAZ209	0-40	ZTX107	0-12
1N645	0-16	ASY29	0-30	BYZ15	1-25	OAZ210	0-40	ZTX108	0-08
1N725A	0-20	ASY36	0-25	BYZ16	0-60	OAZ211	0-40	ZTX300	0-78
1N914	0-06	ASY30	0-20	BZY88	0-10	OAZ222	0-45	ZTX304	0-24
1N4007	0-12	ASY51	0-40	C111	0-65	OAZ223	0-45	ZTX500	0-13
18113	0-25	ASY53	0-20	CRS1/05	0-30	OAZ224	0-45	ZTX503	0-18
18202	0-23	ASY55	0-20	CRS1/40	0-45	OAZ241	0-25	ZTX531	0-25
2G371	0-40	ASY62	0-25	CS4B	1-90	OAZ242	0-15	INTEGRATED CIRCUITS	
2G381	0-22	ASY66	0-33	CS10B	3-60	OAZ244	0-85		
2G414	0-30	ASZ21	1-00	DD000	0-15	OAZ246	0-15	7400	0-18
2G417	0-25	ASZ23	0-75	DD003	0-15	OAZ290	0-38	7401	0-18
2N404	0-22	AU104	1-00	DD006	0-25	OC16	1-00	7402	0-18
2N697	0-16	AU107	1-00	DD007	0-40	OC16T	1-00	7403	0-18
2N698	0-30	BC107	0-14	DD008	0-38	OC19	0-60	7404	0-28
2N706	0-12	BC108	0-13	GD3	0-33	OC22	1-00	7405	0-22
2N706A	0-12	BC109	0-14	GD4	0-10	OC23	1-25	7406	0-42
2N708	0-15	BC113	0-15	GD5	0-33	OC24	1-10	7407	0-42
2N709	0-40	BC115	0-20	GD8	0-25	OC25	0-38	7408	0-28
2N1091	0-55	BC116A	0-23	GD12	0-10	OC26	0-40	7409	0-28
2N1131	0-25	BC118	0-20	GET102	0-50	OC28	0-68	7410	0-18
2N1132	0-24	BC121	0-20	GET103	0-40	OC29	0-65	7411	0-25
2N1302	0-18	BC122	0-20	GET113	0-35	OC30	0-40	7412	0-30
2N1303	0-18	BC125	0-68	GET114	0-30	OC35	0-55	7413	0-38
2N1304	0-28	BC126	0-68	GET115	0-30	OC36	0-60	7416	0-38
2N1305	0-22	BC140	0-65	GET116	0-85	OC41	0-35	7417	0-38
2N1306	0-28	BC147	0-10	GET129	0-50	OC42	0-40	7418	0-38
2N1307	0-28	BC148	0-08	GET872	0-30	OC43	0-70	7422	0-25
2N1308	0-28	BC149	0-10	GET875	0-40	OC44	0-20	7423	0-37
2N147	0-78	BC157	0-14	GET880	0-60	OC44M	0-17	7425	0-37
2N2148	0-60	BC158	0-12	GET881	0-25	OC45	0-20	7427	0-37
2N2160	0-78	BC169	0-14	GET882	0-35	OC45M	0-18	7428	0-40
2N2218	0-23	BC169	0-14	GET885	0-40	OC46	0-27	7430	0-38
2N2219	0-25	BCY31	0-45	GET886	0-40	OC47	0-60	7432	0-37
2N2244	1-09	BCY32	0-85	GET887	0-40	OC48	0-60	7433	0-37
2N2613	0-28	BCY33	0-38	GET888	0-40	OC49	0-60	7437	0-37
2N2646	0-50	BCY34	0-45	GET889	0-40	OC66	0-50	7438	0-37
2N2904	0-20	BCY38	0-65	GET890	0-40	OC70	0-18	7440	0-22
2N2904A	0-25	BCY39	1-50	GET891	0-40	OC71	0-18	7441AN	0-92
2N2906	0-20	BCY40	0-80	GET892	0-40	OC72	0-50	7442	0-18
2N2907	0-22	BCY42	0-30	HG1005	0-50	OC73	0-50	7450	0-18
2N2924	0-13	BCY70	0-18	HB100A	0-20	OC74	0-30	7451	0-18
2N2925	0-15	BCY71	0-22	MAT100	0-20	OC75	0-30	7453	0-18
2N2926	0-12	BCZ10	0-60	MAT101	0-25	OC76	0-30	7454	0-18
2N3034	0-48	BCZ11	0-65	MAT120	0-20	OC77	0-54	7460	0-18
2N3055	0-45	BD121	1-00	MAT121	0-25	OC78	0-25	7470	0-38
2N3702	0-11	BD123	1-00	MJE255	1-27	OC81	0-29	7472	0-38
2N3705	0-15	BD124	0-65	MJE3055	0-77	OC81D	0-28	7473	0-41
2N3706	0-11	BDY11	1-45	MJE340	0-47	OC81M	0-20	7474	0-42
2N3707	0-13	BF115	0-20	MFP102	0-40	OC81DM	0-18	7475	0-59
2N3709	0-10	BF167	0-25	MFP103	0-38	OC81Z	0-45	7476	0-45
2N3710	0-11	BF173	0-28	MFP104	0-35	OC82	0-45	7480	0-80
2N3711	0-11	BF181	0-35	MFP105	0-38	OC82D	0-28	7482	0-87
2N3819	0-38	BF184	0-22	NKT128	0-45	OC83	0-27	7484	1-00
2N4298	0-30	BF185	0-28	NKT129	0-30	OC84	0-30	7486	0-47
2N5027	0-63	BF194	0-10	NKT211	0-25	OC110	0-38	7490	0-55
2N5088	0-33	BF195	0-13	NKT212	0-25	OC122	1-00	7491AN	1-00
2S301	0-59	BF196	0-15	NKT214	0-24	OC123	1-10	7492	0-70
2S304	1-15	BF197	0-18	NKT216	0-40	OC139	0-40	7493	0-70
2S501	0-75	BF861	0-25	NKT217	0-45	OC140	1-14	7494	0-86
2S703	1-00	BF898	0-25	NKT218	1-12	OC141	0-80	7495	0-80
AA129	0-20	BFX12	0-20	NKT219	0-33	OC169	0-20	7496	0-95
AAZ12	0-75	BFX13	0-28	NKT222	0-30	OC170	0-30	7497	3-87
AAZ13	0-12	BFX29	0-28	NKT224	0-25	OC171	0-30	74100	1-89
AC107	0-51	BFX30	0-28	NKT251	0-24	OC200	0-64	74107	0-45
AC126	0-25	BFX63	0-60	NKT271	0-20	OC201	1-00	74111	0-58
AC127	0-25	BFX64	0-25	NKT272	0-20	OC202	0-90	74116	0-58
AC128	0-15	BFX85	0-28	NKT273	0-20	OC203	0-55	74118	0-90
AC187	0-21	BFX86	0-25	NKT274	0-20	OC204	0-65	74119	1-68
AC188	0-20	BFX87	0-25	NKT275	0-25	OC205	1-10	74121	0-50
AC197	0-40	BFX88	0-24	NKT277	0-20	OC206	1-10	74122	0-70
AC198	0-27	BFY10	1-00	NKT278	0-25	OC207	1-00	74123	1-00
AC199	0-27	BFY11	0-60	NKT301	0-85	OC460	0-20	74141	0-80
AC200	0-22	BFY17	0-40	NKT304	0-75	OC470	0-30	74145	1-10
AC221	0-22	BFY18	0-45	NKT403	0-70	OCPT1	1-20	74150	1-75
AC222	0-16	BFY19	0-55	NKT404	0-68	ORP12	0-80	74151	1-00
AC227	0-25	BFY24	0-45	NKT678	0-30	ORP60	0-55	74154	2-00
AC278	0-25	BFY44	1-00	NKT713	0-30	ORP61	0-48	74155	1-00
AC398	0-78	BFY50	0-21	NKT773	0-25	RX68	0-20	74156	1-00
AC400	0-22	BFY51	0-20	NKT777	0-38	RX631	0-45	74157	0-85
AC441	0-22	BFY52	0-20	OA8	0-75	RX635	0-55	74170	2-52
AC444	0-32	BFY53	0-17	OA7	0-08	RX641	0-75	74175	1-10
AD140	0-50	BFY64	0-38	OA70	0-10	SX642	0-60	74176	1-28
AD149	0-50	BFY90	0-81	OA71	0-20	SX644	0-85	74190	2-00
AD161	0-44	BSX27	0-50	OA73	0-15	SX645	0-85	74191	2-00
AD162	0-44	BSX60	0-93	OA74	0-15	SX646	0-85	74192	2-00
AF106	0-30	BSX76	0-18	OA79	0-10	TIC44	0-29	74193	2-00
AF114	0-25	BSY26	0-17	OA81	0-18	V15/30P	0-75	74194	1-80
AF115	0-25	BSY27	0-20	OA85	0-15	V30/201P	0-75	74195	1-10
AF116	0-25	BSY51	0-50	OA86	0-15	V60/201P	0-50	74196	1-20
AF117	0-24	BSY95A	0-12	OA86	0-15	V60/201P	0-75	74197	1-20
AF118	0-57	BSY95	0-12	OA90	0-07	XA101	0-10	74198	2-77
AF119	0-20	BT102/500R	0-91	OA91	0-07	XA102	0-15	74199	2-52
AF124	0-30	BTY42	0-75	OA95	0-07	XA102	0-18	Plug in sockets —low profile 14 pin DIL	
AF125	0-30	BTY43	0-92	OA95	0-08	XA103	0-15		
AF126	0-30	BTY79/100R	0-75	OA202	0-08	XA152	0-15	16 pin DIL	
AF127	0-30	BTY79/400R	0-75	OA210	0-20	XA161	0-25		
AF139	0-41	BY100	0-27	OA211	0-35	XA162	0-25	0-17	
AF178	0-55	BY126	0-14	OAZ200	0-50	XB101	0-43		
AF179	0-65	BY127	0-12	OAZ202	0-45	XB102	0-30	0-17	
AF180	0-55	BY127	0-12	OAZ203	0-45	XB103	0-35		
AF181	0-50	BY182	0-85	OAZ204	0-45	XB113	0-30	0-17	
AF186	0-48					XB121	0-43		

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only • Tel. 01-677 2424-7
All orders subject to V.A.T. at 8% rate. This must
be added to the total order including postage.

Prices correct
when going
to press.


SAXON

Money saving high
performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

SA35 35W RMS 25-50V 7 transistors, 7 diodes	£5.45	Carriage free	★ 25Hz-25kHz ★ 0.2% distortion ★ Noise—80dB ★ 500mV into 20K
SA50 50W RMS 25-65V 7 transistors, 7 diodes	£6.90	Carriage free	★ 4-16 ohms ★ Simple wiring ★ Short and open circuit proof
SA100 100W RMS 45-70V 10 transistors, 7 diodes	£12.50	Carriage free	★ Continuously rated ★ Top-grade components

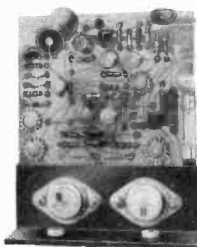120 watt module complete with built-in supply—extra heavy duty £22.50 Carr. 60p



THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED—READY WIRED

PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	£5.45	Carriage 30p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	£8.45	Carriage 40p

STABILISED

PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	£4.45	Carriage free
MT45	Transformer for above	£3.50	Carriage 30p
PS70	Suits 2 SA100	£5.45	Carriage free
MT70	Transformer for above	£4.90	Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22.50 Carr. 30p

This well tried Pre-Amp mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17in x 3in x 4in deep.



DISCO MODULE £9.50 Carr. 20p

Thousands sold of this extremely popular mono Pre-Amp. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: h/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2in deep. Professional standards at a price you can afford!




SINGLE CHANNEL VERSION £7.50 Carr. free Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders

MULTI-PURPOSE MIXERS

M4HL Carr. 50p **M6HL Carr. 50p**
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

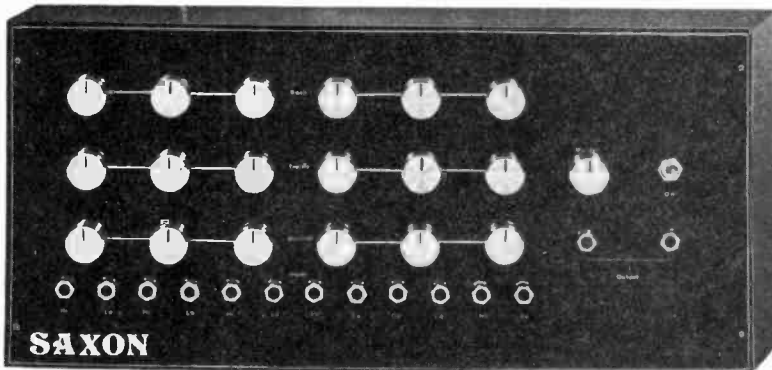VA30 CHANNEL MODULE £3.50 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)




SAXON CSE 100

COMPLETE AMPLIFIER

£39.90 Carr. free

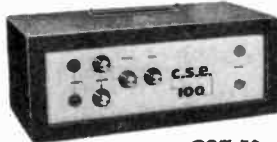100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinyl case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29.50 Carr. free

NEW!!

SAXON MULTIMIX 100 £57 CARR. FREE

100W RMS SLIDER controls PLUS master slider. Wide range bass and treble controls—fantastic value. Ideal for complete Disco's, Groups, Clubs, etc.

SAXON MULTIMIX 50 EXACTLY AS ABOVE £45 BUT 50W RMS

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD • CROYDON CR0 2HS
(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. - 5 p.m. — LUNCH 12.30 - 1.30 p.m. MAIL ORDER DESK: 10 a.m. - 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p. for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.

The largest selection

EX-COMPUTER STABILISED POWER MODULES

Complete with circuit diagrams, etc.
99p each plus 22p P. & P.

LOW COST CAPACITORS

0.01µF 400V. 3p each
500µF 50V. Elect. 10p each

FIBRE-GLASS PRINTED CIRCUIT BOARDS

161 x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen
99p each

VEROBOARDS

Packs containing approx. 50sq. in. various sizes, all 0.1 metric 55p

REPANCO CHOKES & COILS

RF Chokes
CH1: 2.5mH 22p CH2: 5.0mH 30p
CH3: 7.5mH 31p CH4: 10mH 33p
CH5: 1.5mH 28p

COILS

DRX1 Crystal set 31p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 8p
1" Cores & Formers 10p

SWITCHES

DP/DT Toggle 36p SP/ST Toggle 30p

FUSES

1" and 20mm. 100mA, 200mA, 250mA,
500mA, 1A, 1.5A, 2A
QUICK-BLOW 5p each.

EARPHONES

Crystal 2.5mm plug 42p
Crystal 3.5mm plug 42p
8 ohms 2.5mm plug 22p
8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223, 200 ohms plus on/off switch and
2.5mm and 3.5mm plugs £1.85

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007, 80 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4"	2"	£1.35
BV2	11"	6"	3"	£1.75

ALUMINIUM BOXES

Box	Length	Width	Height	Price
BA1	4 1/2"	2 1/2"	1 1/2"	49p
BA2	4"	4"	1 1/2"	49p
BA3	4"	2 1/2"	1 1/2"	49p
BA4	5 1/2"	4"	1 1/2"	58p
BA5	4"	2 1/2"	2"	49p
BA6	3"	2"	1"	42p
BA7	7"	3"	2 1/2"	85p
BA8	8"	6"	3"	£1.10
BA9	6"	4"	2"	70p

P. & P. 10p on each box

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. 36A. Record/Styleus Cleaning Kit 33p
Ref. 43. Record Care Kit £2.42
Ref. 31. Cassette Head Cleaner 58p
Ref. 32. Tape editing Kit £1.68
Model 9. Wire Stripper/Cutter 83p
Ref. 46. Spirit Level 62p

Ref. B. Stylus and Turntable Cleaning Kit
Ref. P. Hi-Fi Cleaner 31p 34p
Ref. 32A. Stylus Balance £1.37
Ref. J. Tape Head Cleaning Kit 62p
Ref. 36. Hi-Fi Stereo Hints and Tips 42p
Ref. 45. Auto Changer Groove Cleaner £1.08

ANTEX SOLDERING IRONS

X25. 25 watt £2.05
CCN 240. 15 watt £2.48
Model G. 18 watt £2.26
SK2. Soldering Kit £3.25
STANDS: ST3, suitable for all models £1
SOLDER: 188WG Multicore 7oz £1.61
228WG 7oz £1.61. 188WG 22ft 61p
228WG Tube 83p

ANTEX BITS AND ELEMENTS

Bits No.
102 For model CCN240 3/4" 42p
104 For model CCN240 1/2" 42p
1100 For model CCN240 3/4" 42p
1101 For model CCN240 1/2" 42p
1102 For model CCN240 1" 42p
1020 For model G240 3/4" 42p
1021 For model G240 1" 42p
1022 For model G240 1/2" 42p
50 For model X25 3/4" 48p
51 For model X25 1" 48p
52 For model X25 1/2" 48p

ELEMENTS

ECN 240 £1.30 ECCN 240 £1.32
EG 240 £1.07 EX 25 £1.16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add
10p P. & P. (U.K. only). Overseas orders
please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack	No. Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0.54
C2	150	Capacitors mixed values approx. count by weight	0.54
C3	50	Precision Resistors 0.1%, 0.01% mixed values	0.54
C4	75	1/4 W Resistors mixed preferred values	0.54
C5	5	Pieces assorted Ferrite Rods	0.54
C6	2	Tuning Gangs, MW/LW VHF	0.54
C7	1	Pack Wire 50 metres assorted colours	0.54
C8	10	Reed Switches	0.54
C9	3	Micro Switches	0.54
C10	15	Assorted Pots & Pre-Bets	0.54
C11	5	Jack Sockets 3" x 3/8" 2 x Standard Switch Type	0.54
C12	30	Paper Condensers preferred types mixed values	0.54
C13	20	Electrolytics Trans. types	0.54
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0.54
C15	5	Mains Slide Switches	0.54
C16	20	Assorted Tag Strips & Panels	0.54
C17	10	Assorted Control Knobs	0.54
C18	4	Rotary Wavy Change Switches	0.54
C19	2	Relays 6—24V Operating	0.54
C20	1	Pack Sheets of Copper Laminate approx. 20 sq. ins.	0.54

PLUGS AND SOCKETS

PLUGS
PS 1 D.I.N. 2 Pin (Speaker) 0.11
PS 2 D.I.N. 3 Pin 0.12
PS 3 D.I.N. 4 Pin 0.15
PS 4 D.I.N. 5 Pin 180° 0.16
PS 5 D.I.N. 5 Pin 240° 0.16
PS 6 D.I.N. 6 Pin 0.17
PS 7 D.I.N. 7 Pin 0.18
PS 8 Jack 2.5mm Screened 0.18
PS 9 Jack 3.5mm Plastic 0.12
PS 10 Jack 3.5mm Screened 0.18
PS 11 Jack 1" Plastic 0.15
PS 12 Jack 1" Screened 0.22
PS 13 Jack Stereo Screened 0.36
PS 14 Phono 0.10
PS 15 Car Aerial 0.22
PS 16 Co-Axial 0.15

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0.14
PS 22 D.I.N. 3 Pin 0.20
PS 23 D.I.N. 5 Pin 180° 0.20
PS 24 D.I.N. 5 Pin 240° 0.20
PS 25 Jack 2.5mm Plastic 0.16
PS 26 Jack 3.5mm Plastic 0.16
PS 27 Jack 1" Plastic 0.30
PS 28 Jack 1" Screened 0.35
PS 29 Jack Stereo Plastic 0.30
PS 30 Jack Stereo Screened 0.38
PS 31 Phono Screened 0.18
PS 32 Car Aerial 0.22
PS 33 Co-Axial 0.22

SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0.08
PS 36 D.I.N. 3 Pin 0.11
PS 37 D.I.N. 5 Pin 180° 0.11
PS 38 D.I.N. 5 Pin 240° 0.11
PS 39 Jack 2.5mm Switched 0.12
PS 40 Jack 3.5mm Switched 0.12
PS 41 Jack 1" Switched 0.20
PS 42 Jack Stereo Switched 0.30
PS 43 Phono Single 0.08
PS 44 Phono Double 0.10
PS 46 Co-Axial Surface 0.10
PS 47 Co-Axial Flush 0.20

LEADS

LS 1 Speaker Lead 2 pin D.I.N. plug to open ends approx 3 metres long (coded) 0.20

CABLES

CP 1 Single Lapped Screen 0.07
CP 2 Twin Common Screen 0.11
CP 3 Stereo Screened 0.12
CP 4 Four Core Common Screen 0.12
CP 5 Four Core Individually Screened 0.30
CP 6 Microphone Fully Braided Cable 0.10
CP 7 Three Core Mains Cable 0.09
CP 8 Twin Oval Mains Cable 0.07
CP 9 Speaker Cable 0.05
CP 10 Low Loss Co-Axial 0.18

CARBON POTENTIOMETERS

Log and Lin
4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
VC 1 Single Less Switch 0.15
VC 2 Single D.P. Switch 0.28
VC 3 Tandem Less Switch 0.46
VC 4 1K Lin Less Switch 0.15
VC 5 100K Anti-Log 0.46

HORIZONTAL CARBON PRESETS

0.1 watt 0.06 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

SOLVE THOSE STICKY PROBLEMS!

with



CYANOACRYLATE C2 ADHESIVE

The wonder bond which works in seconds—bond plastic, rubber, metals, transistors, components, permanently, immediately.

OUR PRICE ONLY 54p
for 2 gm. phial

BATTERY HOLDER

Takes 4, HP7's complete with terminal, clip and lead. 34p.

WORLD SCOOP

JUMBO SEMICONDUCTOR PACK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners. ALL NEW AND CODED.

APPROX. 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

RECORD STORAGE/CARRY CASES

7in EP. 18 1/2in x 7in x 8in (50 records) £2.10
12in LP. 13 1/2in x 7 1/2in x 12 1/2in (50 records) £2.95

CASSETTE CASES £1.30

Holds 12, 10in x 3 1/2in x 5in. Lock and handle.

8-TRACK CART. CASES

Holds 14, 1 1/2in x 5in x 6in £1.95
Holds 24, 1 1/2in x 8in x 5 1/2in £2.70
Both with lock and handle.

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able 115W. TO3. Metal Case.

OUR SPECIAL PRICE 8 for £1

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tapings 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 25V, 31V, 33V, 40, 50 and 25V-0-25V.

Type	Amps	Price	P. & P.
MT50/1	1	£1.93	45p
MT50/1	1	£2.42	48p
MT50/2	2	£3.30	60p

CARTRIDGES

ACOS
GP91-18C 200mV at 1/2cm/sec £1.35
GP93-1280mV at 1cm/sec £1.85
GP95-1100mV at 1cm/sec £2.80
J-2005 Crystal/Hi Output £1.05
J-2010C Crystal/Hi Output Compatible £1.20
J-2008S Stereo/Hi Output £1.75
J-2105 Ceramic/Med Output £1.85
J-2203 Magnetic 3mV/cm/sec, including stylus £4.95
J-2203S Replacement stylus for above £3.00
AT-55 Audio-technica magnetic cartridge 4mV/cm/sec £3.30

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1 watt available in PAKS of 50 pieces, assorted into the following groups:

R1	50 Mixed 100 ohms-820 ohms	50p
R2	50 Mixed 1kΩ-8.2kΩ	50p
R3	50 Mixed 10kΩ-82kΩ	50p
R4	50 Mixed 100kΩ-1MΩ	50p

THESE ARE UNEBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C60, 36p; C90, 48p; C120, 60p.

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

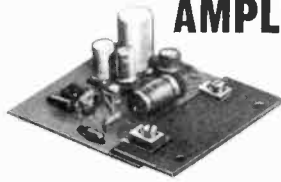

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	$P_o = 3 \text{ WATTS } f = 1 \text{ KHz}$	0-25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	$f = 1 \text{ KHz}$	100 k Ω
FREQUENCY RESPONSE —3dB	$P_o = 2 \text{ WATTS}$	50 Hz-25 KHz
SENSITIVITY for RATED O/P	$V_s = 25 \text{ V. } R_L = 8 \Omega f = 1 \text{ KHz}$	75mV. RMS
DIMENSIONS	—	3" x 2 1/4" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. ($R_L = 8 \Omega f = 1 \text{ KHz}$)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2-50
AL 20. 5 watts	£2-85
AL 30. 10 watts	£3-20

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 95p	
SPM 80. (Use with AL60) £3-25	
FRONT PANELS FP 12 with Knobs	£1-00

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 and AL30)	£4-35
PA 100. (Use with AL60)	£13-15

TRANSFORMERS

T461 (Use with AL10)	£1-60 P & P 22p
T638 (Use with AL20, AL30) £2-30 P & P	22p
BMT80 (Use with AL60) £2-75	P & P 37p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz-50KHz (—3dB)
Bass control—
 $\pm 12 \text{ dB at } 60 \text{ Hz}$
Treble control—
 $\pm 14 \text{ dB at } 14 \text{ KHz}$
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
Input 2. Impedance
30 K ohms
Sensitivity 4mV


Look for our

SEMICONDUCTOR ADVERTISEMENTS in
Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, Volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control $\pm 12 \text{ dB at } 60 \text{ Hz}$ typically 0-25% at 1 watt. Treble con. $\pm 14 \text{ dB at } 14 \text{ kHz}$.

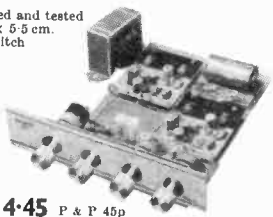

£14-45 P & P 45p

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) Size 10 1/2" x 8 1/2" x 3", £3-95 plus 45p postage.

SHP80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls, £4-95

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £4-25



- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0-1% at 1KHz
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

STABILISED POWER MODULE SPM80



SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1-5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3-25

TRANSFORMER BMT80 £2-15 p. & p. 40p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response 20Hz-20KHz $\pm 1 \text{ dB}$
Harmonic Distortion better than 0-1%
Inputs: 1. Tape Head 3-25 mV into 600 Ω
2. Radio, Tuner 75 mV into 50K Ω
3. Magnetic P.U. 3 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within $\pm 1 \text{ dB}$ from 20Hz to 20KHz.
Bass Control $\pm 12 \text{ dB at } 20 \text{ Hz}$
Treble Control $\pm 14 \text{ dB at } 20 \text{ KHz}$
Filters: Rumble (High Pass) 100Hz
Scratch (Low Pass) 8KHz
Signal/Noise Ratio better than -65dB
Input overload $\pm 26 \text{ dB}$
Supply +35 volts at 20mA
Dimensions 292mm x 82mm x 35mm

ONLY £14-25

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29-75 plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 14 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc. Kit price: £29-95 plus 45p postage.

Giro No 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 10p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

CHINAGLIA DINO - ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

CHINAGLIA




PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

CORTINA MINOR

33 RANGE POCKET MULTIMETER

- SENSITIVITY 20,000 Ω /VOLT (D.C.), 4,000 Ω /VOLT (A.C.).
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1,500V; D.C. CURRENT 0-50 μ A, 5mA, 50mA, 500mA, 2.5A; A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V; A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A; dB RANGES -10 to +69; AF VOLTS RANGES 0-1,500V; RESISTANCE RANGES 10k Ω , 10M Ω F.S.D. CAPACITANCE RANGES 100 μ F IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2.5%; A.C. VOLTAGE AND CURRENT 3.5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

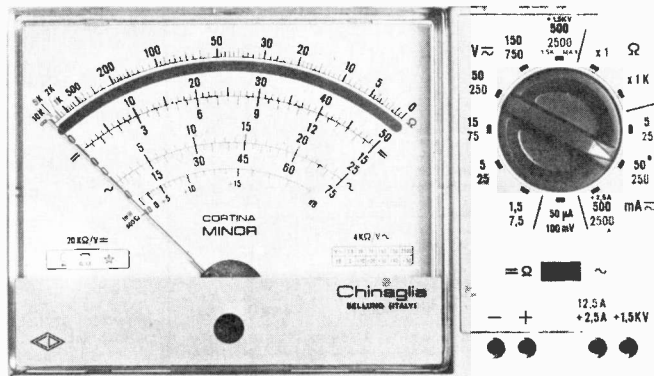

METER PRICE £16.30 (p & p 80p) PROBE £8.80 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone:—

CHINAGLIA (U.K.) LIMITED

19 Mulberry Walk, London S.W.3.


Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT
PRICES

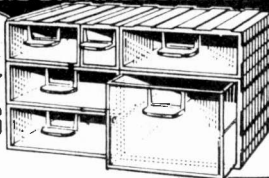

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES
ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £3.50 DOZEN.

TREBLE (3D) £3.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4.90 for 8.

EXTRA LARGE SIZE (6D1) £4.50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 8% V.A.T. to total remittance

FLAID (Dept PE3), 124 Cricklewood Broadway, London, N.W.2
Tel. 01-460 4844

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back-up service to ensure your success.

VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coils, also available P.W. tele-tennis game. Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

CROFTON ELECTRONICS

124 Colne Road, Twickenham Middlesex TW2 6QS

Telephone 01-898 1569

Telex 934642 Cadanac LDN



SET UP YOUR OWN HI-FI A BEGINNER'S GUIDE

by R. H. Warring Price £1-90

STEREO F.M. RADIO HANDBOOK

by P. Harvey/K. J. Bohlman. Price £2-70.

RAPID SERVICING OF TRANSISTOR EQUIPMENT by G. J. King. Price £2-05.

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £2-05.

ELEMENTS OF TRANSISTOR PULSE CIRCUITS by T. D. Towers. Price £3-70.

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price £1-35.

UNDERSTANDING SOLID STATE ELECTRONICS by Texas Instruments. Price £1-35.

ELECTRONIC SECURITY SYSTEMS by Leo G. Sands. Price £3-30.

PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES. Price £2-80.

SEMICONDUCTOR ELECTRONICS BY WORKED EXAMPLES by F. Brogan. Price £2-70.

TELEVISION RECEIVER THEORY I by G. H. Hutson. Price £2-55.

★ TOTAL PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books
19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

ELECTROVALUE

Present

a price-stabilizing policy for 1975

New revised catalogue • attractive discounts • free postage (U.K.)

A 100 OF THE BEST out of our latest catalogue

2N1307	47p	AF200U	40p	BD132	52p
2N2646	51p	AF239	60p	BD135	37p
2N3053	30p	E1906	35p	BD136	39p
2N3054	60p	BA138	31p	BDY20	85p
2N3055	70p	BB103	24p	BF194	15p
2N3702	11p	BB105	34p	BFR39	23p
2N3703	10p	BB109	43p	BFR79	23p
2N3704	11p	BC107A	18p	BFX29	33p
2N3705	10p	BC107B	18p	BFX84	27p
2N3794	18p	BC108B	15p	BFV51	25p
2N3819	25p	BC108C	15p	BRV39	50p
2N4062	11p	BC109B	18p	BY164	51p
2N4443	93p	BC109C	18p	C106B1	42p
2N5062	42p	BC147A	12p	C106D1	47p
2N5163	20p	BC147B	13p	C1406	76p
2N5459	35p	BC148B	12p	MJ481	£1.20
40361	48p	BC149C	13p	MJ491	£1.35
40362	44p	BC158B	15p	MJ2955	80p
40602	46p	BC159	15p	MJE371	89p
40636	£1.36	BC167B	13p	MJE521	81p
40669	£1.10	BC168B	12p	MJE2955	£1.12
AC129	17p	BC169B	12p	CA91	6p
AC151R	36p	BC169C	13p	SD4	8p
AC153	27p	BC179B	26p	TIP31A	70p
AC153K	37p	BC182L	12p	TIP32A	80p
AC176	24p	BC184L	10p	TIP41A	80p
AC176K	38p	BC212L	12p	TIP42A	£1.00
AC187K	31p	BC214L	14p	WO2	30p
AC188K	29p	BC257A	14p	ZTX300	14p
AD133	£1.92	BC259B	14p	ZTX304	23p
AD136	£1.11	BCY58	30p	ZTX500	14p
AD149	52p	BD130	70p	ZTX504	45p
AD161	42p	BD131	48p		
AD162	40p				

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6.3V	10V	16V	25V	40V	63V	100V
0.47	—	—	—	—	—	11p	8p	8p
1.0	—	—	—	—	—	11p	8p	8p
2.2	—	—	—	—	11p	—	8p	8p
4.7	—	—	—	11p	—	—	8p	8p
10	—	11p	—	—	8p	8p	8p	8p
22	—	—	8p	—	8p	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	9p	8p	8p	8p	8p	10p	12p	19p
220	8p	8p	10p	10p	11p	17p	25p	—
470	9p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	—	—	26p	37p	41p	—	—
4,700	—	—	36p	—	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	—	—	—	—	(see note below)
C	—	4.7-470K	1-3	1-1	0-9 nett
C	—	4.7-10M	1-3	1-1	0-9 nett
C	—	4.7-10M	1-5	1-2	0-97 nett
C	—	4.7-10M	3-2	2-5	1-92 nett
MO	—	10-1M	4	3-3	2-3 nett
WW	1	0.22-0.47	16	14	11 nett
WW	1	0.56-3.9Ω	12	10	8 nett
WW	3	1-10K	9p	8p	6 nett
WW	7	1-10K	11	10	8 nett

Codes:

C = carbon film, high stability, low noise.
MO = metal oxide. Electroslit TR5 ultra low noise.
WW = wire wound. Plessey.

Values: All E12 except C & W. C & W and MO & W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.

E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:

5% except WW 10% = 0.05Ω below 10Ω and & W MO 2%.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only.

1975 is the year of challenge. Rather than sit back and wait for things to happen, we have produced our own policy to help stabilize price structure and maintain the services for which ELECTROVALUE are pre-eminent.

PRICES

as shown in our latest catalogue (No. 7, issue 3) will be maintained at least until March 31st next (except in cases of severe market fluctuation) and then held after review for further three month periods instead of making day to day price changes.

CATALOGUE 7 ISSUE 3

is now ready with 108 pages of bargains and information. Price—30p post paid including 25p refund voucher for use on orders list value £5 or more.

DISCOUNTS

apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

FREE POSTAGE AND PACKING

in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under, there is an additional handling charge of 10p.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

V.A.T. at 8%

must be added to total value of orders. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.

ANTEX Soldering Irons

C240	£2.25	Spare bits	32p
CCN240	£2.65	Spare bits	42p

WAVECHANGE SWITCHES

1 pole 12 way 2 pole 6 way	each 33p
3 pole 4 way 4 pole 3 way	11p
TAG STRIP 28 way	

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 21p; 6BA NUTS 28p; 4BA Screws 30p;
6BA Screws 24p; Threaded pillars 6BA;
hexagonal £1.38; Plain spacers 7p; £1.32.

CAPACITORS

DAILY ELECTROLYTIC in cans, plastic sleeved
1000mF/25V 34p 2200/100 £1.91
1000/100 £1.00

5000/100 £3.56 1000/50 50p
2000/150 70p 5000/50 £1.44

5000 25V 75p

POLYESTER TYPE C.280. Radial leads for P.C.B. mounting.
Working voltage 250V d.c.

0.01, 0.015, 0.022, 0.033, 0.047 each 3p
0.068, 0.1, 0.15 each 4p
0.22 5p; 0.33 7p; 0.47 8p; 0.68 11p; 1.0 14p; 1.5 21p; 2.2 24p.

SILVERED MICA. Working voltage 500V d.c. Tolerance 1% or 0.5pF.

Values in pFs—2.2 to 250 in 26 stages each 6p. 270-820 in 9 stages, each 7p.

1000, 1500, 1800 9p; 2200 10p; 2700, 3600, 4700, 5000 16p; 6800, 8200, 10,000 25p.

TANTALUM BEAD

0.1-0.22, 0.47, 1.0 mF/35V, 1.5 20V, 3.5 16V each 16p
2.2 16V, 2.2 35V, 4.7 16V, 10/6 3V each 16p
4.7 35V, 10/16V, 22/6 3V each 21p
10/25V, 22/16V, 27/6 3V, 100/3V, 6.8 25V, 15/25V each 23p

POLYCARBONATE

Type B42540 Working Voltage—250V. Values in mF:
0.0047, 0.0068, 0.01, 0.015, 0.22 each 4p
0.018, 0.027, 0.033, 0.039, 0.047, 0.068, 0.082, 0.1 each 5p
100 V. Values—0.1 5p; 0.12, 0.15 6p; 0.18, 0.22 7p; 0.27, 0.33 8p; 0.39, 0.47 11p; 0.56, 0.68 16p.

CERAMIC PLATE

Working voltage 50V d.c.
In 26 values from 22pF to 6800nF, each 2p.

POTENTIOMETERS

ROTARY, CARBON TRACK

Double wipers for good contact and long working life

P.20 SINGLE linear 100 ohms to 4.7 megohms. each 14p
P.20 SINGLE log. 4.7 Kohms to 2.2 megohms. each 14p
JP.20 DUAL GANG lin. 4.7 Kohms to 2.2 megohms each 48p
JP.20 DUAL GANG log. 4.7 Kohms to 2.2 megohms. each 48p

JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only. each 48p

JP.20 DUAL GANG antilog 10K only. each 48p

2A DP mains switch for any of above 14p extra

Skeleton Carbon Presets, Decades of 10, 22 and 47 only available within limits in ranges above.

Type PR, horizontal or vertical 100Ω-10MΩ. each 6p

SLIDER

Linear or log mono 4.7K to 1 meg. in all popular values

each 30p

STEREO, matched tracks, lin. or log. in all popular values

from 4.7K to 1 meg. 60p

Escutchion plates, mono, black or grey. each 10p

Control knobs, blk/wht/red/yel/grn/blue/dk. grey, lt. grey. each 7p

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules 0-9 and decimal point. 9mm characters in 16 lead DIL. £1.15

Suitable BCD decoder driver 7447. £1.20

3015G showing + or - & 1 & dec. pt. £1.20

LEDS (Light Emitting Diodes) 25p

Photo Cells cadmium sulphide. each 40p

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address.
Dept. PE3. S.A.E. with enquiries requiring answers.

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily. Sat. 9-1 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily. Sat. 9-1 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA. P O Box 27, Swarthmore PA 19081.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7.75
Baker Group 35 3, 8 or 15 ohm	£8.50
Baker Group 50/12 8 or 15 ohm	£12.50
Baker Deluxe 12in d/cone	£10.75
Baker Major 12in d/cone	£8.50
Baker Regent	£7.75
Baker Superb	£14.50
Baker Auditorium 12	£12.50
Celestion MH1000, 8 or 15 ohm	£10.95
Celestion PS18 for Unilex	£3.25
Celestion G12M 8 or 15 ohm	£12.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Coral 6in d/cone roll surr. 8 ohm	£2.50
Coral 8in d/cone roll surr. 8 ohm	£3.25
EMI 13in x 8in 3, 8 or 15 ohm	£2.25
EMI 13in x 8in 150 d/c 8 ohm	£2.50
EMI 13in x 8in 450 l/w, 3, 8 or 15 ohm	£3.75
EMI 13in x 8in type 350 8 or 15 ohm	£8.25
EMI 13in x 8in 20W bass	£6.60
EMI 6in 93850 4 or 8 ohm	£3.00
EMI 5in 14A/7030 mid range 8 ohm	£2.50
EMI 8 x 5 d/cone, roll surr. 10W	£2.50
EMI 2in tweeter 97492AT	£0.65
Eagle DT33 30W tweeter	£5.45
Eagle HT15 horn tweeter	£3.80
Eagle CT5 cone tweeter	£1.75
Eagle CT10 tweeter 8 or 16 ohm	£2.55
Eagle MHT10 horn tweeter	£3.80
Eagle crossover CN23, CN28, CN216	£1.50
Eagle FR4	£5.30
Eagle FR65	£8.35
Eagle FR8	£10.65
Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm	£2.80
Elac 6in 8RM171 d/c roll surr.	£3.50
Elac 6in 6RM220 d/cone	£2.65
Elac 4in tweeter TW4	£1.50
Elac 10in d/cone 10RM239 8 ohm	£2.65
Elac 8in 8CS175 3 ohm	£2.50
Fane Pop 15W 12in	£5.25
Fane Pop 25T 30W 12in	£7.25
Fane Pop 50W 12in	£12.00
Fane Pop 55 50W 12in	£12.50
Fane Pop 60W 15in	£13.25
Fane Pop 100W 18in	£24.50
Fane Crescendo 12A 100W 12in	£29.00
Fane Crescendo 12B bass	£29.00
Fane Crescendo 15in 100W	£36.00
Fane Crescendo 18in 150W	£51.95
Fane 801T 8in d/c roll surr.	£7.00
Fane 807T 8in d/c roll surr.	£3.85
Fane 808T 8in d/c	£2.75
Fane 701 twin ribbon horn	£35.00
Fane 910 horn	£12.75
Fane 920 horn	£33.00
Goodmans 8P 8 or 15 ohm	£5.00

Goodmans 10P 8 or 15 ohm	£5.30
Goodmans 12P 8 or 15 ohm	£12.95
Goodmans 12P-D 8 or 15 ohm	£16.75
Goodmans 12P-G 8 or 15 ohm	£15.75
Goodmans Audiomax 12AX 100W	£36.50
Goodmans Audiomax 15AX	£40.25
Goodmans 15P 8 or 15 ohm	£21.00
Goodmans 18P 8 or 15 ohm	£36.00
Goodmans Midax 750	£16.00
Goodmans Axent 100 tweeter	£7.25
Goodmans Audiom 100 ohm	£12.00
Goodmans Axiom 401 12in	£17.25
Goodmans Twinaxiom 8	£8.25
Goodmans Twinaxiom 10	£9.00
Kel T27	£5.25
Kel T15	£6.00
Kel B110	£7.25
Kel B200	£8.25
Kel B139	£14.25
Kel DN8	£2.00
Kel DN12	£4.95
Kel DN13	£3.30
STC4001G super tweeter	£6.15
Richard Allan CG8T 8in d/c r/surr.	£6.35
2 1/2in 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£0.65
2 1/2in 75 ohm	£0.50
7in x 4in 3 or 8 ohm	£1.40
8in x 5in 3 or 8 ohm	£1.50
10in x 6in 3, 8 or 15 ohm	£2.30

SPEAKER KITS

Baker Major Module	each £10.75
Goodmans Mezzo	each £45.00
Goodmans DIN 20	each £9.75
Helme XLK25	pair £22.00
Helme XLK30	pair £14.95
Helme XLK50	pair £39.95
Kelkit 1	each £20.95
Kelkit 3	each £36.75
Richard Allan Twinkit	each £8.95
Richard Allan Triple 8	each £13.75
Richard Allan Triple	each £19.95
Richard Allan Super Triple	each £23.75
Wharfedale Linton 2 kit	pair £19.25
Wharfedale Glendale 3 kit	pair £34.50
Wharfedale Dovedale 3 kit	pair £52.50

PA/DISCO AMPLIFIERS

Baker Major 100 watt	£49.75
Linear 30/40	£30.00
Linear 40/60	£35.00
Linear 60/100	£58.95
Linear 100 watt slave	£44.00

Eagle PA range in stock—ask for catalogue

FREE with speaker orders over £7

'Hi-Fi Loudspeaker Enclosures' book.
All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair), tweeters and crossovers 20p.
Send stamp for free booklet 'Choosing a Speaker'.
ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF.
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.

CALCULATORS

BUY FROM THE SPECIALISTS
UP TO 45% OFF RRP



All guaranteed 1 year. Money refunded on goods returned within 7 days.

VATMAN £14.91 + VAT

Model	Our Price	Functions
Decimo Valman	14.91	P. [A], R, G, 8D, E, F, K4, H, J, C, L5, B, N.
Decimo Valman	16.91	P. [A], R, G, 8D, E, F, K4, H, J, C, L5, BM, N.
Decimo Memory	23.88	P. M, [A], R, G, 8D, E, F, K4, H, J, C, L5, BM, N, [W].
Decimo Slide rule	25.88	P. M, [A], R, G, 8D, E, F, K4, [H], [X], [J], C, L5, BM, N, S, M, [A], R, G, 8D, E, F, K2, H, J, L5, BM, N.
Decimo £202	39.83	P. M, [A], R, G, 8D, E, F, K4, H, J, C, B, N.
Anita B11	39.95	P. M, [A], R, G, 8D, E, F, K4, H, J, C, B, N.
Bohn Omnitrex*	44.95	T. M, [A], R, G, 8D, E, F, K4, H, J, C, BM, M.
Bohn Omnitrex SQ1*	50.95	T. M, [A], R, G, 8D, E, F, K2, G, [H], [X], [J], C, M, V, U.

JUST OUT
Bohn Metric* 59.22 T. W, [A], R, G, 8D, E, F, K2, H, J, C, V also 12 conversions in/cm, ft/metres, yds/metres, miles/km, ozs/ccs, qt/ltres, gals/ltres, F/C, ozs/grams, lbs/kg, area measurement, cubic measurement.
Bowmar MX75* 39.97 T. M, [A], R, 8D, E, F, K4, H, J, C, V.
Bowmar MX100* 65.99 T. M, 8D, E, F, K4, C, V, J, true scientific 20 functions for algebra, geometry, logs, calculus, integrals, etc.
Special Import 19.90 P. M, [A], R, 8D, E, F/2/4, K4, M, J, C, V, N.
Ricomec 1000P 81.97 2 colour print-out, A, 10D, F/S, K4, M, sub total, acc + X buffer.
Ricomec 1220 121.19 Ditto, plus 12D, [A], 2M, rounding, [W] silent.

Code: A = percentage, B = battery (mainly adaptor only), BM = battery (mainly adaptor incl.), C = carrying case, D = digit, E = +, x, =, F = floating decimal point, F/S = floating point and select, F2 = floating point and 2 places, F7 = floating point and 7 places, G = green display, H = x², x, J = x, K = constant x, K' = constant x, - =, L5 = 50 hr. battery life, L10 = 100 hr. battery life, M = memory, N = negative entry, P = pocket, R = prorating, S = desk model, T = hand and desk, U = display blanking, V = rechargeable, W = exchange, X = V.A. [] extra separate keys, + = positive feed.
50p P & P and please add 8% VAT on all total prices.

BARCLAY ELECTRONICS
STANLEY HOUSE, 1115 FINCHLEY ROAD
LONDON, NW11

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200/220/240V
30W, £2.10; 50W, £2.70; 75W £3.45; 100W, £4.50; 500W, £12.75; 750W, £18.50; 1000W, £28.25, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6-3V 1.5A, £1.45; 3A, £1.80; 6A, £3.80; 12V 1.5A, £1.80; 3A, £3.30; 6A, £4.50; 18V 1.5A, £2.30; 24V 1.5A, £2.30; 30V 1.5A, £2.30; 996V 1.5A, £2.30; 1000V 1.5A, £2.30; 1006V 1.5A, £2.30; 1012V 1.5A, £2.30; 1018V 1.5A, £2.30; 1024V 1.5A, £2.30; 1030V 1.5A, £2.30; 1036V 1.5A, £2.30; 1042V 1.5A, £2.30; 1048V 1.5A, £2.30; 1054V 1.5A, £2.30; 1060V 1.5A, £2.30; 1066V 1.5A, £2.30; 1072V 1.5A, £2.30; 1078V 1.5A, £2.30; 1084V 1.5A, £2.30; 1090V 1.5A, £2.30; 1096V 1.5A, £2.30; 1100V 1.5A, £2.30; 1106V 1.5A, £2.30; 1112V 1.5A, £2.30; 1118V 1.5A, £2.30; 1124V 1.5A, £2.30; 1130V 1.5A, £2.30; 1136V 1.5A, £2.30; 1142V 1.5A, £2.30; 1148V 1.5A, £2.30; 1154V 1.5A, £2.30; 1160V 1.5A, £2.30; 1166V 1.5A, £2.30; 1172V 1.5A, £2.30; 1178V 1.5A, £2.30; 1184V 1.5A, £2.30; 1190V 1.5A, £2.30; 1196V 1.5A, £2.30; 1200V 1.5A, £2.30; 1206V 1.5A, £2.30; 1212V 1.5A, £2.30; 1218V 1.5A, £2.30; 1224V 1.5A, £2.30; 1230V 1.5A, £2.30; 1236V 1.5A, £2.30; 1242V 1.5A, £2.30; 1248V 1.5A, £2.30; 1254V 1.5A, £2.30; 1260V 1.5A, £2.30; 1266V 1.5A, £2.30; 1272V 1.5A, £2.30; 1278V 1.5A, £2.30; 1284V 1.5A, £2.30; 1290V 1.5A, £2.30; 1296V 1.5A, £2.30; 1300V 1.5A, £2.30; 1306V 1.5A, £2.30; 1312V 1.5A, £2.30; 1318V 1.5A, £2.30; 1324V 1.5A, £2.30; 1330V 1.5A, £2.30; 1336V 1.5A, £2.30; 1342V 1.5A, £2.30; 1348V 1.5A, £2.30; 1354V 1.5A, £2.30; 1360V 1.5A, £2.30; 1366V 1.5A, £2.30; 1372V 1.5A, £2.30; 1378V 1.5A, £2.30; 1384V 1.5A, £2.30; 1390V 1.5A, £2.30; 1396V 1.5A, £2.30; 1400V 1.5A, £2.30; 1406V 1.5A, £2.30; 1412V 1.5A, £2.30; 1418V 1.5A, £2.30; 1424V 1.5A, £2.30; 1430V 1.5A, £2.30; 1436V 1.5A, £2.30; 1442V 1.5A, £2.30; 1448V 1.5A, £2.30; 1454V 1.5A, £2.30; 1460V 1.5A, £2.30; 1466V 1.5A, £2.30; 1472V 1.5A, £2.30; 1478V 1.5A, £2.30; 1484V 1.5A, £2.30; 1490V 1.5A, £2.30; 1496V 1.5A, £2.30; 1500V 1.5A, £2.30; 1506V 1.5A, £2.30; 1512V 1.5A, £2.30; 1518V 1.5A, £2.30; 1524V 1.5A, £2.30; 1530V 1.5A, £2.30; 1536V 1.5A, £2.30; 1542V 1.5A, £2.30; 1548V 1.5A, £2.30; 1554V 1.5A, £2.30; 1560V 1.5A, £2.30; 1566V 1.5A, £2.30; 1572V 1.5A, £2.30; 1578V 1.5A, £2.30; 1584V 1.5A, £2.30; 1590V 1.5A, £2.30; 1596V 1.5A, £2.30; 1600V 1.5A, £2.30; 1606V 1.5A, £2.30; 1612V 1.5A, £2.30; 1618V 1.5A, £2.30; 1624V 1.5A, £2.30; 1630V 1.5A, £2.30; 1636V 1.5A, £2.30; 1642V 1.5A, £2.30; 1648V 1.5A, £2.30; 1654V 1.5A, £2.30; 1660V 1.5A, £2.30; 1666V 1.5A, £2.30; 1672V 1.5A, £2.30; 1678V 1.5A, £2.30; 1684V 1.5A, £2.30; 1690V 1.5A, £2.30; 1696V 1.5A, £2.30; 1700V 1.5A, £2.30; 1706V 1.5A, £2.30; 1712V 1.5A, £2.30; 1718V 1.5A, £2.30; 1724V 1.5A, £2.30; 1730V 1.5A, £2.30; 1736V 1.5A, £2.30; 1742V 1.5A, £2.30; 1748V 1.5A, £2.30; 1754V 1.5A, £2.30; 1760V 1.5A, £2.30; 1766V 1.5A, £2.30; 1772V 1.5A, £2.30; 1778V 1.5A, £2.30; 1784V 1.5A, £2.30; 1790V 1.5A, £2.30; 1796V 1.5A, £2.30; 1800V 1.5A, £2.30; 1806V 1.5A, £2.30; 1812V 1.5A, £2.30; 1818V 1.5A, £2.30; 1824V 1.5A, £2.30; 1830V 1.5A, £2.30; 1836V 1.5A, £2.30; 1842V 1.5A, £2.30; 1848V 1.5A, £2.30; 1854V 1.5A, £2.30; 1860V 1.5A, £2.30; 1866V 1.5A, £2.30; 1872V 1.5A, £2.30; 1878V 1.5A, £2.30; 1884V 1.5A, £2.30; 1890V 1.5A, £2.30; 1896V 1.5A, £2.30; 1900V 1.5A, £2.30; 1906V 1.5A, £2.30; 1912V 1.5A, £2.30; 1918V 1.5A, £2.30; 1924V 1.5A, £2.30; 1930V 1.5A, £2.30; 1936V 1.5A, £2.30; 1942V 1.5A, £2.30; 1948V 1.5A, £2.30; 1954V 1.5A, £2.30; 1960V 1.5A, £2.30; 1966V 1.5A, £2.30; 1972V 1.5A, £2.30; 1978V 1.5A, £2.30; 1984V 1.5A, £2.30; 1990V 1.5A, £2.30; 1996V 1.5A, £2.30; 2000V 1.5A, £2.30; 2006V 1.5A, £2.30; 2012V 1.5A, £2.30; 2018V 1.5A, £2.30; 2024V 1.5A, £2.30; 2030V 1.5A, £2.30; 2036V 1.5A, £2.30; 2042V 1.5A, £2.30; 2048V 1.5A, £2.30; 2054V 1.5A, £2.30; 2060V 1.5A, £2.30; 2066V 1.5A, £2.30; 2072V 1.5A, £2.30; 2078V 1.5A, £2.30; 2084V 1.5A, £2.30; 2090V 1.5A, £2.30; 2096V 1.5A, £2.30; 2100V 1.5A, £2.30; 2106V 1.5A, £2.30; 2112V 1.5A, £2.30; 2118V 1.5A, £2.30; 2124V 1.5A, £2.30; 2130V 1.5A, £2.30; 2136V 1.5A, £2.30; 2142V 1.5A, £2.30; 2148V 1.5A, £2.30; 2154V 1.5A, £2.30; 2160V 1.5A, £2.3

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

BARGAINS FROM OUR FREE CATALOGUE

6th edition. 20 large pages filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy by return. Meanwhile, for prompt delivery order from our ad. this month NOW.

B.P.P. TRANSISTOR PACKS ALL AT 50p EACH

TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec diodes. 1,000 PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945
B81	10	Read Switches, 1in long pin dia. Highspeed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked	H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66
H38	30	Short lead Transistors. NPN Silicon Planar types Ex-equipment	H66	4	40362 Type PNP Sil. transistors TO-5 can comp. to H65

UNMARKED AND UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H20	20	BY126.7 Type Silicon Rectifiers 1 amp plastic. Mixed volts
B66	150	Germanium Diodes Min. glass type	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	H67	10	3819N Channel FET's plastic case type
B86	100	Sil. Diodes sub. min. IN814 and IN916 types			

PLASTIC POWER TRANSISTORS—2 ranges

In NPN or PNP at shatteringly low prices under our Tested and Guaranteed terms.

Range 1. V.C.E. Min 15, HFE Min 15	Range 2. V.C.E. Min 40, HFE Min 40
1-12 13-25 26-50	1-12 13-25 26-50
40 watt 20p 18p 16p	40 watt 30p 28p 25p
90 watt 24p 22p 20p	90 watt 35p 33p 30p

Please state NPN or PNP on order.

X-HATCH GENERATOR MK.2



Four patterns—essential for colour TV alignment. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3in x 5in x 3in. Operates from three U-2-type batteries (extra).

Ready built unit only **£9.93**

Complete kit **£7.93**

OVER 1,000,000 TRANSISTORS

of all most-needed types in stock including power, diode, rectifier, etc. Marked, tested and guaranteed. Hundreds of worthwhile bargains are to be found in our FREE CATALOGUE (6th edn.). Also zener diodes, I.C.s, etc.

SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1. Rev. counter device (for cars) £1. UHF/TV Tuner Unit £2.50. LM380 Audio I.C. £1. Technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders. POSTAGE Except where stated, add 15p for postage and packing in U.K. Overseas—add £1. any difference being charged or refunded. PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS. IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg No 820719

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF NECESSARY



CHALLENGING VALUES!

Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatch and include well printed instructions.

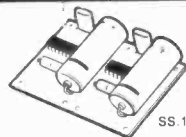

SS.103-3


AMPLIFIER MODULES

Pre-amplifiers; tone control

SS.100 Active tone control unit to provide bass, treble, balance and volume controls **£1.60**

SS.101 Pre-amp for ceramic cartridge, tape and radio **£1.60**

SS.102 Pre-amp for low output magnetic cartridge tape and radio. With R.I.A.A. correction $\pm 1\text{dB}$ at 1kHz **£2.25**

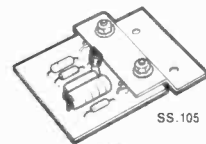

SS.105

POWER AMPLIFIERS


SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6-22. Size 3in x 2in. **£1.75**

SS.103-3 Stereo version of above using one I.C. on each channel **£3.25**


SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2in x 1in. **£1.95**

SS.110 Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26-32V. **£2.40**

SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. T.H.D. better than 0.2%. Power requirements—45V d.c. With 0.15in centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms **£3.60**

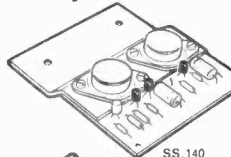

SS.140

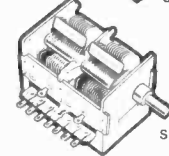


SS.201

TUNER MODULES


SS.201 Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V. **£6.25**

SS.202 I.F. stage (with I.C.). Pre-tuned. A.F.C. connection. Operates from 4.5-14V. **£5.25**

SS.203 Stereo Decoder. Designed essentially for use with SS.201 and SS.202, this module can also be used on most mono F.M. tuners. A.L.E.D. may be attached. Operating voltage 9-16V d.c. **£5.62**

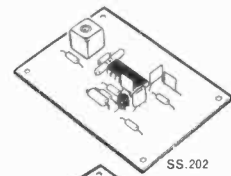


SS.202

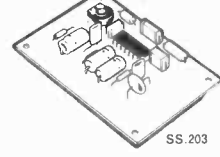

SS.203

POWER SUPPLY STABILISER

SS.300 Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable. **£3.25**

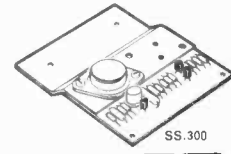

SS.300

- * ALL MODULES TESTED AND GUARANTEED
- * WITH WELL PRINTED INSTRUCTIONS
- * FULL RANGES OF ANCILLARY COMPONENTS AVAILABLE—SEE CATALOGUE

Have you had your FREE CATALOGUE?

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

Please send


for which I enclose inc. V.A.T.

NAME

ADDRESS

PE3

'BIG' Discounts

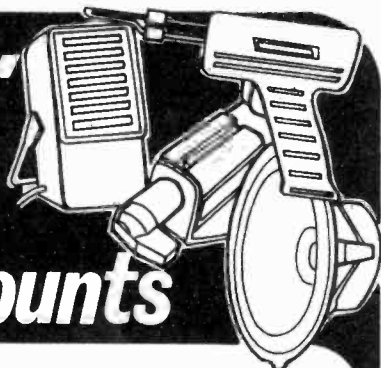

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS			
EMI 13in x 8in 3, 8 or 15 ohm		ELAC 8in 8 ohm Dual cone	2-30
Plain	2-05	ELAC 10in 8 ohm Dual cone	3-50
With Co-Axial Tweeter		GOODMANS 6in 8 ohm Dual cone	2-15
8 ohm only	2-20	FANE, 7in x 4in, 3 or 8 ohm	1-00
Twin Tweeter 8 ohm only	3-95	ADASTRA 10in, 8 or 15 ohm, 10W	3-55
Type 350, 8 ohm, 20W	7-95	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-95
6in, 8 ohm, 10W	2-40		P. & P. 0-40
8in, 8 ohm, 10W	3-75		0-85
12in, 8 ohm, 20W	6-70		0-55
8in x 5in, C/Mag. 5W	1-40		0-15
8in x 5in, Dual cone 8 ohm, 10W	2-55		
ELAC 6in 8 ohm Dual cone	2-15		

TWEETER AND CROSSOVER			
EMI 3in, 3 or 8 ohm C/Mag.	1-30	Donne Tweeter 8 ohm, 30W	5-60
Cone Tweeter 8 or 15 ohm, 10W	2-60	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-30
Cone Tweeter 8 ohm, 3W	1-45		P. & P. 0-15
Horn Tweeter 8 ohm, 20W	6-40		

KIT FORM CABINETS, TEAK VENEER			
12in x 12in x 6in with 8in, 8in x 5in or 6in and 3in cutout	3-40	13in x 8in cutout	4-25
17in x 10in x 9in with 8in or		18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-75
			P. & P. each 0-50

MICROPHONES			
CM70 Planet stick metal, switch crystal	1-55	TW209	5-75
DM160 Dynamic omni-dir, ball metal	4-90	CONDENSER MIKE 600 ohm, uni-dir	9-35
UD130 50K/600 ohm, uni-dir, ball metal	6-40	Cassette Stick Mike with R. Control on/off switch (2-5 and 3-5mm J/Ply)	1-50
			P. & P. 0-30

SOLDERING IRONS			
ANTEX CN240 15W	2-00	spare Bib, etc.	3-40
SK1 Kit (15 watt iron, 2)		X25 25W (low leakage)	2-00
			P. & P. 0-15

CARTRIDGES AND STYLII			
ACOS GP91/28C or 38C Stereo comp.	1-00	SONOTONE 9TAHC or 9TAHC/G diam.	1-90
GP93/1 or 93/1 Stereo crystal	1-35	3509 Stereo ceramic diam.	1-90
GP94/1 or 94/1 Stereo ceramic	1-75	OLD DRING G850	2-95
GP101 Crystal comp.	0-80	G800	3-95
GP104 Stereo ceramic	1-85	G800E	6-90
BSR X5M or 5XH Crystal comp.	1-70		P. & P. 0-15
SX6M or SX6H Crystal comp.	1-90	D. Diamond Stylus for above	1-25
SC5M Stereo ceramic	2-60	G800/G850	1-95
		G800E	3-95
			P. & P. 0-05

BATTERY ELIMINATORS			
240V input 6, 7.5 or 9 300mA	2-95	12V (please specify output) 300mA	2-30
			P. & P. 0-15

TAPES			
8std.	LP	DP	
5in 50p	65p	1-25p	
5in 65p	80p	1-45p	
7in 80p	1-10p	1-80p	

LOW NOISE CASSETTES			
C60	1-5	6-10	11-20
C60	35p	33p	30p
C90	85p	43p	40p
C120	75p	52p	50p

BIB ACCESSORIES			
Tape Editing Kit, Ref. 23	1-35		
Recording Tape Splicer, Ref. 20	1-15		
Cassette Tape, Editing, Ref. 24	1-50		
Cassette Salvage Kit, Ref. 29	0-45		
12" Cassette Case, Ref. 34	1-50		
Stylus Balance, Ref. 32A	1-20		
Spirit Level, Ref. 46	0-50		
Hi-Fi Stereo Test Cassette	2-10		
Groove-Kleen Record Cleaner	1-90		
	P. & P. 0-15		

BIB ACCESSORIES			
Tape Editing Kit, Ref. 23	1-35		
Recording Tape Splicer, Ref. 20	1-15		
Cassette Tape, Editing, Ref. 24	1-50		
Cassette Salvage Kit, Ref. 29	0-45		
12" Cassette Case, Ref. 34	1-50		
Stylus Balance, Ref. 32A	1-20		
Spirit Level, Ref. 46	0-50		
Hi-Fi Stereo Test Cassette	2-10		
Groove-Kleen Record Cleaner	1-90		
	P. & P. 0-15		

CALCULATORS			
SINCLAIR Cambridge Scientific			£19-95
			£29-95

WHARFEDALE SPEAKER BARGAINS			
Linton 2 Kit (pr.)			19-00 1-50
Glendale 3 Kit (pr.)			33-50 2-00
Dovedale 3 Kit (pr.)			52-00 2-00
Denton 2 Speaker (pr.)			30-00 2-50
Linton 2 Speaker (pr.)			39-50 2-50
Dovedale 3 Speaker (each)			42-00 2-50
Glendale 3 Speaker (pr.)			57-00 3-50
Kingdale 3 Speaker (each)			58-95 4-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics
Mail Order Department PE3
P.O. Box 470, Manchester M60 4BU

CJL PRICES INCLUDE P&P AND V.A.T.

□ AERIAL, telescopic, 15-120cm.	£1.20
□ AERIAL, telescopic, h and v swivel, 15-80cm.	£1.78

BIB HI-FI ACCESSORIES

□ CASSETTE TAPE RECORDER CARE KIT	£1.95
□ CASSETTE SPLICING AND EDITING KIT	£1.50
□ HI-FI STEREO TEST CASSETTE	£2.10
□ 1" TAPE EDITING KIT	£1.35
□ GROOV-KLEEN RECORD CLEANER	£1.85
□ EARPHONE, stethoscope style, 8 ohm dynamic	£1.00
□ HAND DRILL, (Leytool), compact precision drill, 5/16" chuck. Gears totally enclosed, S/L bearings.	£2.99

INTEGRATED CIRCUITS

□ AUDIO POWER AMPLIFIER (National) LM380	£1.00
□ A.M. RADIO RECEIVER (RCA) CA3123E	£1.40
□ F.M. STEREO DECODER (Motorola) MC1310P	£2.80
□ TIMER (Signetics) NE555V	£0.78
□ VOLTAGE REGULATOR (Fairchild) uA7805	£1.70
□ VOLTAGE REGULATOR (Signetics) NE550A	£0.80
□ D.I.L. SOCKETS (Pk of 3) 8 or 14 pin	£0.50

□ KEYNECTOR, rapid connect to mains-angle/multiple leads. Built-in piano switches, neon & 13A fuse	£3.20
--	-------

□ LOCKFLEX RULE (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return.	
--	--

A superb rule	£0.93
---------------	-------

□ MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output	£1.80
---	-------

□ MULTIMETER, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA, R-150k	£4.95
--	-------

□ SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv	£3.92
--	-------

□ SOLDERING IRON, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable)	£1.85
---	-------

□ 3/32" bit £0.45 □ 3/16" bit £0.45 □ Element	£0.95
---	-------

□ STAND, ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits	£0.95
---	-------

□ SPEAKER, miniature, 75mm dia, 8 ohms	£0.80
--	-------

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

London College of Furniture

Department of Musical Instrument Technology

Full-time Courses

HIGHER DIPLOMA COURSE:

Advanced studies for those who are 19 years of age or over and who have suitable educational or industrial qualifications.

Higher Diploma in Musical Instrument Technology.
(Subject to approval).

CERTIFICATE COURSES IN:

Piano Tuning, Construction, Repair and Maintenance, Early Stringed Keyboard Instrument Construction, Harpsichord, Clavichords, Fretted Instruments, Guitars, Lutes, Violas and Cellos, Electronics for Musical Instruments.

PART-TIME COURSES:

Block Release or Day Release.

Stringed Keyboard Instrument Design and Manufacture, Violin Making, Early Fretted Instrument Making, Piano Tuning and Maintenance, Woodwind Instrument Maintenance.

ilea

Further information from Senior Administrative Officer, London College of Furniture, 41 Commercial Road, London E1 1LA. Tel. 01-247 1953

Europe's Largest Hi-Fi Retailers

give you the greatest choice

TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv. multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0.0.6.6.30 120/600/1200V D.C. 0.6.6.30 120/600/1200V A.C. Current: 0.0.6.6.60/600mA. Resistance: 0.10 100K. 1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm.



AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: 0.10/50/250/1,000 volt AC and DC. DC current: 0.1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size: 90 x 50 x 28mm. Complete with test leads.



AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edge wise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0.300 uA/0.300mA DC. Resistance: x10 & x100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



HIKI 720X VOM

A versatile, accurate measuring instrument. Ranges: 2000 opv. 0/5/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.



MODEL C7202EN

20,000 op. v. DC. 10,000 op. v. AC. Mirror scale. Ranges: 5.25/50/250/500/1000/2500 V DC. 10/50/100/500/1000 V AC. DC Resistance: x10. x1000 (30); centre scale. DC Current: 50uA. 2.5mA/250mA. -20 to +68 dB.



MODEL PL436

20,000 opv. DC. 8000 opv. AC. Mirror scale. Ranges: 6/12/30/120/600V DC. 3/30/120/600uA/60/600mA. 10/100K/1Meg/10 Meg Ohms. -20 to 46dB.



U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.



HIKI 730X

30,000 opv. Overload protection. Ranges: 6/30/60/120/200V DC. 12/60/120/600/1200V AC. 60uA/30mA/300mA. 2K/200K. 2 Meg Ohm. -10 to 63dB.



U4323 MULTIMETER

20,000 opv. Simple unit with audio/IF indicator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x10. x100. x1,000. x10,000 (50); 500; 5K; 50K (centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.




U435 MULTIMETER

20,000 opv. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 0.5/2.5A AC. Resistance: 0.3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.




MODEL C7208FM

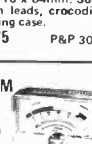30,000 opv. DC. 15,000 opv. AC. Ranges: 6/3/15/60/300/600/1200V DC. 120/600/1200V AC. DC Resistance: x1. x10. x100. x1000 (50); centre scale. DC Current: 30uA. 3/30/600mA. -20 to +63dB.




U4324 MULTIMETER

High sensitivity, overload protected. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size: 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

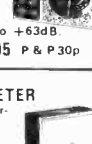

MODEL 500

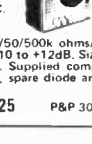30,000 opv with overload protection. Mirror scale. Ranges: 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB.



HIKI MODEL 700X

100,000 opv. Overload protection. Mirror scale. Ranges: 0/0.6/1.2/3/12/30/60/120/300/600/1200V DC. 1.5/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/300mA/6/12A DC. 2k/200k/2M/20M Ohms. -20 to +63dB.



MODEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. Ranges: 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600V AC. 0/10uA/6/60/300mA/12A amp. 0/2k/200k/2M/20 Meg Ohm. -20 to 17dB.



KAMODEN HM7208 FET VOM

Input impedance 10 Megohms. Ranges: 0/25/125/10/50/1000V DC. 0/2.5/10/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms.



KAMODEN 360 MULTIMETER

High sensitivity. DC 100k ohm/V. AC 10k ohm/V. 5" mirror scale. overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/10/100k ohms/10/100M ohms. Decibels: -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads.




Model HT100B4 MULTIMETER

Overload protected, shock proof circuit. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/1/50/250/500/1000V DC. 2.5/10/50/250/1000V AC. DC resistance: 0-20/200k/2/20 Meg ohms. DC current: -10/250uA/2.5/25/250 mA/10A. AC current: -0-10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



370WTR MULTIMETER

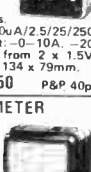Features AC current ranges, 20,000 opv. Ranges: 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, 36mm mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/5/10/50/250mA/1.5A DC. 0.25/0.5/1/5/10/50/250mA/1.5A AC. Resistance: 0.5/10/100/200 ohms/1/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.



MODEL C7208EN

Giant mirror scale. 20,000 opv. Ranges: 0/0.25/1/2.5/10/50/250/1000V DC. 0/2.5/10/50/250/1000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. -20 to +50dB.



MODEL 500

30,000 opv with overload protection. Mirror scale. Ranges: 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/50/250/1000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/2M/20M Ohms. -20 to +63dB.



MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. Ranges: 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V AC. 0/30uA/6/60/300mA/12A amp. 0/10k/1M/10M/100M Meg Ohms. -20 to 17dB.



TMK MODEL 117 FET ELECTRONIC VOLT METER

Battery operated. 11 Meg input, 26 ranges. Large 4 1/2" mirror scale. Size: 149 x 117 x 60mm. 0.3-12000V DC. 3-300V RMS AC. 8-800V P-P. DC current 0.12-12mA. Resistance up to 2000M Ohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.



TMK 100K LAB TESTER

100,000 opv. 6 1/2" scale. Buzzer. short circuit check. Sensitivity 100,000 opv DC. 5kV AC. DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. Current: 10/100uA. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. LED indication. Operates on two 1.5V batteries. Complete with instructions etc.



KAMODEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current at diode current. Amplification factor of PNP, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



U4341 Multimeter & Transistor Tester

27 ranges, 16,700 opv. Overload protection. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/7.5/30/150/300/900V AC. Current: 0.06/0.6/6/60/600mA DC. 0.3/30/300mA AC. Resistance: 0.06/0.6/2/20/200k ohms/2 Megohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.




100TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. Ranges: 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/600uA/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg Ohms. -20 to +50dB. 0.01-0.2 MF. Transistor tester measures Alpha, Beta and Ico. Complete with instructions, batteries and leads.



SWR METER MODEL SWR3

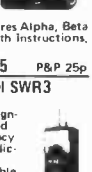Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52 Ohm. Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.



CIS PULSE OSCILLOSCOPE

For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity: 100kHz VRMS/mm. 0.1-25; HOR. AMP. Bandwidth: 500kHz. Sensitivity: 100kHz VRMS/mm. 0.3-25. Preset triggered sweep. 1-2000/sec. Free running 20-200 kHz in nine ranges. Calibrator: 20-200 x 360 x 430mm. 115-230V AC.



ALL PRICES EXCLUDE VAT

Also see following pages

SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR
3 LISLE ST., 311 EDGWARE RD., & 152 FLEET
ST., BRANCHES or order by post.




USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.
Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.90
100uA	£3.85
200uA	£3.80
500uA	£3.75
50-0-500uA	£3.85
100-0-100uA	£3.80
1mA	£3.75
5mA	£3.75
10mA	£3.75
50mA	£3.75
100mA	£3.75
500mA	£3.75
1A DC	£3.75
5A DC	£3.75
10A DC	£3.75
5V DC	£3.75
10V DC	£3.75
20V DC	£3.75
30V DC	£3.75
300V AC	£3.85
VU Meter	£4.00

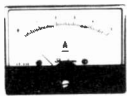

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm


50uA	£4.40
100uA	£4.35
200uA	£4.30
500uA	£4.25
50-0-500uA	£4.35
100-0-100uA	£4.30
1mA	£4.20
5mA	£4.20
10mA	£4.20
50mA	£4.20
100mA	£4.20
500mA	£4.20
1A DC	£4.20
5A DC	£4.20
10A DC	£4.20
5V DC	£4.20
10V DC	£4.20
20V DC	£4.20
30V DC	£4.20
300V AC	£4.30
VU Meter	£4.50



CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm


50uA	£4.05
100uA	£3.95
200uA	£3.90
500uA	£3.85
50-0-500uA	£3.95
100-0-100uA	£3.90
1mA	£3.80
5mA	£3.80
10mA	£3.80
50mA	£3.80
100mA	£3.80
500mA	£3.80
1A DC	£3.80
5A DC	£3.80
10A DC	£3.80
5V DC	£3.80
10V DC	£3.80
20V DC	£3.80
30V DC	£3.80
300V AC	£3.80
VU Meter	£3.80

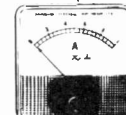

CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.70
100uA	£4.60
200uA	£4.50
500uA	£4.40
50-0-500uA	£4.55
100-0-100uA	£4.50
1mA	£4.40
5mA	£4.40
10mA	£4.40
50mA	£4.40
100mA	£4.40
500mA	£4.40
1A DC	£4.40
5A DC	£4.40
10A DC	£4.40
5V DC	£4.40
10V DC	£4.40
20V DC	£4.40
30V DC	£4.40
300V AC	£4.55
VU Meter	£5.00

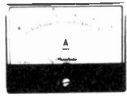

CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3.30
100uA	£3.25
200uA	£3.20
500uA	£3.10
50-0-500uA	£3.25
100-0-100uA	£3.20
1mA	£3.05
5mA	£3.05
10mA	£3.05
50mA	£3.05
100mA	£3.05
500mA	£3.05
1A DC	£3.05
5A DC	£3.05
10A DC	£3.05
5V DC	£3.05
10V DC	£3.05
20V DC	£3.05
30V DC	£3.05
300V AC	£3.15
VU Meter	£3.05



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.60
100uA	£4.55
200uA	£4.50
500uA	£4.45
50-0-500uA	£4.55
100-0-100uA	£4.50
1mA	£4.30
5mA	£4.30
10mA	£4.30
50mA	£4.30
100mA	£4.30
500mA	£4.30
1A DC	£4.30
5A DC	£4.30
10A DC	£4.30
5V DC	£4.30
10V DC	£4.30
20V DC	£4.30
30V DC	£4.30
300V AC	£4.40
VU Meter	£4.80



EDGWISE MODEL PE70

Size: 100 x 34mm

50uA	£4.25
100uA	£4.20
200uA	£4.15
500uA	£4.10
50-0-500uA	£4.20
100-0-100uA	£4.15
1mA	£3.95
5mA	£3.95
10mA	£3.95
50mA	£3.95
100mA	£3.95
500mA	£3.95
1A DC	£3.95
5A DC	£3.95
10A DC	£3.95
5V DC	£3.95
10V DC	£3.95
20V DC	£3.95
30V DC	£3.95
300V AC	£4.05
VU Meter	£4.40



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£8.70
100uA	£8.10
200uA	£8.10
500uA	£8.10
50-0-500uA	£8.10
100-0-100uA	£8.10
1mA	£7.80
5mA	£7.80
10mA	£7.80
50mA	£7.80
100mA	£7.80
500mA	£7.80
1A DC	£7.80
5A DC	£7.80
10A DC	£7.80
5V DC	£7.80
10V DC	£7.80
20V DC	£7.80
30V DC	£7.80
300V AC	£7.80



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£2.90
50-0-500uA	£3.15
100-0-100uA	£3.10
1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
10A DC	£2.85
5V DC	£2.85
10V DC	£2.85
20V DC	£2.85
30V DC	£2.85
300V AC	£2.85
VU Meter	£3.30



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.80
100uA	£3.80
200uA	£3.80
500uA	£3.80
50-0-500uA	£3.80
100-0-100uA	£3.80
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
5V DC	£3.40
10V DC	£3.40
20V DC	£3.40
30V DC	£3.40
300V AC	£3.40
VU Meter	£3.40



CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.80
100uA	£5.65
200uA	£5.50
500uA	£5.40
50-0-500uA	£5.65
100-0-100uA	£5.50
1mA	£5.35
5mA	£5.35
10mA	£5.35
50mA	£5.35
100mA	£5.35
500mA	£5.35
1A DC	£5.35
5A DC	£5.35
10A DC	£5.35
5V DC	£5.35
10V DC	£5.35
20V DC	£5.35
30V DC	£5.35
300V AC	£5.35
VU Meter	£5.35



CLEAR PLASTIC MODEL SD460

Size: 59 x 46mm

50uA	£3.60
100uA	£3.55
200uA	£3.50
500uA	£3.45
50-0-500uA	£3.55
100-0-100uA	£3.50
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
5V DC	£3.40
10V DC	£3.40
20V DC	£3.40
30V DC	£3.40
300V AC	£3.40
VU Meter	£3.75



POSTAGE & PACKING 15p

240° Wide Angle

1mA METERS

MW1-6 60 x 60 mm

£6.50 P & P 15p

MW1-8 80 x 80 mm

£6.90 P & P 15p.



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.

MODEL S260 BENCH MOUNTING

P&P

1A £10.50 50p

2.5A £12.00 50p

5A £17.50 50p

8A £30.35 £1.00

10A £33.75 £1.00

12A £35.40 £1.00

20A £85.00 £1.50

25A £95.00 £1.50

40A £120.00 £1.50



ALL PRICES EXCLUDE VAT



FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 8% VAT to total value of goods including post and packing.

TO LASKYS CUSTOMER SERVICES DIVISION

Audiotronic House, The Hyde, London NW9 6JJ Tel 01-200 1321

Please send me the following items

TOTAL PURCHASE PRICE (inc. P&P and VAT)

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is

NAME

ADDRESS

Signature

Registered in England No. 347947 at 12 Lower Grosvenor Place London SW10E

32 Page Hi-Fi PRICE LIST

BARCLAYCARD & ACCESS

Phone your order to 01-200 0037 or call into any branch

NO DEPOSIT TERMS available on most goods for personal callers

CHEQUES TO THE VALUE OF £30. ACCEPTED FROM PERSONAL SHOPPERS WITH BANKERS CARD. IN OTHER CASES AND FOR AMOUNTS IN EXCESS OF £30. PLEASE ALLOW TIME FOR CLEARANCE. BANKERS DRAFTS ACCEPTED.

All prices correct at 13/1/75 subject to change without notice E.&O.E.

A member of the Audiotronic Group of Companies



Whether your project is electrical or electronic, SCS Components have a complete professional service for the non-professional. We are franchised distributors of Mullard components and Motorola, Ferranti, Signetics, G.I. and Monsanto, too. Our Trade Counter can supply you with all you need, including first-class technical advice. Or simply send cash with your order.

Never before have you been able to get top quality, guaranteed components so quickly, so inexpensively. Send for a free copy of our latest price list. Try us; we think you'll notice the difference.



SCS Components,
Northfield Industrial Estate,
Beresford Avenue, Wembley,
Middlesex HA0 1SD
Tel: 01-903 3168

PLEASE SEND ME _____ COPIES OF YOUR
FREE PRICE LIST
NAME _____
ADDRESS _____

ON GUARD

WHILE technology continually advances, bringing many improvements at the material level, human nature on the other hand seems to undergo little change with the passage of time. For instance, the struggle waged between occupier and trespasser, and between owner and would-be purloiner goes on just as relentlessly today as it did in times long past.

The odds against the criminal have not altered much either, it seems, despite the increasing involvement of electronic and other technical aids. In fact electronics is probably responsible to some extent for the greater abundance of valuable, and often portable, loot that tempts today's criminals. The villains also have access to advanced technology and can, if they are sufficiently determined, surmount or otherwise render innoxious many of the security systems created to deter or defeat them. The safest intruder detection systems obviously are those that do not advertise their presence, or at any rate their vital sensing elements. For in the final reckoning it is immunity from hostile action that makes a security system really 100 per cent. effective.

In this regard security systems relying upon invisible radiations have considerable advantages. Both infra-red and radio frequencies are used in security applications. Some of the more advanced commercial systems employ microwaves and exploit the Doppler shift effect to detect the presence and movement of a body within a protected area. But the use of radio transmitters does bring both the equipment and the intended user within the jurisdiction of the official licensing authority (currently the Home Office, Radio Regulatory Division). The complications involved (which include obtaining design approval for the apparatus concerned) are not likely to be worthwhile for the average person who wishes to build and install his own intruder detection system without fuss or bother. Such needs however are likely to be fully met by a Doppler shift system using ultrasonic radiations. This method can be highly effective in detecting the slightest of movements within the area under surveillance and presents none of the problems of licensing which are associated with radio frequency versions.

This month's design for an Ultrasonic Doppler Shift Intruder Alarm has been fully tested and has proved highly sensitive and consistent in performance in rooms of varying size. Undoubtedly this project will be the answer in many cases where effective monitoring of an enclosed area is required. The equipment can be installed unobtrusively so that its presence (or purpose) is not suspected by unauthorised persons, thus saving it from malicious attentions of technically knowledgeable anti-social types. The importance of this aspect cannot be over-stressed. Electronic techniques can be used for defensive or offensive purposes, and the technical capabilities and resources of today's criminal classes must not be underestimated in any degree.

INCREASE IN COVER PRICE

With effect from this month, the cover price of PRACTICAL ELECTRONICS is increased by 5p to 30p. Further substantial rises in the cost of paper are chiefly responsible. We naturally regret the need for this increase but trust our readers will understand that it is unavoidable.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

ULTRASONIC INTRUDER

A SIMPLE ultrasonic intruder alarm can be made in which the alarm is triggered when the intruder breaks the ultrasonic beam. Unfortunately such a simple arrangement is not very satisfactory since it may be impossible to ensure that an intruder will always pass through the beam. In addition, this type of equipment must be set up very carefully or a sufficient part of the ultrasonic signal will reach the receiver even when the intruder is in the beam and his presence will remain undetected.

This article describes an ultrasonic intruder alarm based on the Doppler shift principle. It can detect the movement of any object within a room when the object has dimensions of not less than a few cms. For example, it has been found that if a person inside the protected area breathes in, the movement of his chest can trigger the alarm. The movement of a person's hand at a speed exceeding about one inch per second can trigger the alarm.

Whilst there is some variation in sensitivity from one point to another the equipment is usually effective throughout most of the volume of a room and

there is no necessity for a burglar to be in any particular region of the room for detection to take place.

DOPPLER SHIFT

The basics of Doppler shift are familiar to everyone who has detected a fall in the frequency of the note received as a fast moving noisy object passes by him. This fall is very apparent in the case of low flying aircraft or when a car passes close to the observer with its horn sounding.

Similarly, if an observer moves towards a stationary source of sound, the frequency he observes will be higher than that emitted by the source.

THEORY

Let us imagine that the stationary source shown in Fig. 1 emits waves at a frequency of f Hz. If the observer is stationary, f waves will pass him per second and he will therefore observe this frequency. If, however, the observer moves towards the source, he will meet more waves per second, since these additional waves are distributed in the space through which he is moving.

The wavelength, λ , of the waves is equal to v/f metres where v is their velocity in metres/second. If the observer moves towards the source with a velocity of b metres/second, he will meet an additional $b/\lambda = bf/v$ waves per second. Thus he meets a total of $(f + bf/v) = f(1 + b/v)$ waves per second. In other words, the movement of the observer towards the source causes the frequency he receives to be raised from f to $f(1 + b/v)$ Hz.

If the observer moves towards the source with a velocity of 1% of the velocity of sound (namely about 3 m/s), the received frequency will be raised by 1%. If the waves are reflected from the observer back towards the source, a person at the source will find that the reflected waves are raised in frequency by twice this amount (that is, by 2%). This is because the observer is reflecting the waves at the

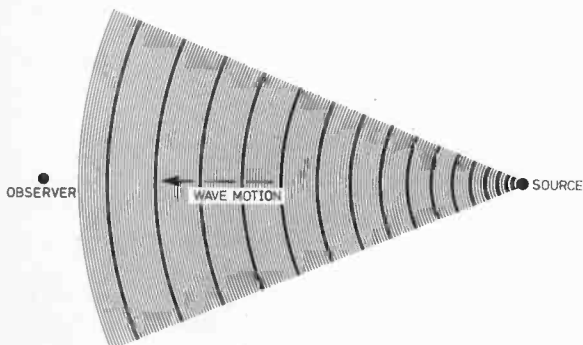


Fig. 1. Wave motion from source to observer, showing how Doppler effects can be observed

DOPPLER SHIFT ALARM

By J. B. DANCE M.Sc.

frequency he is receiving them, but these reflected waves occupy a shorter distance in space owing to the movement of the observer towards the source.

A similar change will occur when the observer moves away from the source, but the frequency of the reflected waves will then be lower than the transmitted frequency.

ULTRASONICS

Let us consider the Doppler effect in ultrasonics when a transducer is employed which emits waves at the typical frequency of 40kHz. If a reflecting object moves at 3m/s, the reflected waves reaching the transducer will have a frequency shift of about 2% of 40kHz, namely 800Hz.

In the case of an intruder moving about in a room, the major components of the velocity of parts of his body are more likely to be in the range 20 mm/s to 1 m/s. The reflected waves therefore reach the transmitter with a frequency shift of roughly 5Hz to 300Hz.

In the present project the transmitting transducer and the receiver of the reflected waves are not in the same position. This will cause the frequency shift to be somewhat reduced (depending on the relative position of the reflecting object), but nevertheless the frequency change will be of the same order. The equipment must therefore be designed to detect shifts in the low audio and sub-audio frequency ranges.

POSSIBLE TECHNIQUES

Various techniques can be employed to detect the frequency shift. All depend on the detection of the frequency difference between the emitted and received frequencies and not on measurement of the frequencies themselves.

It is possible to employ a single ultrasonic transducer to transmit ultrasonic pulses and during the intervals between the pulses, use the transducer as a


receiver of the reflected signals. This would complicate the circuit so much that it would outweigh the saving in the cost of an extra transducer.

BEAT NOTE

In order to keep the project as simple as possible a system which will detect the beat note developed when the transmitted frequency and the Doppler shifted reflected frequency reach the receiver simultaneously is used.

The signal from the receiver transducer is greatly amplified at 40kHz before it is fed to a diode pump circuit. By a suitable choice of time constant, most of the 40kHz signal can be filtered out to leave the audio or sub-audio beat note. This is used to drive a level detector circuit which, in turn, operates a relay.

TRANSMITTER

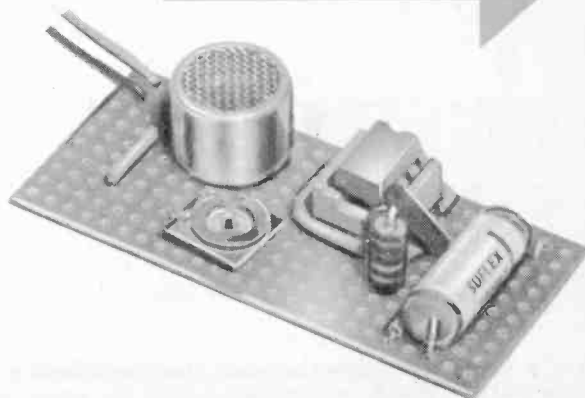

TRANSMITTER CIRCUIT

The circuit of the transmitter is shown in Fig. 2. A 555 integrated circuit is employed so that the circuit can be as simple as possible.

The output at pin 3 continually switches between potentials slightly above that of the negative line and slightly below that of the positive line. This square voltage waveform drives the transducer. The frequency is set by VR1.

THE TRANSDUCERS

The output of the 555 is used to operate a new type of miniature ultrasonic transducer, the 96D-40. This is available in "T" and "R" types for the transmitter and receiver respectively. Optimum results will be obtained only if the "T" type is used in the transmitter and the "R" type in the receiver, although results may be obtained if these units are interchanged.

TRANSMITTER

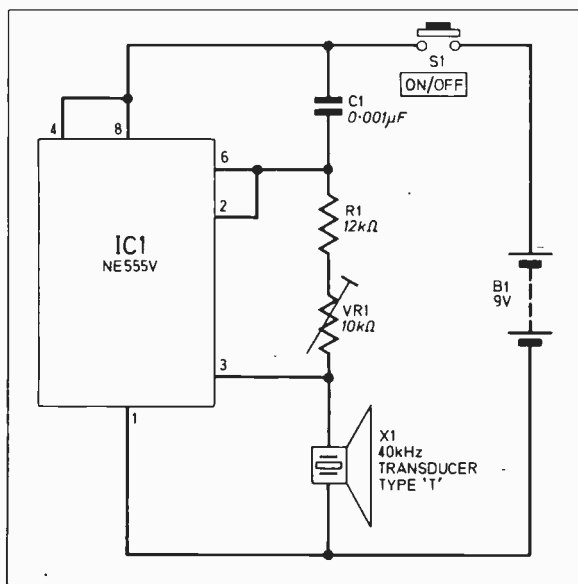


Fig. 2. The transmitter circuit

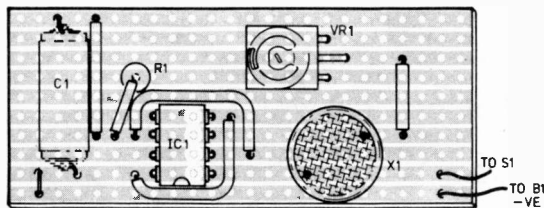


Fig. 5. Component layout and Veroboard cuts for the transmitter of Fig. 2

These transducers contain small piezo-ceramic "bimorph" plates sealed in a small aluminium cylinder slightly over ¼ in diameter. There are two connecting pins on the back and the one connected to the aluminium case should be earthed. The ceramic plates resonate at about 40kHz and cannot be used at frequencies which are more than about 1kHz from this frequency.

When the square wave voltage from the 555 circuit is applied to the transmitter transducer, the ceramic plate resonates and emits an ultrasonic pressure wave into the air through the metal grille at the front of the device.

COMPONENTS . . .

TRANSMITTER

- IC1 NE555V timer i.c.
- C1 0.001µF, 15V, 10% mica or polystyrene
- R1 12kΩ, 10%, 0.1W
- VR1 10kΩ preset trimmer
- X1 40kHz transducer type T, 96D-40 (Hall Electronics)
- S1 SPST on/off switch
- B1 9V battery or suitable p.s.u.

RECEIVER

Resistors

- R1 6.8kΩ
- R2 100Ω
- R3 100kΩ
- R4 390kΩ
- R5 10kΩ
- R6 10kΩ
- All 10%, 0.1W or larger.

Capacitors

- C1 25µF (Fig. 3), 8µF (Fig. 4), 15V elect.
- C2 8µF 15V elect.
- C3 8µF 15V elect.
- C4 8µF 15V elect.
- C5 47pF polystyrene or mica
- C6 0.01µF 63V polyester
- C7 10nF (Fig. 3), 0.1µF (Fig. 4)
- C8 0.1µF (Fig. 3), 1.0µF (Fig. 4)
- C9 500µF (Fig. 3), 0.01µF (Fig. 4)
- C10 1µF
- C11 0.1µF

Semiconductors

- IC1 TAA930 (Phoenix Electronics Ltd., 139 Havant Rd., Portsmouth, PO6 2AA)
- IC2 LM380N audio power amplifier
- TR1 C450, BC109, etc.
- TR2 D40C1 Darlington device (Jermyn Industries Ltd., Vestry Estate, Sevenoaks, Kent)
- D1-5 HG1011, OA95, OA81, 1N914, 1S914, etc. (5 off)

Miscellaneous

Transducers, 96 D-40 types T and R for transmitter and receiver respectively (Hall Electronics, 48 Avondale Rd., Leyton, London, E.17.). 8Ω loudspeaker. Relay RLA, 12V with 2 pair changeover contacts, e.g. GPR100 (Pye TMC Components, Roper Rd., Canterbury, Kent). 8- and 14-pin d.i.l. sockets if required. Veroboard to suit. Die-cast boxes or cases made to suit. Batteries or power supply, wire, solder, etc.

BASIC RECEIVER

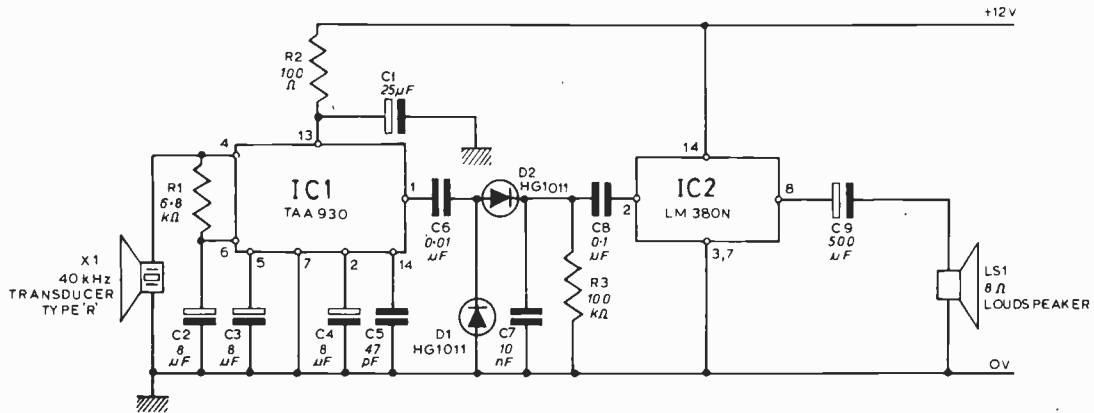


Fig. 3. Circuit diagram of the basic ultrasonic receiver

THE RECEIVER

When an ultrasonic signal strikes the transducer in the receiver a 40kHz signal appears across the transducer terminals. The amplitude of this signal may be of the order of $100\mu\text{V}$. One can amplify this signal by using discrete transistors, but a TAA 930 integrated circuit has been used in this project since it greatly reduces the number of components required.

One of the first circuits used by the writer to detect the beat frequency is shown in Fig. 3. The 40kHz signal from the transducer is first amplified by the TAA 930.

This integrated circuit is actually intended for use in the sound section of television receivers as a 5.5MHz i.f. amplifier/limiter and demodulator. It contains four cascaded differential amplifiers coupled by emitter followers and allows a high gain to be obtained with stability.

The 40kHz output of the amplitude limiter at pin 10 is just over 1V peak-to-peak when the input to pin 4 exceeds the threshold value of about $50\mu\text{V}$. However, the signal at pin 10 is internally connected to the section of the TAA 930 intended for use as an f.m. demodulator. It was found that a low

impedance 8V peak-to-peak 40kHz signal could be obtained from pin 1 (which is the audio output when the device is used in television receivers).

In the circuit shown, the output from pin 1 is fed to a diode pump which has a load with a 1 ms time constant. The audio beat note is developed across this load and in Fig. 3 is fed to an LM380N audio power amplifier which drives a loudspeaker.

IN USE

The transmitter is placed a few feet from the receiver and VR1 of Fig. 2 is adjusted until a maximum voltage is obtained across C7 of Fig. 3. Whenever a person moves his hand or any other object fairly rapidly in the room, the beat note is heard in the loudspeaker. If the movement is very slow, the beat note frequency becomes too low to be heard, as would be expected from the theory.

RELAY DRIVE

The circuit of Fig. 4 is used with the transmitter of Fig. 2 as a true intruder alarm.

As in the circuit of Fig. 3, a low amplitude beat note is formed across C7 of Fig. 4. This is amplified by TR1. This transistor may be any low cur-

RECEIVER ALARM CIRCUIT

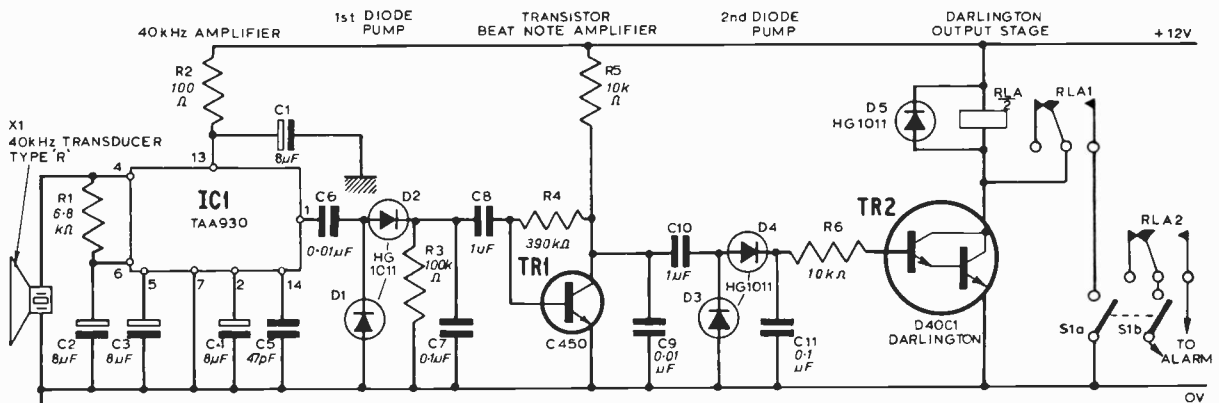


Fig. 4. An alarm receiver circuit including a latching relay at the output


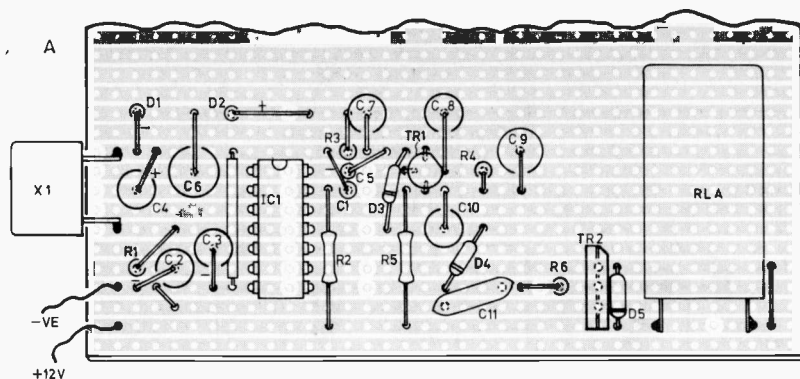


Fig. 6. Component layout and Veroboard cutting details for the receiver of Fig. 4. Note the mounting of the transducer and the extra board space which may be used for power supply or other items

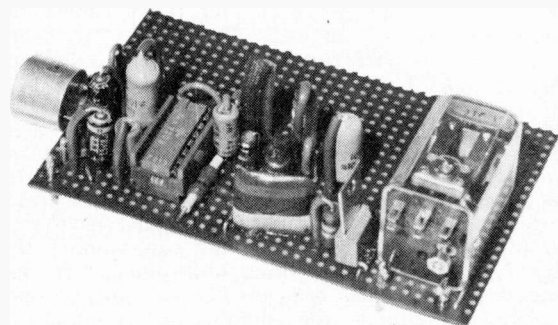

rent, high gain *n*pn transistor. Large coupling capacitors are used so that the circuit will be sensitive to the low (sub-audio) frequency beat notes which occur when the intruder moves slowly.

The output from TR1 is fed to a second diode pump, D3 and D4. This converts the beat note into a steady voltage. When this steady voltage across C11 exceeds about 1.1V, it drives the D40C1 Darlington device into conduction and the relay closes.

The diode D5 across the relay merely removes the transient reverse voltages which appear across the relay coil when the current falls. If D5 is omitted, these transients may damage the D40C1 device. Whilst the writer employed HG1011 diodes, any small low power germanium (or silicon) diodes should be satisfactory in this application. OA95 and OA81 are satisfactory.

LATCH-ON

When the switch S1 is open, the relay will open and close as the amplitude of the beat note rises and falls. The circuit should be tested with S1 open so that one can ascertain how much movement is required to close the relay without having to open S1 in order to de-energise the relay for the next test.

When S1 is closed, the relay will be energised by the beat note as before, but a current will now continue to flow through the relay coil and the contacts RLA1 even when the beat note has ceased. The relay will therefore remain latched on. Contacts RLA2 remain closed after the alarm has been triggered until the equipment is reset by opening the switch S1.

CONSTRUCTION

The transmitter and the final form of the receiver may be made up to suit individual requirements on Lektrokit, p.c.b. or on Veroboard. The transmitter layout is not at all critical but it would be wise with the receiver to keep the input leads as short as possible as the high amplification used can make the unit sensitive to external stimuli.

The prototypes shown in Figs. 5 and 6 are mounted on Veroboard for convenience and component layouts and board cutting details are shown in the figures.

Both models were constructed with a view to mounting in fairly confined spaces both because they are in any case not very large anyway and because this aids concealment if it is not wished to advertise the presence of security equipment. Each unit could be mounted in a false book back made from an old

book from which the "heart" had been cut. The aperture required in the book spine can be covered with fine muslin and painted or dyed to suit the rest of the book.

As can be seen, the receiver is mounted on a larger than needed piece of Veroboard so that, if required, a power supply or, for that matter, batteries, can be mounted on the same board.

If the constructor wishes to mount the units in plain boxes this is equally simple and 6 B.A. holding bolts can be used to secure the boards in place in any suitable die-cast or plastic box without trouble. Of course an aperture would have to be provided in one box wall to which the transducer is presented.


The switch S1 is not mounted on the receiver board as its operation "arms" the system when the transmitter is operating. If set-up by someone in the same room who then leaves, obviously the alarm will be actuated. Under normal circumstances one would house this set/reset switch outside the area to be protected.

ADJUSTMENTS

When each power supply is first connected the current consumption should be checked. It should be about 8mA for the transmitter and about 15mA for the receiver with the relay not operated.

The units should be placed so that the transducers are close together and facing each other. A high impedance voltmeter is placed across C7 of Fig. 4. VR1 of Fig. 2 is adjusted for a maximum reading on this meter. The units are then separated by a few feet and rotated so that the transducers no longer face one another as shown in Fig. 7. A fine adjustment is made to VR1 for maximum reading on the meter connected in the relay unit.

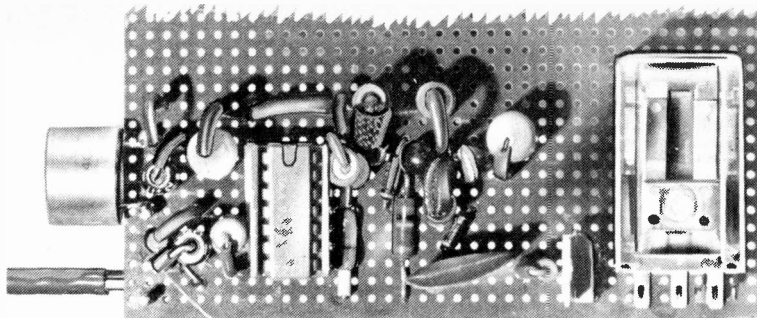This frequency adjustment ensures that the 555 oscillator frequency matches the resonant frequency of the two transducers.



PRACTICAL POINTS

When the prototype units were close together with the transducers facing one another, it was found that the relay always remained closed even when no movement was occurring within the room. Presumably enough of the 40kHz signal then reaches TR1 for it to operate the second diode pump. Variations will occur with the gain of the components used in the relay unit, but the equipment should be set up so that swamping of the receiver transducer by the transmitted frequency does not occur.

Variations of the arrangement shown in Fig. 7 seem to be best. The two transducers point away from one another towards opposite walls of the room. The reflected signal from an intruder and the reflected signal from the walls of the room will then have amplitudes of the same order and optimum sensitivity will be obtained.

As shown the area immediately in front of the transducers is the most sensitive. Regions well away from the front of the transducers are less sensitive, whilst the areas behind the equipment are least sensitive of all. When testing the equipment, remember that one cannot always expect to obtain a beat note if one moves so that one keeps the same distance from the equipment. In practice this is virtually impossible in the most sensitive areas but it may be possible by moving one's hand above the transducers.

CONCLUDING COMMENTS

The circuit is sensitive to movement over almost the whole of the room containing the equipment. It

is virtually impossible for an intruder to enter the room without triggering the system when the equipment is working.

Obviously the equipment has room size limitations but it has been tested successfully in rooms up to 17 x 17ft. Clearly, in a large room some thought should be given to the placing of the equipment in relation to the doors and windows of the room and in relation to any valuable objects requiring special protection.

Remember to shut all windows in the protected room before the equipment is switched on. Otherwise a curtain blowing in the breeze or a bird entering the window can easily trigger the alarm and someone may be aroused from his bed in the early hours of the morning!

If one wishes to have very complete protection, one may arrange that the alarm sounds when either the normally closed contacts of RLA open or when the normally open contacts close. If the intruder cuts the wires to RLA or joins them, the alarm will then sound.

The intruder alarm can, incidentally, form a useful party game where one has to move out of the room extremely slowly without triggering the alarm. In order to give people a reasonable chance, the gain may be reduced by including a resistor in the emitter circuit of TR1.

CRITICAL SETTINGS

The basic circuit does not include the gain control mentioned above and readers may find that in use the receiver is sometimes too sensitive, reacting constantly. A simple way of avoiding this is to detune the transmitter slightly by adjusting VR1.

Further, the receiver will not operate with a reduced power supply and operation will in any case be erratic if supply variations are allowed. So good batteries or a stabilised supply are needed.

The manufacturers' tolerances for the transducers used dictate the final maximum voltages used. As this is 7V the transmitter line voltage should not exceed 9V.

The larger board used in the prototype receiver was selected specifically to accept a small power supply suitably stabilised and set to give the required rail voltages. If the two units are positioned close together, as perhaps in a pair of book ends, then it is not difficult to envisage interconnection and of course supply of the mains voltage.

Output could be along a three-core cable carrying both the connections for S1 and the output switched with a common wire. Thus the system can be wired into an existing system as a simple switch if required.

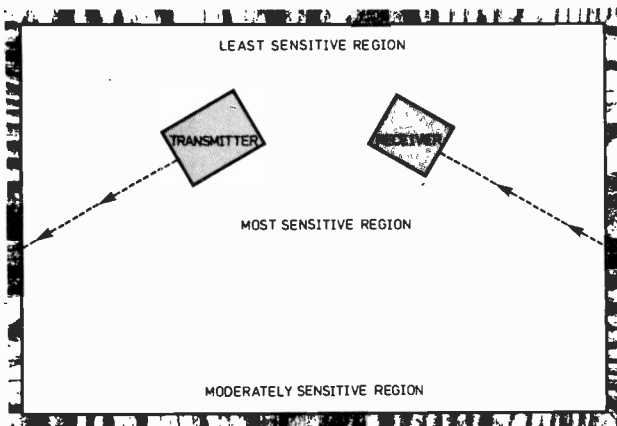



Fig. 7. Locations of the transmitter and receiver in a room for best general effect showing, in general terms, the variations in sensitivity

PE MINISONIC

By G. D. SHAW

PART FIVE

● Making the most of the MINISONIC

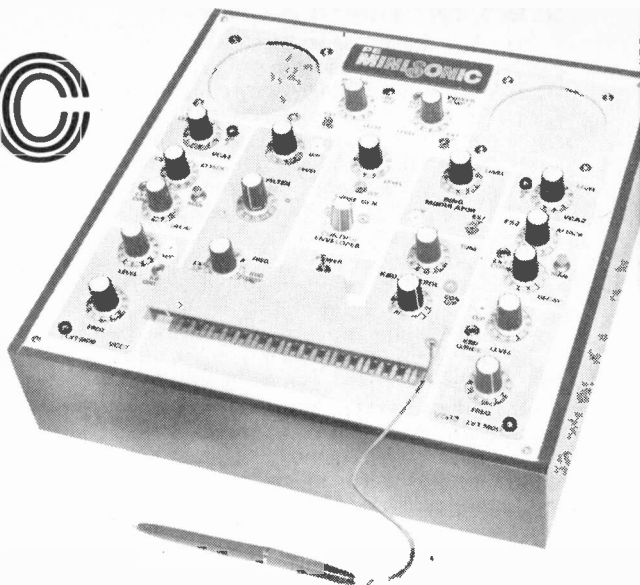

IN THIS the final part of the Minisonic series we will look at some of the ways in which the units of the Minisonic can be connected to produce some interesting effects. These are only suggestions, since the ways in which the Minisonic can be used are limited only by the imagination of the user.

THE VOLTAGE CONTROLLED FILTER

There are three principal ways in which the filter may be used as a sound treatment, of which two have been examined during the check-out procedure. Before going into these in any detail however let us look for a moment at what exactly it is that the filter does to the sawtooth waveform.

Fig. 5.1 illustrates a number of waveforms with the filter control voltage at different levels. In stage

one the control voltage is very low i.e. with the frequency control just off the minimum end stop. If the sawtooth signal is around 1kHz say, the effect of the filter is to remove virtually all the upper harmonics leaving the fundamental which is almost of sine form.

Stage two and three illustrate the situation which occurs when the control voltage is increased successively; in each case the output waveform is assuming more of the sawtooth characteristic albeit still severely rolled off.

In stage four the control voltage is such as to allow the filter to admit the whole of the sawtooth without any roll-off.

Q CONTROL

The degree of roll-off of the filter is affected very largely by the amount of feedback admitted to the ladder network by means of the Q control. With Q at minimum the roll-off is much less accentuated and, indeed, the signal level from the filter is significantly greater than when the Q is at maximum.

Thus, with the Q at minimum the filter can act very much in the same way as a tone control i.e. passing all those frequencies lying below that set by the control voltage and rolling-off all those which lie above the set value at around 6dB per octave.

Increasing the feedback above a critical point will induce the filter to commence self oscillation. Similarly when operating at high Q the filter will also begin to oscillate when the control voltage is advanced beyond a point where the input signal is wholly accepted. This situation is illustrated in stages five and six of Fig. 5.1, the frequency of oscillation being proportional to the increase in ladder current.

What applies, in general terms, to the changes occurring in a sawtooth waveform also applies to other waveforms which are rich in harmonics. In the case of a sine wave input however the effect of the filter is simply to cause a variable degree of attenuation to the signal in a manner dependent on the input frequency, control voltage and Q control settings.

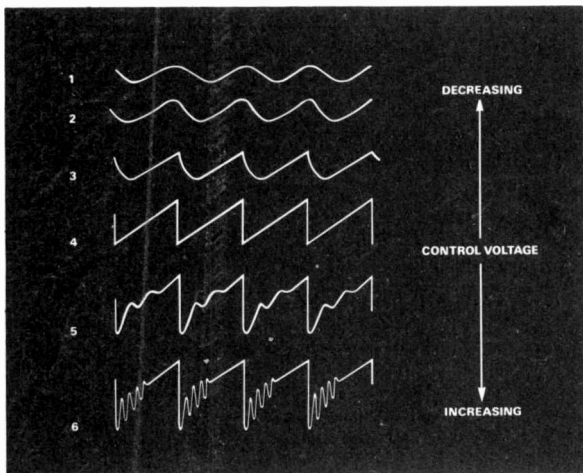


Fig. 5.1. These waveforms illustrate the effect of the VCF on a sawtooth waveform with varying control voltages. The control voltage increases from a minimum at 1 to a maximum at 6

USING THE FILTER AS A VCA

Fig. 5.2 illustrates schematically the method of patching to enable the filter to act as an automatic Waa-Waa or as a voltage controlled amplifier.

In this case the negative output of the CONTROL ENVELOPE INVERTER is patched into the control input (jack socket) of the filter. The VCA level control on channels 1 and 2 should be turned to minimum level and the output of the filter patched into either one of the PA stages.

Set the INVERTER level control about midway with the attack and decay controls of ES1 set about one third of their full rotation.

Place the stylus momentarily on the keyboard and when the resultant sound has decayed away—say in four or five seconds—adjust the frequency control of the filter so that the vco signal is just barely audible.

The keyboard may now be played in the normal way during which time the attack, decay and control envelope controls may be adjusted to achieve the desired effect. Note that the greater the level of the control envelope the harsher will be output signal when the envelope is at its peak.

An inverted Waa-Waa effect can be achieved by setting the filter frequency control to maximum and using the positive going envelope to programme the filter. In this case the output of the filter should be patched into vca1 external input with vco1 level control set to minimum.

TRACKING THE VCO's

With the arrangement of patching as shown in Fig. 5.3 the filter may be used to track the frequency of the vco's. This is because the control input of the filter is directly linked to the output of the HOLD circuit and thus variations in this level will adjust the passband of the filter.

This method of operation is particularly useful if the instrument is being used in an imitative sense or if the constructor wishes to achieve a softer, harmonically reduced output signal. With this mode, the keyboard should be played at the same time adjusting the filter frequency and Q controls until the desired sound is achieved.

It will be found that a number of acoustic instruments can be effectively imitated using this method. For example, wind instruments such as the horn and trombone, string instruments such as the violin and cello and a clarinet tone have all been successfully synthesised with the prototype Minisonic.

THE FILTER AS A TONE CONTROL

In the previous method of operation the passband of the filter was continuously being adjusted as the keyboard was being played such that the proportion of harmonic roll-off was effectively constant regardless of the frequency of the input signal.

If an open circuit jack plug is now placed into the control input socket of the filter the passband is now entirely dependent on the setting of the frequency control. With this at maximum the filter will pass frequencies up to 15kHz (−6dB) more, in fact, than the Minisonic would normally produce in a strictly musical sense.

With the frequency control near its minimum setting the −6dB passband is only 3Hz and thus the greater part of any filtered musical signal from the vco's would not reach the power amplifier stages.

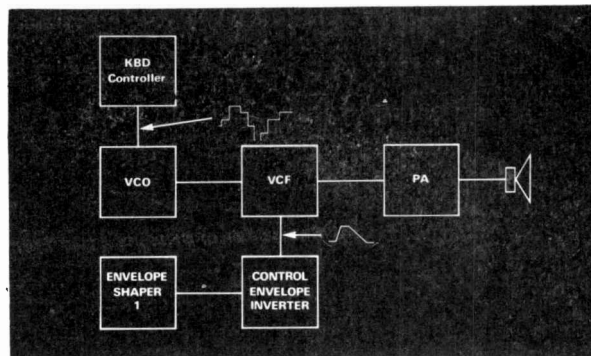


Fig. 5.2. Diagram showing the patching arrangement to use the voltage controlled filter as a Waa-Waa

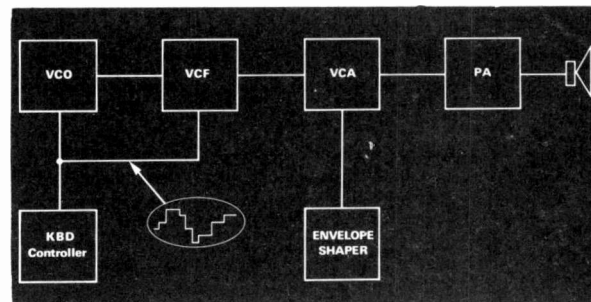


Fig. 5.3. With the patching arrangement shown here the VCF will track the frequency of the VCO's

The filter is now acting as a treble cut system with the degree of cut obtainable being varied by the Q control. With this at minimum the roll-off is about 6dB per octave and at maximum about 15dB per octave.

THE RING MODULATOR

The overall function of the RING MODULATOR has been described elsewhere in this series but it might perhaps be useful to consider some of the uses to which it can be put. In a musical sense the RING MODULATOR can be used to create very rich chord structures.

For example, with both vco's tuned apart by the interval of a fifth, i.e. the frequency of one oscillator is 1.5 times the frequency of the other, the output from the ring modulator will be, in the case of the sum frequency, 2.5 times, and in the case of the difference, 0.5 times, the frequency of the oscillator producing the lowest pitch.

If the output of this latter oscillator is taken as being the fundamental then the output of the RING MODULATOR may be said to comprise the sub-octave and twelfth with respect to the fundamental.

If this signal is now mixed with the outputs of the vco's originating the signals then the end result is a four note, musically concordant chord.

Similar effects may be obtained when the vco's are in unison, an octave apart or tuned to other recognisable musical intervals. In all cases the richness of the resultant sound quite belies the size and complexity of the instrument producing it.

Two methods of patching in the RING MODULATOR to give composite chords are illustrated in Fig. 5.4a and 4b.

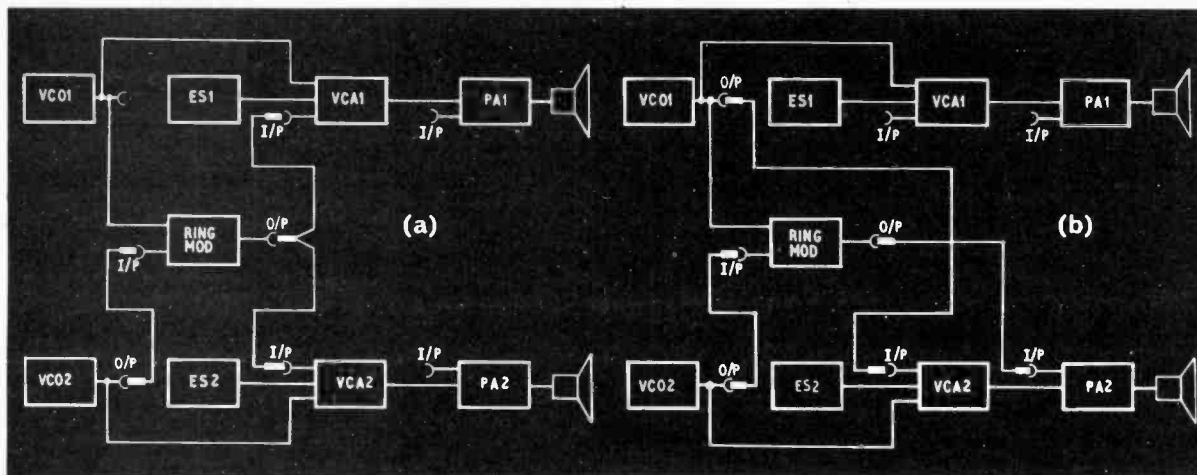


Fig. 5.4a and b. Two methods of patching to give chord effects. In (a) PA1 gives $VCO1 + RING MODULATOR$ output and PA2 gives $VCO2 + RING MODULATOR$ output. In (b) PA1 output is silent and PA2 gives $VCO1 + VCO2 + RING MODULATOR$. In this case ES1 must be disabled by placing an open circuit jack plug in its control input

OTHER RING MODULATOR EFFECTS

Apart from its musical possibilities the RING MODULATOR may be used extensively in the production of sound effects. For example with white noise patched into the uncommitted input and with vco1 running at low frequency—say around 10Hz—the reset point of the sawtooth will be differentiated by the RING MODULATOR input decoupling capacitor such that the output of the RING MODULATOR will comprise a series of staccato cracks akin to machine gun fire. Filtering the output of the modulator can ring the changes quite widely over this one, very simple sound.

Dalek type voices can be produced by the patching arrangement shown in Fig. 5.5. The microphone should be of the ceramic cartridge variety having a fairly substantial output of 100mV or so.

Remember to connect the screen of the microphone lead to the body of the DIN socket. A range of effects may be achieved by varying the frequency of vco1 between about 20Hz and 1kHz bearing in mind that the greater part of the resultant audio signal will be derived from this oscillator.

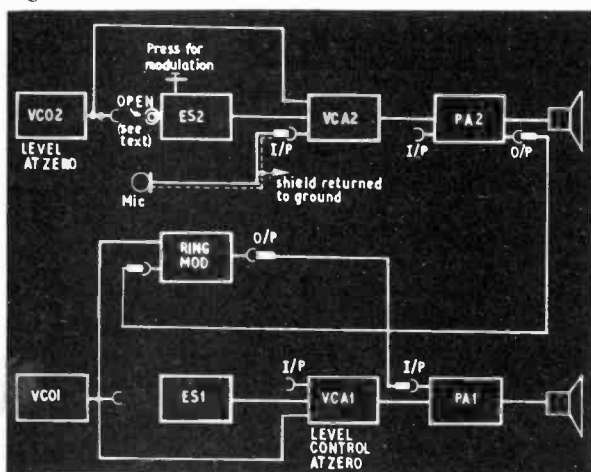


Fig. 5.5. Patching arrangement to give "Dalek" voices. Place open circuit jack plug in ES2 jack socket

If the microphone output appears to be insufficient to fully drive the RING MODULATOR a tape recorder can be employed by first of all taping the required speech and replaying through the Minisonic from the external speaker or earphone output.

NOISE GENERATOR

Other forms of sound effects may be derived from the NOISE GENERATOR in conjunction with the filter. With vco2 level control at zero and the NOISE GENERATOR patched into the audio input of the VCF, set the Q control to maximum and manually swing the frequency control between half and full rotation. The resultant sound will be closely akin to that of howling wind.

Resetting the Q control just off its zero point and swinging the frequency control within its lower half rotation will simulate the sound of heavy, squally rain.

Another interesting experiment with the NOISE GENERATOR and filter combination is to play the passband of the filter from the keyboard. Set Q to a maximum and adjust the keyboard span control so that there is a wider than normal voltage span between consecutive notes. Patch the output of the filter into vca1 and set vco1 level control to zero.

While playing the keyboard adjust the filter frequency control and keyboard span control until there are distinct pitch changes in the audio signal resulting from the playing of successive keys. Pure tones cannot be achieved of course but the ability to change the noise pitch rapidly and predictably comes in very useful when creating say a brush accompaniment line to a pre-recorded melody.

SIMPLE "MULTI-TRACKING"

Those fortunate owners of reel-to-reel recorders with "sound-on-sound" facilities will need no introduction to the methods whereby so-called "multi-tracking" may be employed to produce composite recordings. It is not generally realised however that the humble cassette recorder can also be employed in this way if a second recorder is available.

Fig. 5.6 shows schematically how the "hook-up" may be accomplished bearing in mind that with the

2mm input socket on the PA stage it will be necessary to connect the screen of CR1 output lead to either the DIN socket casing on the Minisonic or to the jack plug shield of the input lead to CR2.

Let us assume that the composite recording is to comprise a simple melodic line punctuated by sound effects of various kinds. The method is as follows:

1. Set the recording level of CR2 and switch to "Record."
2. Play the melodic line as required and check the recording by replaying.
3. If satisfactory, rewind the cassette and transfer to CR1.
4. Set up the patch for the required sound effect and check it.
5. With a fresh cassette in CR2 switch to "Record". Switch CR1 to replay and, at the appropriate time, bring in the required sound effect. This is not as difficult as it might seem because, in order to get the sound effect on to the tape in CR2, the PA level control has to be set fairly high and thus the signal coming from CR1 can be quite clearly heard on the Minisonic loudspeaker. (Remember to set the replay level on CR1 to zero).
6. Repeat steps three to five as necessary until all the required effects have been recorded.

The number of transfers which can be made in the above manner with a cassette recorder is fairly limited due to the generally poor signal to noise ratio of these machines. Nevertheless, if the operation is carried out with care and with regard to recording levels and so on the results are likely to surprise even the most cynical.

ELECTRONIC REVERBERATION

Reverberation in an acoustic sense implies the presence of a series of multiple echoes each following rapidly on the heels of the other, each with a phase difference relative to the other and each, on successive returns, having a diminished intensity.

While the Minisonic does not possess any of the accoutrements normally associated with the production of artificial reverberation, it is nevertheless possible to utilise the long decay characteristic of the ENVELOPE SHAPERS together with the filter to provide a kind of reverberant quality which can be quite pleasing.

REVERBERATION PATCHING

One possible method of patching to achieve this effect is illustrated in Fig. 5.7. Two acoustic channels are used. Channel 2 carries the output from VCO2 together with that of the VCF and has a relatively short envelope decay period. Channel 1 carries the output of VCO1 and the output of the VCF and has a prolonged decay.

If the oscillators are tuned nominally in unison but with a slow beat between them the effect at the VCF is that when the outputs of both oscillators are in phase the total input signal level at the VCF is greater, and therefore more harmonically enriched than when the signals are in antiphase.

Thus when the outputs of the Minisonic are played through the domestic hi-fi system which has the loudspeakers placed reasonably far apart the effect is for the onset of the sound to be central to the listener with a sighing decay to one side or the other.

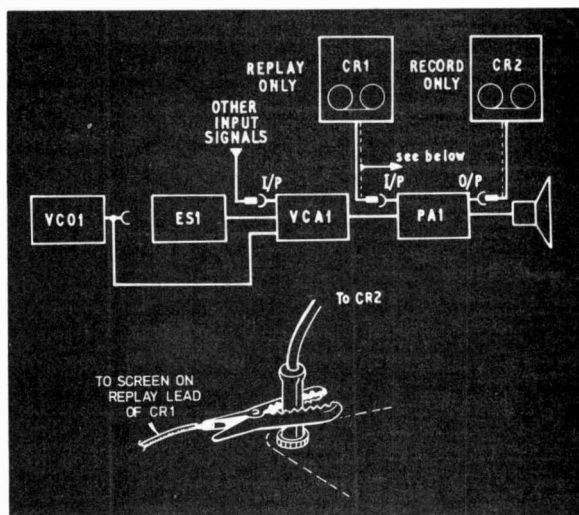


Fig. 5.6. Using two cassette recorders to obtain "multi-tracking". The inset shows how the screen of the replay load can be earthed to the lead from CR2 if metal jack plugs are used

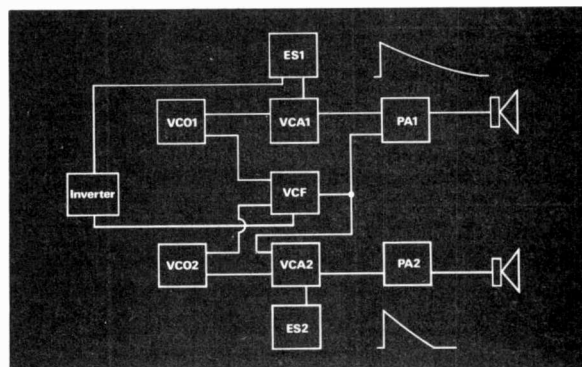


Fig. 5.7. A suggested patching arrangement to give a reverberation effect

With some adjustment to the controls the reverberant quality and spatial movement of the sound can be strikingly effective.

PLAYING THROUGH POWER AMPLIFIERS

The recorder outputs of the Minisonic can be considered to be compatible with the high level inputs to almost all makes of domestic power amplifier. In fact, the playing of the instrument through the domestic system is preferable to using the small monitoring speakers which only have a poor low frequency response. ★

ERRATA:

In Fig. 2.8 (December 1974), breaks shown in column 40 should be repeated in column 21

In Fig. 3.10 and 3.11 a 470μF 16V electrolytic should be connected between +9V rail and 0V. It may be conveniently placed on the Veroboard panel between the two power amplifiers

In Figs. 3.5 and 3.11 (HF DETECTOR), the cathode of D1 should go to -9V not ground

PIONEER II

The second look at Jupiter, a close look, was achieved by *Pioneer 11* early in December. The spacecraft passed inside the proton belt where it was subjected to contact with high energy protons. *Pioneer 10* passed inside the outer shell only. Normally it was to be expected that the spacecraft might have suffered considerably in this passage but the speed of *Pioneer 11*, over 100,000 miles an hour, enabled a safe flight through the proton belt. This remarkable flight took *Pioneer 11* within 26,000 miles of the cloud tops of the planet.

Many of the results from the encounter of Jupiter by *Pioneer 10* were confirmed by *Pioneer 11*. In particular, the very energetic electron emissions into space, modulated in intensity due to the rapid rotation of Jupiter, were encountered when the spacecraft was at the 100,000 mile distance.

It was found that Jupiter is radiating both protons and electrons. This is a puzzle that the teams are attempting to solve. These are found both at the edge and inside the magnetosphere. The extent of this magnetosphere has been confirmed by *Pioneer 11* to be as much as 40 Jupiter radii in the plane of the planet's orbit and as much as 80 radii in the vertical direction. The decametric radiations suggest that the electrons with energies above 3.5 MeV existed as a cause of the radiations. *Pioneer 11* has shown that the flux, deduced from the earthbound observations of radio waves, is rather less than the actual value.

These findings could have far reaching consequences because the level of flux from other sources are usually calculated from the level of radiations that are received. There are some objects, such as the Crab Nebula, that may need a rechecking. On the other hand the synchrotron theory of the radiations, that is the decametre radiations, may need a reappraisal.

Since the fluxes that have been observed at Jupiter are some ten times greater than those calculated from the groundbased observations, there arises very important questions in astrophysics.

JUPITER FINDINGS

The results from *Pioneer 11* are already giving still another possible model of Jupiter. It would appear to be a planet with an extended large magnetosphere which is greatly disturbed by the solar wind and stirred up by the passage of the satellites Amalthea, Io, Ganymede, Callisto and Europa. There appear also to be some special effects of the magnetic fields. For example



the electron densities appear not at the equator of the magnetic field but to the north and to the south.

The convective model suggested by the *Pioneer 10* results is confirmed. Also confirmed is the drop in cloud level towards the poles. The fluid nature and hydrostatic equilibrium of the planet seems to be established beyond doubt.

RED SPOT

The red spot observed by *Pioneer 10* has changed somewhat now. A large white spot has appeared and caught up with the red spot. The tail of the spot seems to be extending. The small red spots that were previously observed have disappeared. The great red spot projects above the surface of the general cloud level by about 5 miles.

The bands at the various latitudes north and south of the planet's equator are in fact the clouds of gas rising from the interior. Because the rotation of Jupiter has a surface velocity of the order of 22,000 miles an hour the clouds are stretched out round the planet to form the bands. This is strikingly different from the clouds on Earth which are formed in circular cyclonic or hurricane patterns.

Other points from the preliminary data refer to the density of the four Galilean satellites. It is shown to have a density of 3.5 grammes/cubic centimetres, Europa 3.4, Ganymede 1.8 and Callisto 1.5. The meteoroid particles which were detected around Jupiter by *Pioneer 10* have been confirmed by *Pioneer 11* as being infalling to the planet. The

experiments to detect such particles have been continued by *Pioneer 11* after leaving the Jovian orbit and suggest that these meteoroids originate from comets.

SATURN FLYPAST

Pioneer 11 has left Jupiter and is on its way to Saturn. Certain re-setting of the track of the spacecraft has been made and it seems that the path will take it through the rings as was hoped. The actual passage should be from above the rings between the gap bounded by the inner rings and the crepe ring.

At the point of "fly through" the spacecraft will be in the shadow of the planet. However, the angle of approach and the angle of departure will be such that the mystery of the rings will be finally settled. The spacecraft will, it is hoped, have a favourable position to take pictures of Titan.

So far calculations point to the date of the encounter of the spacecraft and the planet as being about September 3, 1979.

Pioneer 11 will leave for its journey out of the Solar system in the opposite direction to *Pioneer 10*. Also *Pioneer 11* will be the first of the spacecraft to chart the region above the plane of the ecliptic.


RADIO WAVES FROM EARTH

Since 1970 it has been known that the Earth radiates in a manner similar to the Sun and Jupiter. It was first observed when OS/ carried very low frequency detectors in orbit. This work has been continued on later satellites, one in 1971 and another in 1973. A team from Iowa University have now made a special study of this part of the radio spectrum.

The radiation is very intense and lies between the frequencies of 50 and 500 kHz. It would seem that the level of intensity lies around 10⁹W, as compared with 2 × 10⁷W of the radiations from Jupiter. The Earth radiation occurs at an altitude of under three earth radii. This is the region of high auroral activity.

The team from Iowa have compared the radio storms with auroral photographs from the US Airforce satellite and there seems to be a significant correlation between the pictures and the time of the radio emissions. Usually the radio bursts last for about half an hour to several hours.

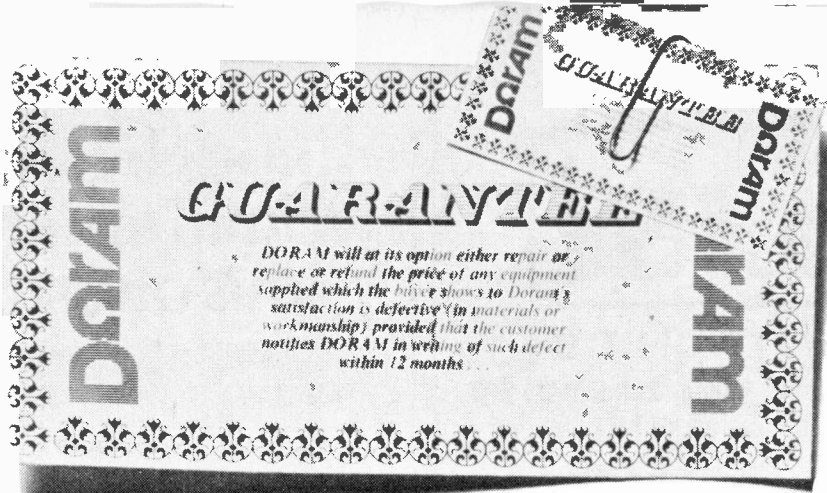The amount of energy which is dissipated during the auroral activity is about 10¹¹W. This suggests that there is 1 per cent dissipated as radio noise. Donald Gurnett, the leader of the Iowa team, thinks that the radiation may originate from a cyclotron process.



With the Doram catalogue, even the guarantee is guaranteed.

Doram is an entirely new way of buying electronic components.

So, to succeed, it's got to have something going for it, right?

We agree with you. And where Doram scores is in the security it gives the amateur buyer.

We'll give you peace of mind three ways.

No-quibble guarantee.

Firstly, we guarantee to replace any component which arrives faulty. Absolutely free of charge.

And secondly, our guarantee is backed by the biggest electronics distribution Group in Britain.

7-day service.

Thirdly, we guarantee you'll have your components within 7 days from our receipt of your orders.

We're so confident of our service that if we can't supply

the part you want within 7 days we'll give you an immediate refund.

So you'll never get a tedious wait.

You know just where you stand with Doram.

All branded goods.

All goods supplied by Doram are made by big-name manufacturers. And they're all to manufacturer's specifications. They're the best money can buy.

In fact, Doram gives the amateur the sort of service only professionals have enjoyed before.

Millions of components.

All in all, we're big enough to offer you stocks of millions of components, on over 4,000 product lines.

All you do is buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager) and then take your pick from it.

Use the coupon now. Send today for the first-ever Doram catalogue. It can take a lot of worry out of amateur components buying.

And for 25p that's not bad, is it?

**I ENCLOSE 25p* PLEASE
SEND ME THE NEW DORAM
CATALOGUE.**

Name.....

Address.....

Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PE/3/75




ELECTRONICS

92 Warwick Road, Ealing, London W5 5PT

Telephone: 01-567 0424

HE 100 100 WATT POWER AMP MODULE

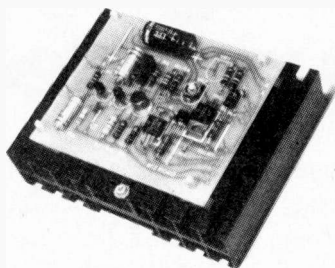

- ★ Includes large black anodised heatsink—no further heatsinks required.
- ★ Top grade glass-fibre P.C.B.
- ★ Uses high quality components.
- ★ Fully protected—short/open circuit proof.
- ★ Only 5 external connections.
- ★ Fully guaranteed.

TECHNICAL SPECIFICATIONS


- ★ Power output : 106W R.M.S. into 8Ω
- ★ Distortion : 0.8% at full O/P. Typ. 0.4%
- ★ Frequency response : 15 Hz–23kHz
- ★ Signal to noise : Better than –96dB
- ★ Input sensitivity : 0dB (0.775V)
- ★ Input impedance : $10k\Omega$
- ★ Supply volts : 45–0–45V

Price £15.12 inc. VAT. (ready built)

Enclose 50p postage & packing.
Power supply for HE 100 (including transformer,
capacitors, rectifier) £8.95 inc. VAT. Postage &
packing 85p.

Pre-amps etc., also available.
SAE for details.

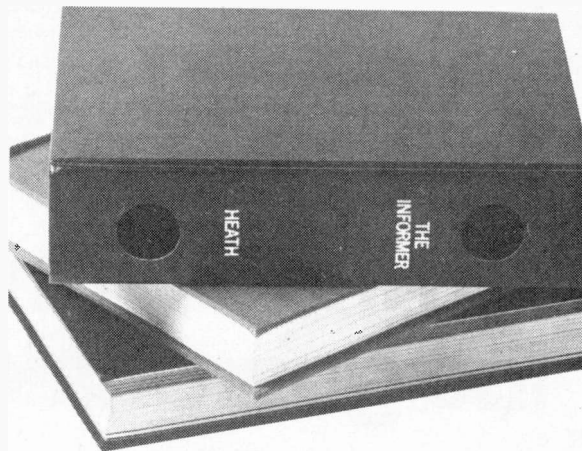Enough books are written about crime, this one stops it.



Outside it's a book. Inside it's an ingenious ultrasonic burglar alarm from Heathkit. The GD-39.

A complete kit that can be assembled in only a few enjoyable hours, with the help of a very easy to follow instruction manual.


The GD-39 works by transmitting a silent, ultrasonic signal throughout the room. And continuously monitoring it. Any movement made by an intruder in the room will then automatically produce a change in the signal. Which triggers off a lamp and, thirty seconds later, a remote buzzer, that just you hear, or a loud bell.

Enough to scare the living daylights out of a burglar.

For more details, and a bookful of other ideas, just post the coupon now for your free Heathkit catalogue.

Or, if you're in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

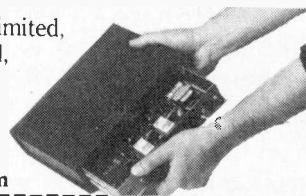Heath (Gloucester) Limited,
Dept. PE35, Bristol Road,
Gloucester GL2 6EE.
Tel: (0452) 29451.



The GD-39 Ultrasonic Burglar Alarm

To: Heath (Gloucester) Limited, Dept. PE35, Gloucester GL2 6EE. Please send me a free Heathkit catalogue.



Name _____

Address _____

Postcode _____

Remember easy terms are available with
the Heathkit Monthly Budget Plan.



INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

An off touch plate could be added as shown dotted so that immediate switching can be effected.

The battery voltage and final transistor selection depends on the bulb used and this in turn depends on the application but in the prototype a BFY51/52 was used. Provided low leakage silicon devices are used no switch is required as the standing current should drop to below $0.5\mu\text{A}$.

The switch S1 is used to keep the torch alight without holding it if this feature is required.

Of course there are other applications for this simple circuit including room lighting and indeed the lamp could be replaced by a triac or relay and be used to give locked switching if required.

P. Sanhen
Sutton, Surrey.

SIMPLE TOUCH SWITCH

THE circuit shown in Fig. 1 was developed as a simple switch for a hand torch. In basic form it will switch itself off after a given delay dependent on the value of C1.

The three transistors form one effective very high gain device and each conducts in turn when a resistance, in this case a finger-tip, is placed between the "on" touch plates. The bulb lights up when the "on" plate is touched and then slowly goes out at a rate set by C1 once the finger is removed.

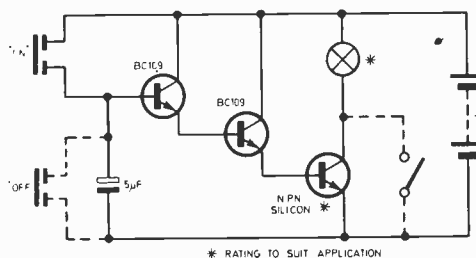


Fig. 1.

THIS simple circuit (Fig. 1) using one i.c., consists of a relaxation oscillator formed by gates G1 and G2 of a 7400 with timing components C1, C2, R1 and R2. The outputs are gated through gates G3 and G4 to the loudspeakers LS1 and LS2 when associated morse keys MK1 and MK2 are operated.

Whilst the frequency may be varied by choice of the capacitors and resistors mentioned, it is probably advisable to stick to the values given since there can be problems with the circuit not starting.

A number of loudspeakers were tried, as well as headphones and all worked well. Although the recommended logic supply voltage is 5V, a 6V lantern battery has been used over a long period with no trouble. Drain in use is about 20mA so battery life is good.

The resistors R5 and R6 are included as current limiters and the loudspeakers may be replaced by l.e.d.s if visual display is required as for example with deaf operators.

A. Ward,
Jersey.

TWO-WAY MORSE TRAINER

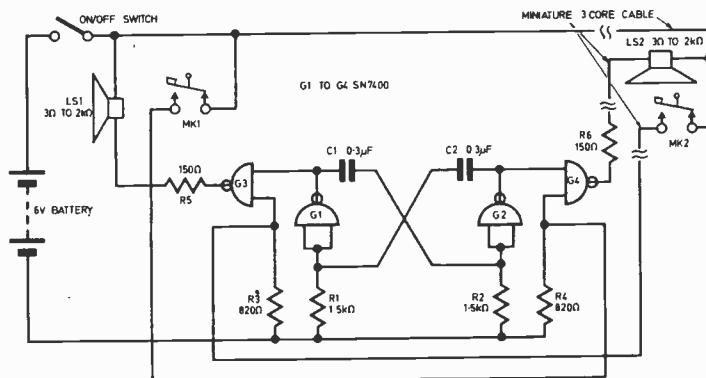


Fig. 1.

TRANSISTOR TESTER

WITH a view to holding costs at a reasonable level and using ex-equipment devices where possible the circuit of Fig. 1 was developed to test transistors.

Used as a plug-in extension to an existing multimeter, the tester will measure I_{coe} from 0 to $30\mu A$ and 0 to $300\mu A$ and β from 0 to 120 and 0 to 300 at $5mA$. The values of the components given are for a multimeter with a $30\mu A$, $1k\Omega$ movement, but calculations for other instruments are quite straightforward.

Heart of the unit is the constant current source, R3, R4, R5, D1, D2, which feeds a known I_b to the transistor under test. The choice of voltage for D1 and D2 is fairly restricted as it has to be high enough to overcome V_{be} variations but sufficiently low to allow a reasonable use of the battery supply. In the event, 6V seems a good compromise.

Neglecting a small I_{coe} , β is given by I_c/I_b which gives

$$R_{base} = \frac{V_{effective}}{I_b} \text{ or } \frac{V_{eff} \times \beta}{I_c}$$

The voltage across the base resistance R_b is only the effective voltage V_{eff} of one diode as the forward voltage of the other is approximately equal to V_{be} . R3 is chosen such that it allows I_b to flow even at a low battery voltage but does not consume excessive power.

As constant alteration of meter setting is not attractive in such an application the flexibility is accommodated in the circuit of Fig. 1 and the meter is used on its most sensitive range. R9 protects overcurrent from flowing in the event of a shorted device. R10 shunts the still

protected meter up to $300\mu A$.

For leakage measurements S3 is open circuit and even though the base is connected to ground via D1 and D2 it is effectively open circuit.

R9 must be shorted for β measurements and R8 is used to shunt the meter to $5mA$. In this position R6 gives some protection, limiting the current to about $15mA$ on short circuit. For a diode test R7 limits the current to $3mA$.

For reliable operation the battery voltage should be greater than 7V and the battery should be capable of supplying $6mA$.

For a transistor holder I used half an 8-pin d.i.l. socket soldered on a piece of Veroboard which in turn was Araldited to the top of a box containing the circuitry and switches.

S4 is connected so that with S4a open and S4b closed both h_{fe} and leakage measurements are at their least sensitive. The meter is less

likely to be overloaded if S4 is kept in this state and switched if needed.

S2 gives *npn* in position a, *pnp* in position b and battery test in position c. For diode testing the device to be tested is inserted in the anode and cathode sockets. If it conducts on *npn* then the anode and cathode terminals indicate actual terminations, if the reverse then the opposite connections apply.

The unit is not intended to be accurate beyond about 10 per cent but devices can be matched to about 2 per cent.

N. E. Thomas,
Oxford.

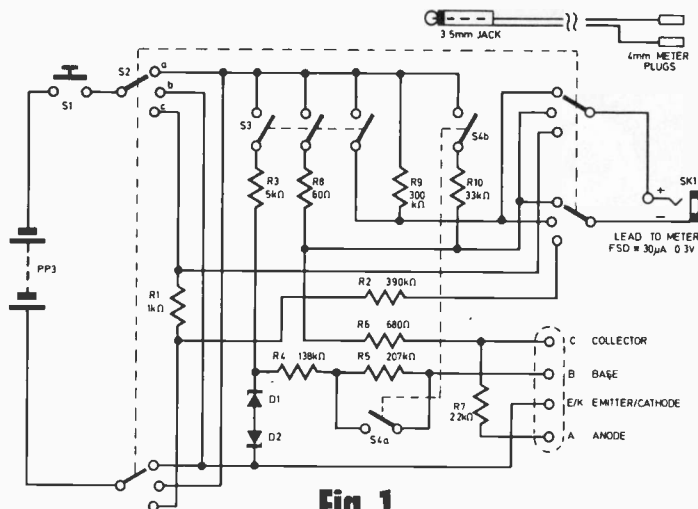


Fig. 1.

LIGHTING CONTROL MODIFICATIONS

SOME readers may find that the circuit used in the "Lighting Control Unit" (July 1973 issue) is not entirely suited to some salvaged components. In particular the transistor TR1.

If a silicon device is used in this position there is a danger of base-emitter breakdown due to reverse bias and this indeed occurred with two BC169C's used in the writer's circuit.

The insertion of protection diodes in the base leads has served to cure the problem quite easily and readily available OA81 devices were used. Equally, OA71 could be used.

A further modification to this useful circuit, shown in Fig. 1, is to include two controls for the original VR1 so as to obtain greater control over some of the effects.

J. Adams,
Oxford.

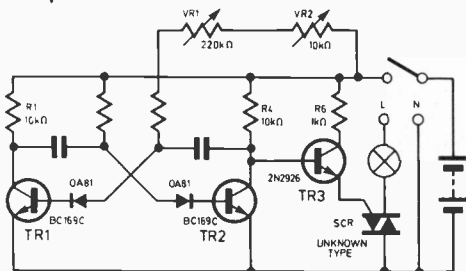


Fig. 1.

POINTS ARISING

P.E. ORION (January and February 1975)

In the components list the case was quoted as being GB3, this should be GB1.

The mains transformer SL8 can be obtained direct from Gardners Transformers Ltd. see Market Place page 234.

P.E. MINISONIC-3 (January 1975)

In the components list, for the H.F. Detector transistor, TR1 was not listed. This should be type BC184.

DIGITAL LEAF (January 1975)

See Market Place page 234.

MARINE SPEEDOMETER (February 1975)

Due to poor reproduction of Fig. 3 it is impossible to identify the breaks in the copperstrips of the Veroboard. Assuming the board is annotated from the top left corner, strips A to NN and holes 1 to 46, the breaks should be made at the following points: 26G, 9J, 12T, X38, CC10, DD10, EE10, FF10, HH19, II19, LL38.

INTRODUCING

SEAS

by Macel

The Elite of Scandinavian Loudspeakers

High Quality High Fidelity Loudspeaker Kits

INTRODUCTORY OFFER INCLUDES VAT AT 8% AND POSTAGE (UK ONLY)

**(ALL KITS INCLUDE FULL WIRING DIAGRAM AND CABINET DRAWING)
(8 ohms impedance)**

Improve your Disco, P.A. and Guitar sound by using these Hi-Fi Kits in recommended compact enclosure designs. These are Hi-Fi speakers of rugged construction capable of withstanding the high power used in the Music Industry and yet the Kits have good sensitivity giving more acoustical power out for a given electrical power input.

Kit 35 illustrated here is particularly recommended for the Music Industry. The recommended enclosure size is 24" x 14" x 10".

Naturally all Kits are ideal for Hi-Fi at home.



Kit 35 (60 watts)

PRICE LIST

The following include High Compliance Bass Units and Cone Middle/Treble Units.

Kit 91H: 2 way and crossover (1 x 6½" plus 1 x 3½") (8-18 litre box) 10 watts 60-20,000 c/s. £7.35 each.
Kit 94H: 3 way and crossover (1 x 11" x 6½" plus 1 x 3½" plus 1 x 2") (25-40 litre box) 25 watts 45-20,000 c/s. £13.25 each.

The following include Neoprene Edge Bass Units and Dome Middle/Treble Units. Outer connecting lead and all internal wiring with mechanical push-on connectors.

Kit 10-2: 2 way and crossover (1 x 6½" plus 1" dome) (8-12 litre box) 20 watts 45-20,000 c/s. £15.35 each.
Kit 18: 2 way and crossover (1 x 8" plus 1½" dome) (15-20 litre box) 30 watts 35-20,000 c/s. £16.30 each.
Kit 30: 2 way and crossover (1 x 10" plus 1½" dome) (25-35 litre box) 35 watt 30-20,000 c/s. £16.95 each.
Kit 35: 3 speakers and crossover (2 x 8" plus 1½" dome) (30-40 litre box) 60 watts 30-20,000 c/s. £23.30 each.
Kit 60: 4 speakers and crossover (2 x 10" plus 1 x 6" x 4" plus 1½" dome) (50-70 litre box) 25-20,000 c/s. £34.95 each.

TO MACEL ELECTRONICS LTD

P.O. Box 64, 14 High Street, Ipswich IP1 3LR.
Tel. 0473 215465
I enclose cheque/postal order

£..... for.....

NAME

ADDRESS

*Please debit my *Barclaycard/Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	7p	BDY20	96p	MJ802/MJ4502		ZTX302	24p
AC107	8p	BF115	30p		£7.65	ZTX303	15p
AC126	25p	BF167	29p	MJ900	£1.88	ZTX304	30p
AC128	22p	BF180	50p	MJ1000	£1.50	ZTX314	18p
AC128/AC176		BF194	18p	MJ4502	£4.00	ZTX320	40p
AC151	26p	BF195	18p	MLM309K	£2.08	ZTX500	20p
AC152	40p	BF196	18p	MPF102	49p	ZTX501	22p
AC153	42p	BF200	46p	MPF103		ZTX502	25p
AC176	29p	BF254	17p	(2N5457)	45p	ZTX503	20p
AC153/176K	71p	BF255	17p	MPF104		ZTX504	60p
AC187K	40p	BF259	39p	(2N5458)	61p	1N914	4p
AC188K	36p	BF284	34p	MPF105		1N3754	18p
AC187/188K	76p	BF285	41p	(2N5459)	45p	1N4001	4p
AC17	41p	BF286	35p	NE555V	78p	1N4002	4p
AC18	28p	BF287	33p	NKT0033	92p	1N4003	5p
AC19	32p	BF288	30p	NKT211	32p	1N4004	7p
AC20	26p	BFY50	33p	NKT212	32p	1N4005	8p
AC21	30p	BFY51	30p	NKT271	22p	1N4006	7p
AC22	10p	BFY52	31p	NKT272	22p	1N4007	9p
AD140	80p	BFY53	28p	NKT275	29p	1N4148	4p
AD149	70p	BFY90	£1.35	NKT279A	36p	1N5400	16p
AD161	64p	BRX29	£1.62	NKT281	22p	1N5404	22p
AD162	64p	BR100	£2.22	NKT401	88p	1N5408	33p
AD161/162	£1.28	BR100	£2.22	NKT401	88p	1N5408	33p
AF106	40p	BR100	£2.22	NKT401	88p	1N5408	33p
AF114	46p	BR100	£2.22	NKT401	88p	1N5408	33p
AF115	40p	BR100	£2.22	NKT401	88p	1N5408	33p
AF116	58p	BR100	£2.22	NKT401	88p	1N5408	33p
AF117	40p	BR100	£2.22	NKT401	88p	1N5408	33p
AF124	38p	BR100	£2.22	NKT401	88p	1N5408	33p
AF125	38p	BR100	£2.22	NKT401	88p	1N5408	33p
AF126	38p	BR100	£2.22	NKT401	88p	1N5408	33p
AF139	64p	BR100	£2.22	NKT401	88p	1N5408	33p
AF186	30p	BR100	£2.22	NKT401	88p	1N5408	33p
AF239	69p	BR100	£2.22	NKT401	88p	1N5408	33p
AF279	74p	BR100	£2.22	NKT401	88p	1N5408	33p
ASV26	70p	BR100	£2.22	NKT401	88p	1N5408	33p
ASV27	72p	BR100	£2.22	NKT401	88p	1N5408	33p
BA138	35p	BR100	£2.22	NKT401	88p	1N5408	33p
BB103	27p	BR100	£2.22	NKT401	88p	1N5408	33p
BB104	50p	BR100	£2.22	NKT401	88p	1N5408	33p
BB105	37p	BR100	£2.22	NKT401	88p	1N5408	33p
BC107	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC107/BC177	46p	BR100	£2.22	NKT401	88p	1N5408	33p
BC108	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC108/BC178	49p	BR100	£2.22	NKT401	88p	1N5408	33p
BC109	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC109/BC179	44p	BR100	£2.22	NKT401	88p	1N5408	33p
BC109C	18p	BR100	£2.22	NKT401	88p	1N5408	33p
BC140	52p	BR100	£2.22	NKT401	88p	1N5408	33p
BC147	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC148	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC149	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC157	17p	BR100	£2.22	NKT401	88p	1N5408	33p
BC158	17p	BR100	£2.22	NKT401	88p	1N5408	33p
BC159	17p	BR100	£2.22	NKT401	88p	1N5408	33p
BC147 157	33p	BR100	£2.22	NKT401	88p	1N5408	33p
BC148 158	31p	BR100	£2.22	NKT401	88p	1N5408	33p
BC149 159	33p	BR100	£2.22	NKT401	88p	1N5408	33p
BC167	15p	BR100	£2.22	NKT401	88p	1N5408	33p
BC168	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC169	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC169C	15p	BR100	£2.22	NKT401	88p	1N5408	33p
BC177	30p	BR100	£2.22	NKT401	88p	1N5408	33p
BC178	35p	BR100	£2.22	NKT401	88p	1N5408	33p
BC179	28p	BR100	£2.22	NKT401	88p	1N5408	33p
BC182	15p	BR100	£2.22	NKT401	88p	1N5408	33p
BC182L	15p	BR100	£2.22	NKT401	88p	1N5408	33p
BC183	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC183L	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC184	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC184L	13p	BR100	£2.22	NKT401	88p	1N5408	33p
BC212	19p	BR100	£2.22	NKT401	88p	1N5408	33p
BC212L	19p	BR100	£2.22	NKT401	88p	1N5408	33p
BC238	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BC238/308	28p	BR100	£2.22	NKT401	88p	1N5408	33p
BC257	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC258	15p	BR100	£2.22	NKT401	88p	1N5408	33p
BC259	16p	BR100	£2.22	NKT401	88p	1N5408	33p
BC307	17p	BR100	£2.22	NKT401	88p	1N5408	33p
BC308	14p	BR100	£2.22	NKT401	88p	1N5408	33p
BCY70	22p	BR100	£2.22	NKT401	88p	1N5408	33p
BCY71	33p	BR100	£2.22	NKT401	88p	1N5408	33p
BCY72	19p	BR100	£2.22	NKT401	88p	1N5408	33p
BD241A	54p	BR100	£2.22	NKT401	88p	1N5408	33p
BD242A	80p	BR100	£2.22	NKT401	88p	1N5408	33p
BD243A	72p	BR100	£2.22	NKT401	88p	1N5408	33p
BD244A	78p	BR100	£2.22	NKT401	88p	1N5408	33p
BD124	£1.00	BR100	£2.22	NKT401	88p	1N5408	33p

COSMOS LOGIC

CD4000AE	46p	CD4017AE	£2.27	CD4030AE	89p
CD4001AE	46p	CD4018AE	£2.27	CD4035AE	£2.23
CD4002AE	46p	CD4019AE	£1.04	CD4040AE	£2.70
CD4007AE	46p	CD4020AE	£2.53	CD4042AE	£1.80
CD4009AE	91p	CD4022AE	£2.23	CD4043AE	£2.02
CD4010AE	91p	CD4023AE	46p	CD4044AE	£2.02
CD4011AE	46p	CD4024AE	£1.62	CD4049AE	72p
CD4012AE	46p	CD4025AE	46p	CD4050AE	72p
CD4013AE	83p	CD4026AE	£3.04	CD4051AE	£2.36
CD4014AE	£2.27	CD4027AE	£1.35	CD4058AE	£1.80
CD4015AE	£2.27	CD4028AE	£1.97	CD4060AE	£3.56
CD4016AE	86p	CD4029AE	£3.06	CD4069AE	46p

MULLARD MODULES

LP1185 FM IF Module	£4.69
LP1186 FM Tuner Module with Diode Tuning	£6.00
LP1400 High performance stereo decoder module using frequency multiplex system	£6.00

ORDER AS TYPE NO. + MULLARD MODULES

DATA AND APPLICATION CIRCUIT FREE WITH MODULE UPON REQUEST

N.B. SEE BELOW FOR SPECIAL DISCOUNT ALLOWANCE

LOGIC PROBE

Powered by 5V DC supply of circuit under test, this device gives instant indication of Logic High (Red) 1 and Logic Low (Green) 0. L.E.D. Indicators.
Leaflet on request
See below for special discount allowance

LIGHT DIMMER BY ANCO

For exciting lighting from Off to full brilliance controlling up to 250 watts. Designed to fit in place of standard wall switches. (Not suitable for Fluorescent Lighting.)

CA3401 QUAD OP. AMP.

Interchangeable with MC3401

INTEGRATED CIRCUIT PINS

The lowest priced IC mounting available. Pin Sockets come in a reel, just drill your board at required centres, drop in pins and solder. Break off frame holders—your DIL mounting is complete!

Pin Sockets	1,000 pieces	£7.00
Pin Sockets	100 pieces	£1.00

NE555V TIMER I.C.

As used in magazine articles including July Practical Wireless.
DATA AND CIRCUITS

CA3123E I.C.

Superhet System with RF Amp. IF Amp. Mixer. OSC. g.c. Detector and Voltage Regulator. Ideal for car radio applications.
APPLICATION SHEET AND DATA

SEVEN WATT AUDIO AMP. I.C.

TBA810S
Featuring thermal protection. Ideal for car radio applications.
APPLICATION SHEET AND DATA



SPECIALISE IN EDUCATIONAL AND GOVERNMENT ORDERS

—See catalogue for further details.



SERVICE PLUS

10% DISCOUNT OVER £4. NO POSTAGE AND PACKING. TOP QUALITY PRODUCTS ALWAYS BY RETURN


COMPREHENSIVE CAT.

Important Notice: All prices are exclusive of V.A.T. Please add V.A.T. to the final total of your order after deducting any discount which may be due.
VAT. REG. 246062672

ARROW ELECTRONICS LTD.

DEPT. PE 12, 7 COPTFOLD ROAD
BRENTWOOD
ESSEX CM14 4BN

SWITCHING POWER SUPPLIES

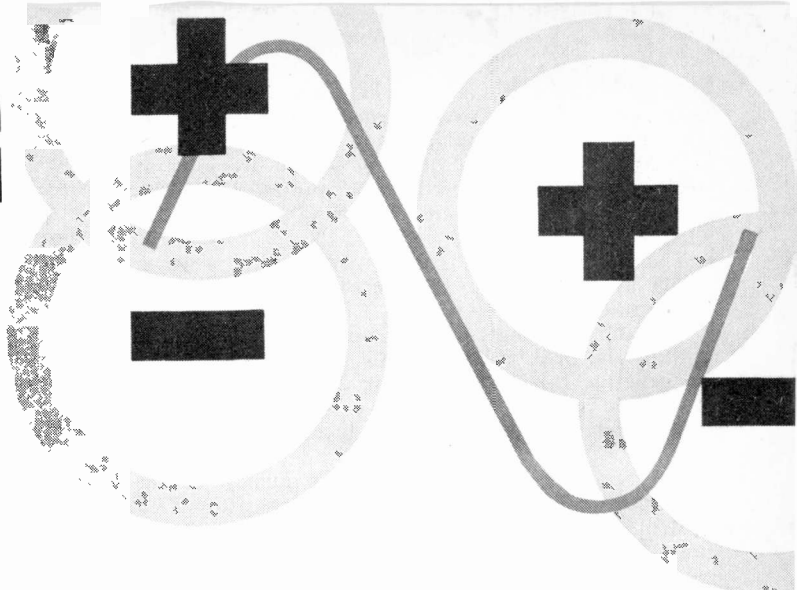

IN THE majority of power supplies, the mains transformer and the smoothing and reservoir capacitors account for most of the bulk and weight. This situation, although unavoidable in the past, is unfortunate because the mains transformer, which contributes a major part of the weight, plays no vital part in the functioning of the power supply, its only real purpose being to isolate the mains from the output of the power supply. In practice the main transformer is also used to step down the input voltage to a convenient level, but this could easily be achieved by other means.

The basic concepts behind transformerless, or switching, power supply units have been known for some considerable time. Unfortunately, until two or three years ago, components capable of putting the ideas into practice were not available.

Switching regulators dispense with bulky 50Hz transformers and smoothing components, yet achieve isolation between the mains and power supply output. The reduction in size and weight achieved is in the order of 8:1 but as with everything else, one does not get something for nothing. However, in the vast majority of cases, the trade-off is extremely worthwhile. In some cases the performances may not be as high as with linear techniques. This point will be dealt with in more detail later in the article.

OPERATING PRINCIPLES

Transformerless or switching power supplies achieve isolation between mains and output by employing a high-frequency transformer as against the

conventional 50Hz transformer and herein lies the secret of the small size of switching power supplies. It is a fundamental fact that the higher the frequency employed the smaller a transformer can become to handle a given amount of power.

The basic principles of switching regulator operation are illustrated in Fig. 1. The mains input is converted to d.c. by a bridge rectifier and smoothing circuit after high frequency filtering. This d.c. is applied to a pair of switching transistors which are driven at tens of kHz by the control circuitry. The square wave output of the switching transistors is applied to a small h.f. transformer, the output of which is rectified and smoothed to provide the output of the power supply. This voltage is compared with a reference voltage and, if a difference exists, an error signal is generated and fed to the control circuitry. The control circuitry adjusts the mark-space ratio of the signal applied to the switching transistors in such a way as to reduce the error signal to zero. Another method relies on a frequency variation. This ensures that the output of the power supply remains constant.

It will be noted that two small high-frequency transformers are employed, one in the main current path and one in the feedback loop, to ensure that the output is isolated from the mains.

The two high-frequency filters stop spurious voltages at the switching frequency and its harmonics from being fed back into the mains wiring and into equipment powered by the power supply.

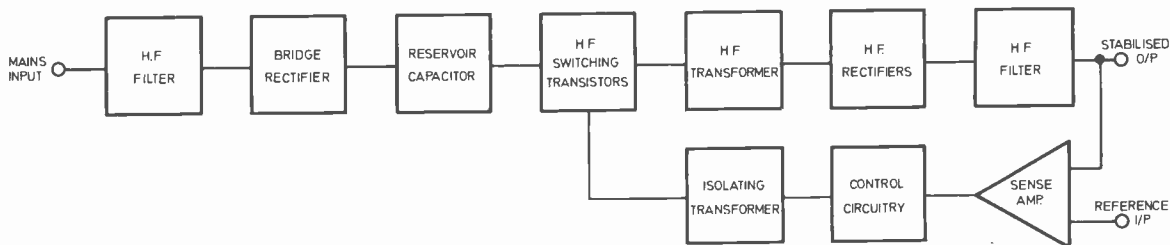


Fig. 1. Block diagram of switching regulator

FIRST SYSTEM

Several circuits have been developed which give a variety of different advantages. The first (see Fig. 2) used a conventional inverter circuit working at 20kHz. This was driven from a multivibrator, the main transistors TR1 and TR2 being alternately on and off.

The output from the transformer is a square wave, which is rectified by fast recovery rectifiers and then smoothed.

The input voltage to the inverter is 150V, thus limiting the peak voltage on the transistors to 300V. To generate this 150V rail, the 240V mains supply is rectified and smoothed to give 340V, which is fed to a switching regulator that reduces the voltage to 150V.

This regulator is a constant frequency circuit with the "on" time of the switching transistor TR3 controlled to keep the rectified output constant via the 150V rail. The two circuits are driven from the same oscillator so that they do not beat together.

Such a unit has four active loss stages and three passive. To remove one of these active loss stages the switching regulator and the inverter must be combined. The normal inverter has alternate stages fully on or fully off, and at all times one stage is on.

The output is set by the turns ratio of the transformers which is fixed, and the input voltage. In the next inverter (Fig. 3) a variable off time is injected between each on period by controlling the ratio of the on and off pulses, thus controlling the output.


The secondary output is a series of pulses of variable mark-space, so that it is now only necessary to filter those pulses to get a mean output, which can then be varied.

CIRCUIT VARIATIONS

Two variations of the circuit are possible depending on the manner in which the mark-space ratio is varied. We can have either a constant on pulse with a variable off time, or a fixed frequency with variable on and off times.

Fixed pulse width gives a system that is free of restraints and is thus more able to overcome sudden overloads interference or mains loss. Since the pulse width determines the ripple voltage for a given choke and output capacitance value, the ripple will remain constant against line and load variations.

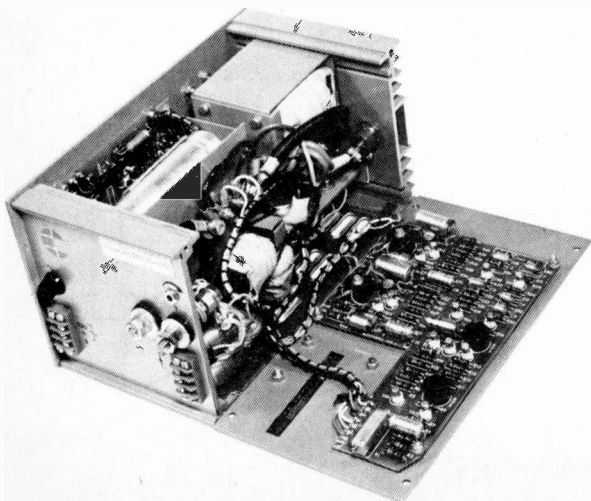Transformerless 4½ to 6V, 50A power supply



Also the circuit can give very large swings of output voltage and input voltage without unlocking. The main disadvantages are that since it operates near the audio range it can, under light load conditions, break into the audio range. Furthermore, as the ripple frequency is variable, it is more difficult to filter out.

The other system (constant frequency) offers an almost exact complement to the fixed pulse width. It is completely quiet under normal working conditions, and filters used external to the equipment can be tuned to give maximum attenuation at this frequency.

It cannot be used over such a wide range of input and output variations, however, and is more prone to jump into an uncontrolled frequency mode of operation.

Both systems are currently in use, depending upon the application.

COMPONENT CONSIDERATIONS

In these two circuits, the components under most danger are the inverting transistors. By using the series type of inverter to limit the peak transistor volts, we have both transistors in series across the line. Control circuits must ensure that both transistors are not turned on at the same time, or a short circuit would be placed across the line, thus destroying one or both of the transistors.

Also, the pulse widths supplied to both transistors on alternate cycles must be identical, or the energy drawn from the series capacitors will be unbalanced. If this happens, the centre voltage will move towards the greater pulse width and the transformer will tend towards saturation.

The output voltage of one side will then fall, and if it falls too low it will not bring its rectifier into conduction. Such a condition is much easier to control in the constant pulse width system.

CONTROL

All control in these systems is by non-dissipating elements apart from saturated switches. Thus the highest dissipation is in the high current output rectifiers. Fast recovery rectifiers have been used for some years with proven reliability, but their saturation voltage is of the order 1 to 1.2V at the currents being used.

Schottky diodes offer an answer to the high dissipation problem in that they have a forward voltage drop of only 0.4V at very high currents and thus considerably reduce dissipation. At present, they only offer an increase in efficiency and not a reduction in size of the heat sink required. This is because their maximum junction temperature is 100°C, so they have to be kept extremely cool.

Transformerless supplies, examples of which are shown in the accompanying photographs, offer three major advantages that are very difficult to provide with linear units. They can operate from mains voltages of from 200 to 264V without tap changes; they can maintain their output voltage at full load with a mains interruption of 30ms, and they can be used over a 0V to 6V range at full current with no tap changes.

In fact they run cooler with lower output voltages, and a 250A 2V unit could easily be produced if it were required. They are thus ideal for use as constant-current units or as bench variables.

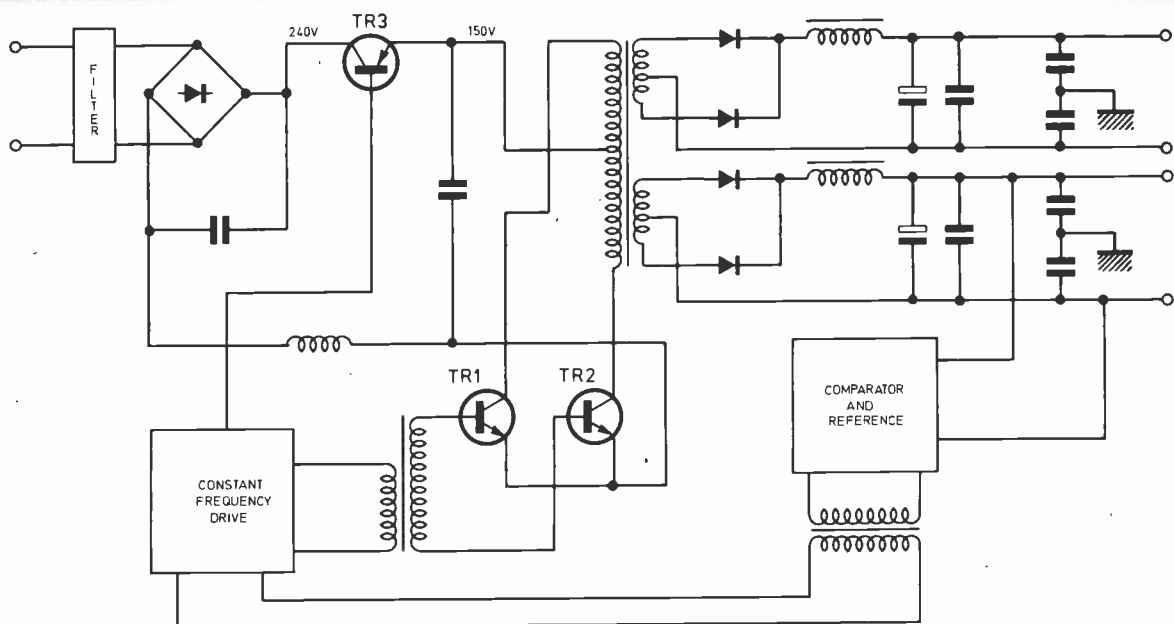


Fig. 2. Conventional inverter circuit diagram

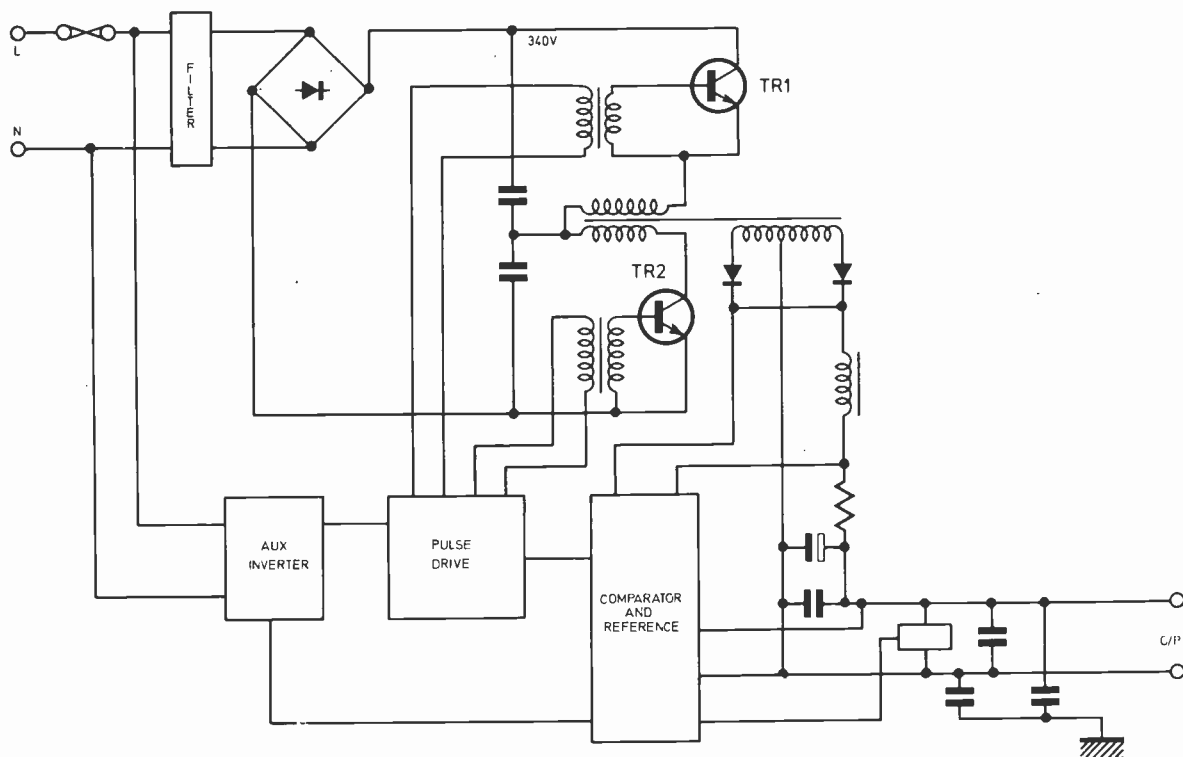


Fig. 3. Variable output inverters

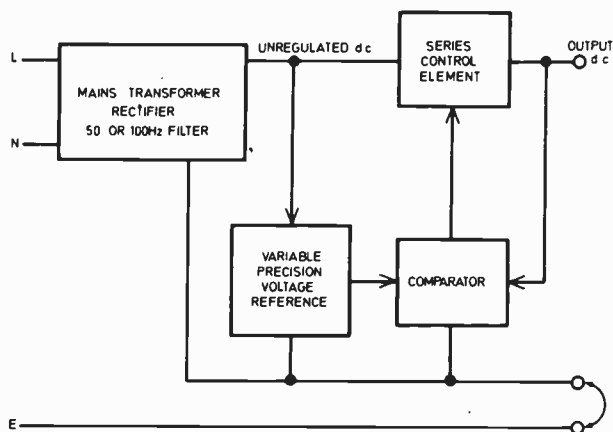


Fig. 4. Linear regulator block diagram

The output specification of these units is satisfactory for TTL circuits, and their use in lightweight desktop equipment is advantageous because of their size and weight.

If any communications equipment is used with these power units, additional screening will probably be required; but even with a large amount of screening their size will prove most attractive.

LIMITATIONS

For highly critical applications, the switching regulator would not normally be used because, inevitably, a small amount of ripple at the switching frequency appears on the output and the transient response is not up to the best that can be achieved by good linear regulators.

However, for many purposes these factors are of no consequence and then the switching regulator

really comes into its own. From the equipment manufacturer's point of view, the space and weight savings enable more compact equipment to be produced at a lower cost.

ONE STEP FURTHER

Having looked at the relative advantages and disadvantages of the switching regulator when compared with the linear regulator, it is now necessary to look at one of the disadvantages of the conventional linear regulator. A block diagram of a typical linear regulator appears in Fig. 4.

The output voltage is compared with a precision voltage reference. If the two differ the comparator either increases or decreases the impedance of the series control transistor to correct the output voltage. To allow the series control element to do its job, the unregulated d.c. from the transformer and rectifier assembly must always be of a higher voltage than the output voltage.

If the power supply had an output which could be varied from 0 to 50V at 10A then the unregulated d.c. supply must be around 55V. At 1V, 10A output, 54V would be dropped across the series control element and 540W would be dissipated in it. This problem is usually overcome by having a range switch which varies the output of the unregulated section so as to limit the power dissipation in the series control element to a reasonable value.

However, large efficient heat sinks are needed for the series control transistor which add to the bulk of the power supply. Due care must be taken with cooling air-flow through the power supply, further adding to the size and weight problems.

A new approach has been recently announced which was developed by APT Electronics Ltd. This involves combining switching and linear regulators in an attempt to achieve the best of both worlds.

COMBINED TECHNIQUES

A number of the disadvantages of both switching and linear regulators can be overcome or minimised by a new technique which combines both linear and

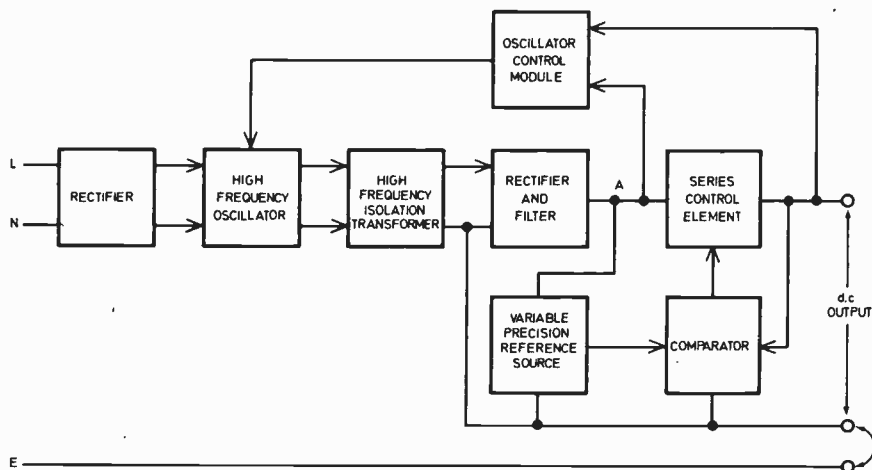


Fig. 5. Power unit incorporating both linear and switching principles

switching regulators in a single unit. A block diagram of a laboratory bench power supply, currently being manufactured by APT, is shown in Fig 5.

Operation of the system is best described by imagining that the unit is switched on and is supplying an output, say 40V, to a load. Point A on the circuit must be at a potential of more than 40V for the series control element to function. For reasons which will become clear later we will state that point A is at 45V.

If the voltage reference source output is deliberately lowered to 30V the comparator will provide an output which will increase the impedance of the series control transistor so as to reduce the output of the power supply to 30V. As this is taking place the voltage drop across the series control element would tend to rise. The oscillator control module senses this increase and lowers the duty cycle of the oscillator so the input voltage to the series element falls. Circuit values are such that the voltage across the series element is maintained at 5V.

With 30V now at the output, therefore, point A will be at 35V. The technique ensures that even for a 0 to 50V 10A power supply, power dissipation in the series control element is limited to 50W even at the normal worst case condition of 1V output at 10A.

The main advantages of the technique are therefore the elimination of the 500W mains transformer and bulky 100Hz smoothing components, and a considerable reduction in internal power dissipation allowing smaller heat sinks to be used.

Such a power supply does not perform as well as a good quality series linear regulator but is much better than a straight switching regulator. For a 50V, 10A power supply the relative advantages of the linear series, switching and combined switching series regulators are summarised in Table 1.


Table 1.

Parameter	Linear	Switching	Linear/ Switching
Regulation	Excellent	Good	Good
Transient response	Excellent	Poor	Fair
Ripple and noise	Excellent	Poor	Good
Ease of output voltage adjustment	Fairly easy	Fairly difficult	Easy
Size	Very large	Very small	Small
Weight	Very heavy (90lb)	Very light (10lb)	Very light (16lb)

A photograph of the combined switching and linear regulator is shown.

THE FUTURE

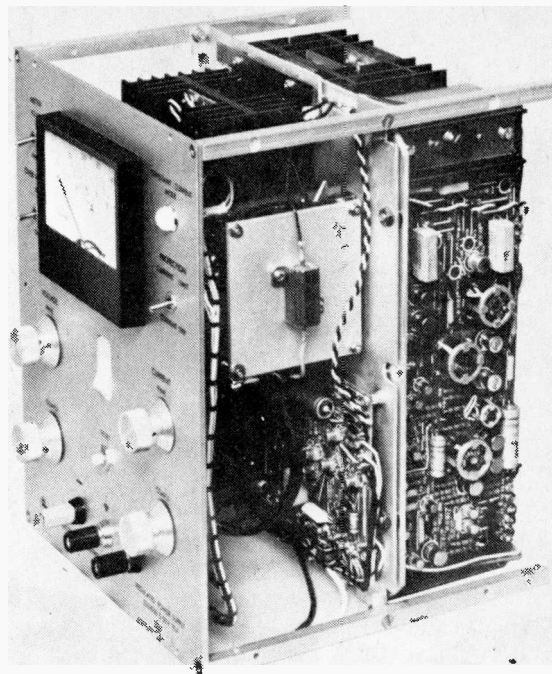Power supply performance will continue to improve and will be assisted by monolithic integrated circuit and thick film hybrid microcircuit developments.



The SSU 10-50, 0 to 50V, 500W laboratory power supply from APT Electronics

Thick film microcircuits consists of a substrate (or base material) on which the circuit to be manufactured is printed. Conductors are printed with palladium, or similar ink and resistors will be formed by printing with one of the many inks available for this purpose. The printed substrate is "baked" in a furnace and then active components such as transistors and integrated circuits are added.

Hybrid microcircuits are very reliable, much more reliable than the printed circuit board with separate components, and can be designed to have a uniformity of performance very difficult to achieve by other means.

This last point is very important in power supply manufacture and indeed complete regulator control circuits using monolithic chips and discrete components are manufactured in hybrid microcircuit form at Coutant's Ilfracombe factory.

Any improvement in the monolithic results in an improvement in the hybrid. The two techniques are therefore complementary. ★

P.E. STAFF VACANCY



There is a vacancy for a technical sub-editor on the staff of Practical Electronics. An interesting and satisfying job for an electronics enthusiast. Sound technical knowledge and practical experience more important than journalistic experience.

Write with brief personal details to The Editor, Practical Electronics, Fleetway House, Farringdon Street, London EC4A/4AD.

... IN CIRCUIT

OHMMETER

By O.N. BISHOP

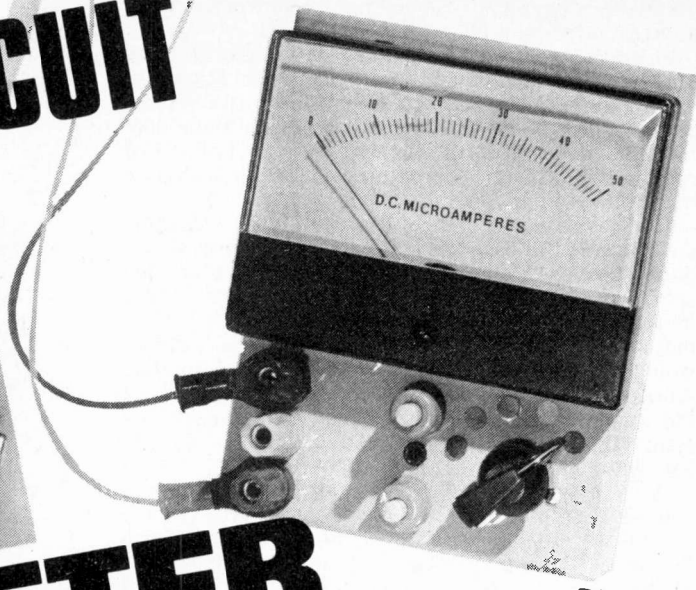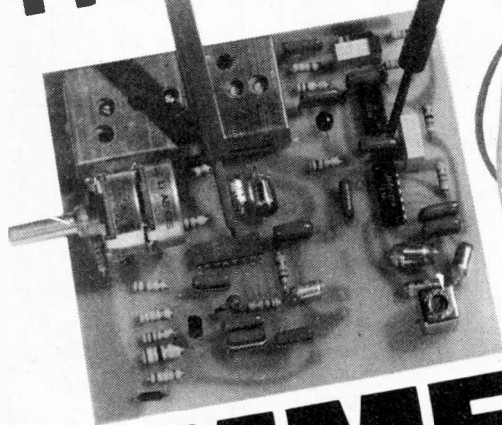

THIS instrument can be used for measuring the resistance of a component without the need to disconnect it from its circuit. This facility can save a lot of time in circuit checking, particularly when working with miniature components on circuit boards. It may also be used in the normal manner for checking unconnected components.

Like a conventional ohmmeter, it can be used for discovering short-circuits and checking continuity—again without removing components from the board.

Utilising a $50\mu\text{A}$ meter, it covers five ranges with full scale deflections of 500Ω , $5k\Omega$, $50k\Omega$, $500k\Omega$ and $5M\Omega$ respectively. Scaling is linear with an accuracy of ± 1 per cent. This means that the meter face does not have to be calibrated.

Other applications include go/no-go checks for semiconductors and capacitors.

HOW IT WORKS

The action of this ohmmeter depends on a special property of the operational amplifier, when connected as shown in Fig. 1. Here, the potential at the inverting input is automatically held at zero, with respect to negative potential. We sometimes say that the inverting input is a "virtual ground".

The non-inverting input (+) is at negative potential simply because it is wired to the negative rail. But the inverting input has a current (I_r) flowing to it. To keep the potential at zero, the amplifier detects this current and almost instantaneously adjusts its own output voltage (E_o) to cause a current (I_x) to flow in its feedback loop. This current is just sufficient to keep the potential of the inverting input at ground, or zero. In other words, the current I_x is

equal in magnitude to I_r , but opposite in sign. It flows away from the inverting input. Mathematically we can say that

$$I_x = -I_r$$

The input, or reference current, comes from a reference cell, of voltage E_r and before reaching the inverting input flows through a reference resistor, R_r , so that

$$I_r = \frac{E_r}{R_r}$$

Similarly for the current in the feedback loop:

$$I_x = \frac{E_o}{R_x}$$

Since I_x is equal but opposite to I_r , we can combine these two equations and get

$$\frac{E_o}{R_x} = -\frac{E_r}{R_r}$$

which by rearrangement of terms gives:

$$R_x = -\frac{R_r}{E_r} \cdot E_o$$

This is the basis of resistance measurements by the ohmmeter. R_x is the unknown resistance which we want to measure. R_r and E_r are known and are constant. For different values of R_x we obtain different values of E_o , and E_o is linearly though inversely related to R_x . If we place a voltmeter between the output of the amplifier and the ground rail we can measure E_o , and use this value to derive the value for R_x . In practice we do not have to do any actual calculation; we simply calibrate the meter scale of the voltmeter to read "Ohms" instead of "Volts".

IN-CIRCUIT OPERATION

Fig. 2 shows R_x as part of a complex network of resistors. Some of the "resistors" in the diagram might be other components with some degree of electrical resistance, such as diodes, transistors, inductances or capacitors. To operate the ohmmeter in these circumstances the distant terminals of all resistors adjacent to R_x must be grounded. In the diagram, points C, D, E and F would need to be grounded.

Terminal A of R_x is at ground potential owing to the nature of the amplifier circuit, as explained above. Points C and D are also grounded. Since both ends of R_c and R_d are at ground potential, no current can flow through these resistors—they might just as well not be there. We can ignore them. Terminal B has a potential E_o provided by the output of the amplifier. Within very wide limits of load this potential is constant. So current flows from ground through R_f and R_x , but without affecting E_o . In this way the meter reads the resistance R_x , and is entirely unaffected by the network around.

The only circumstance in which this circuit will not ignore other resistors is when another resistor is wired in parallel with R_x . Then it is not possible to ground its distant terminal without also grounding either point A or B. The meter will indicate the parallel resistance of R_x and the second resistance, but not the resistance of R_x alone. If the second resistor should be a variable resistor there is no problem, for by grounding the wiper of the resistor we can treat it as two separate resistors.

CIRCUIT DETAILS

The practical circuit is shown in Fig. 3. The current I_r comes from B1, which also powers part of the amplifier IC1. The Zener diode D1 gives a regulated 5.1 volts and the resistors R2 and VR1 connected across D1 act as a potential divider. By adjustment of VR1 a voltage of 0.1 volts can be obtained at the wiper. This is E_r .

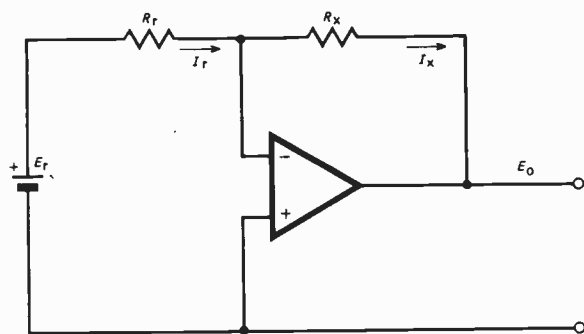


Fig. 1. Basic op. amp. circuit

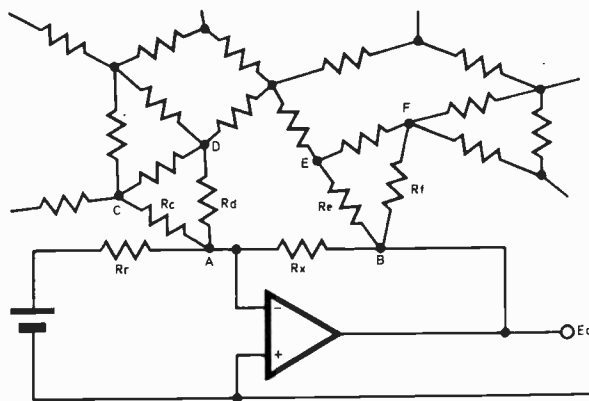


Fig. 2. In-circuit measurement


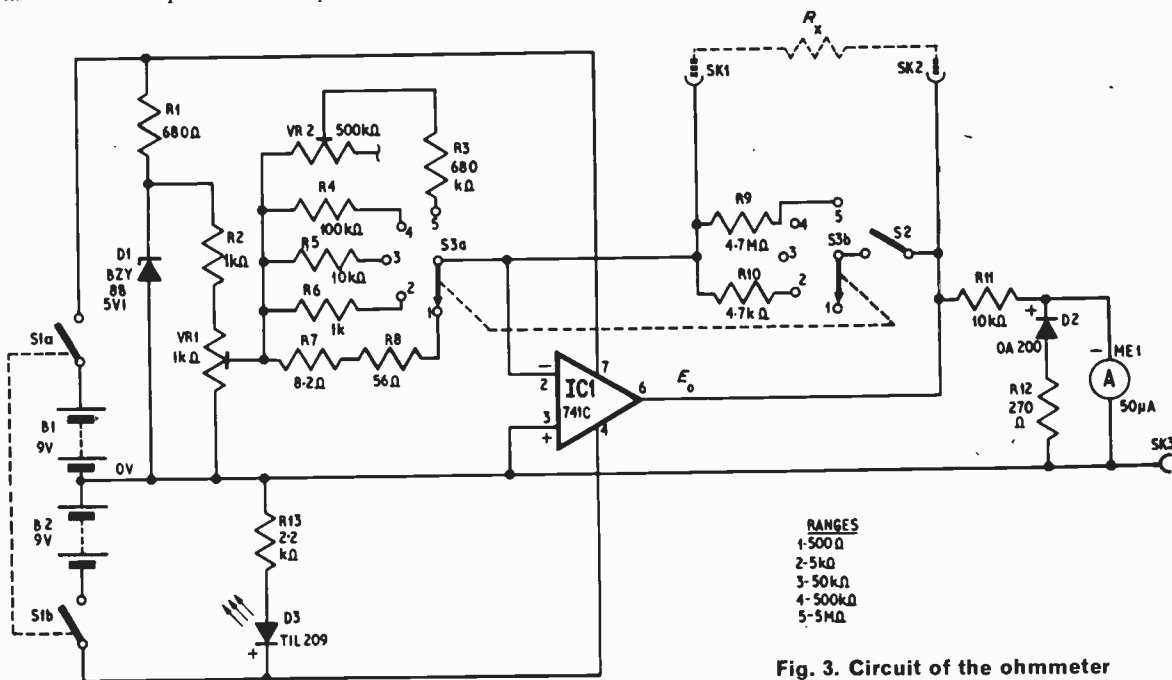


Fig. 3. Circuit of the ohmmeter

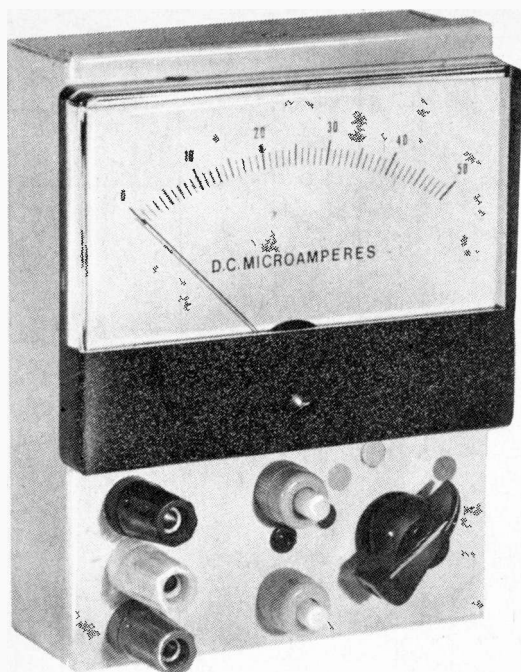

To provide a number of ranges any one of the resistors or resistor combinations R3/VR2, R4, R5, R6, or R7/8 can be switched into circuit, to act as R_r of Fig. 1. The output from the amplifier is fed out to the resistor to be measured through a terminal SK2 and back through SK1 to the inverting input of the amplifier. The voltmeter for output is a microammeter in series with resistor R11. So connected, the meter will give full-scale deflection for $E_o = -0.5$ volts. Inserting these working values of E_r and maximum E_o in the equation, we can calculate that for any range the maximum resistance measurable is:

$$R_{x(\max)} = -\frac{R_r}{0.1} (-0.5) \\ = 5R_r$$

So, when R6 is in circuit, f.s.d. of meter indicates $R_x = 5k\Omega$; similarly, when R5 is in circuit, f.s.d. indicates $50k\Omega$ and with R4, f.s.d. indicates $500k\Omega$. For a f.s.d. of 500Ω one might think that R7 and R8 should total 100Ω , but in practice they total only 64Ω . This is because such a low resistance draws a heavy current from the potential divider, and the potential (E_r) of the wiper falls. A corresponding reduction of R_r from theoretical $100V$ to practical $64V$ restores the balance of the equation, and gives f.s.d. at 500Ω . At the highest range, $5M\Omega$ at f.s.d., the amplifier output does not reach the theoretical level, so the reference current has to be increased by using a reference resistor less than $1M\Omega$. This is provided by R3, with VR2 in series for adjustment to the correct total value.

CONTINUITY CHECKS

On all ranges short-circuiting of SK1 and SK2 puts R_x at zero, so E_o falls to zero. So this instrument can be used for checking continuity. When the terminals are unconnected, R_x is infinite and E_o is infinite too, at least theoretically, though the

characteristics of the amplifier limit it to about -7 volts. Such a high voltage across a meter rated at 0.5 volts would damage the winding so D2 and R12 are wired in parallel to the meter to limit meter current to about $75\mu A$. At low potentials the diode is non-conducting, but with increasing potentials the meter exceeds f.s.d. and the diode begins to conduct in its forward direction so that excess current is shunted through it.

The l.e.d. indicator is important for, unlike an ordinary ohmmeter which uses current only when actually connected to a resistor, this ohmmeter uses current as long as it is switched on. It draws about $7mA$ from B1 and, with the indicator l.e.d. in the B2 circuit, draws about $4.5mA$ from B2. These are low requirements, so small PP3 batteries can be used.

INTERNAL RESISTORS

By closing S2, one of two internal resistors (R9, R10) can be connected across the sockets, if the meter is also switched to range 2 ($5k\Omega$ f.s.d.) or range 5 ($5M\Omega$ f.s.d.). The purpose of these is threefold. They provide a simple check on battery condition and meter adjustment. They are used when checking capacitors or when measuring resistances greater than $5M\Omega$. The calculation for this is given later.

COMPONENTS . . .

Resistors

R1	680 Ω
R2	1k Ω
R3	680k Ω
R4	100k Ω 2%
R5	10k Ω 2%
R6	1k Ω 2%
R7	8.2 Ω
R8	56 Ω
R9	4.7M Ω
R10	4.7k Ω
R11	10k Ω
R12	270 Ω
R13	2.2k Ω
All 5% $\frac{1}{4}$ W carbon unless stated otherwise	

Potentiometers

VR1	1k Ω
VR2	500k Ω
VR3	100 Ω (optional, see text)

Semiconductors

D1	BZY88 Zener 400mW, 5.1V
D2	OA200
D3	TIL209, l.e.d.

Integrated circuit

IC1	741C op. amp.
-----	---------------

Miscellaneous

ME1	Microammeter, 50 μA f.s.d. SEW SD830 or similar
S1	Push-switch or toggle switch, DPST
S2	Push-switch or toggle switch, SPST
S3	Rotary wave-change switch, 2-pole, 6-way
SK1-3	Terminals, yellow, green, black
Veroboard	0.1 in matrix, 24 holes $\times$ 24 strips (half a 5" $\times$ 2 $\frac{1}{4}$ " board)
Veropins	knob for S3, battery connectors.
1% or 2% resistors for calibration (470 Ω , 4.7k Ω , 47k Ω , 470k Ω , 4.7M Ω .)	

OHMMETER WIRING DETAILS


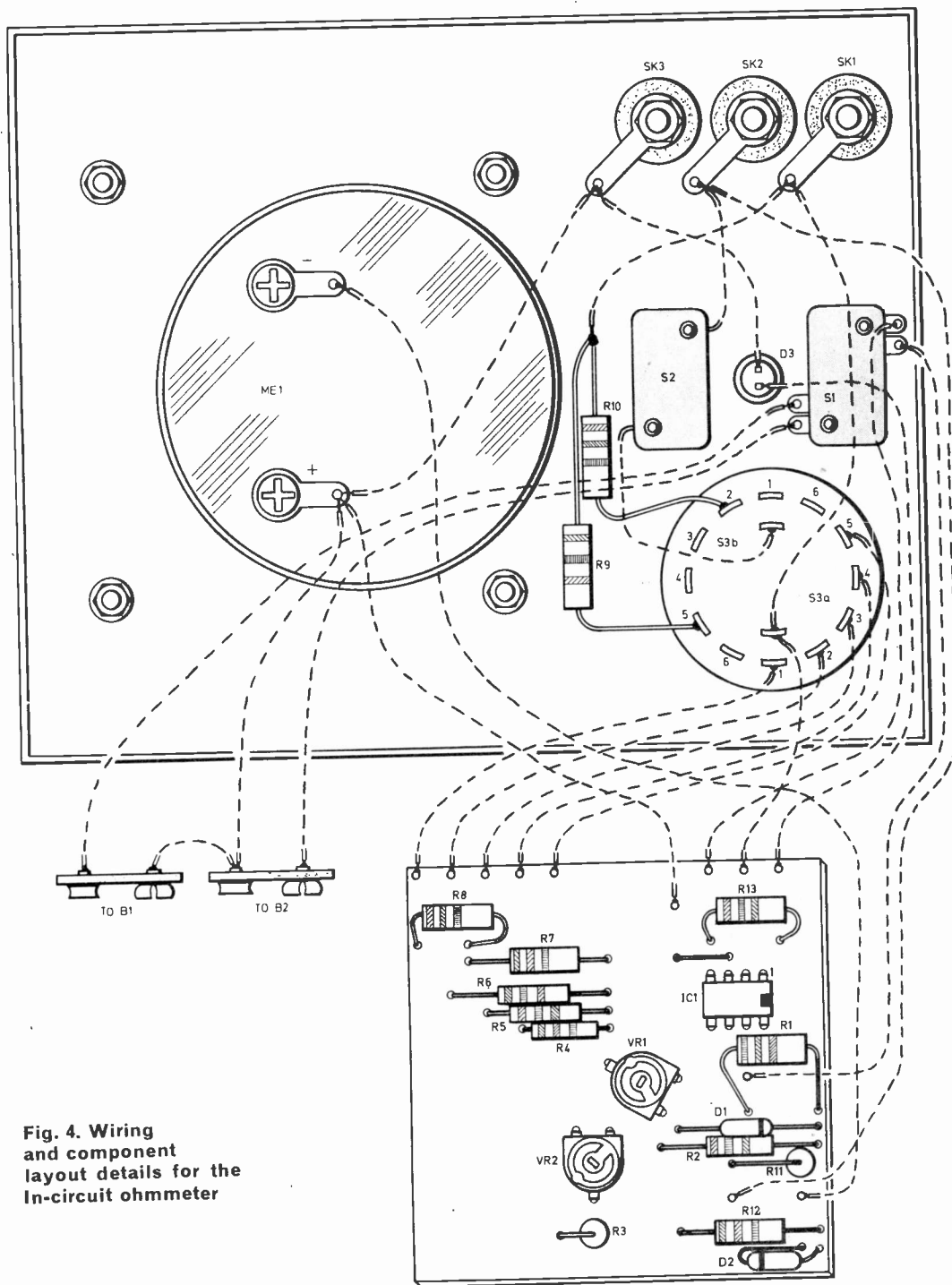


Fig. 4. Wiring and component layout details for the In-circuit ohmmeter

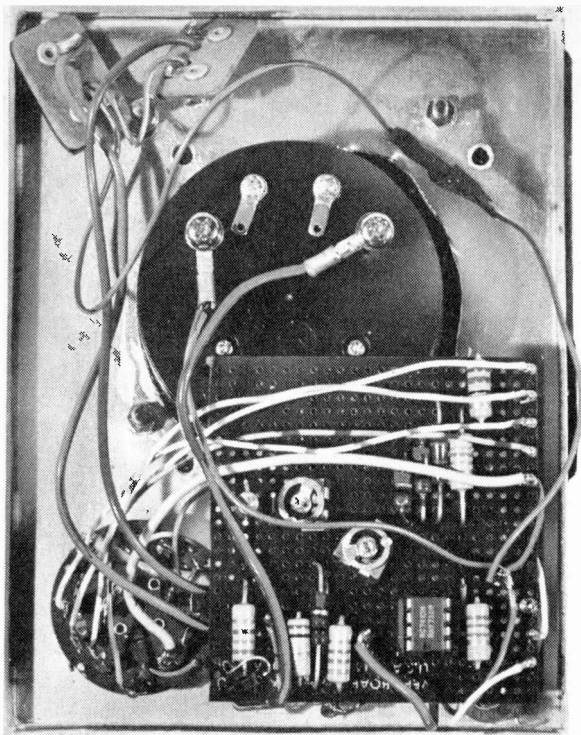

CONSTRUCTION

This presents few problems. Details of layout of circuit board are given in Fig. 4, and are not critical.

The lid of a 10.5cm × 13.5cm × 4cm box was drilled for meter, terminals, switches and l.e.d., and the connections between these were completed before wiring to the circuit board. Fairly long leads were routed to these components, ready for making connections to the Veropins on the circuit board. For convenience the circuit board, with components ready mounted on it, was stuck to the back of the meter case, using contact adhesive; connections to the board then being made.

Apart from marking switch positions for S3, no panel labelling was thought to be necessary. The switch positions were indicated by coloured discs stuck in position on the panel. In order from low to high range these discs were brown, red, orange, yellow and green. This corresponds to the resistor colour code, being the third colour of a resistor corresponding to f.s.d. on each range. Coloured self-adhesive spots sold as colour-slide spots were used for red, yellow and green, and the other discs were punched from coloured card.

SETTING UP

Make sure S2 is open, then connect a 4.7kΩ resistor across terminals SK1 and SK2. If possible, use a 1% or 2% resistor but, if not, try with several 5% resistors. Switch to the 5kΩ range and switch on the batteries. The needle may rest anywhere on the scale, or even swing violently beyond 50. Adjust VR1 until the needle comes to 47 (corresponding to 4.7kΩ on this range). It can now be seen why a precision resistor is not required for R11. Any inaccuracy in R11 is compensated for by adjusting VR1. The value of E_r is only nominally 0.1V and

f.s.d. is only nominally 0.5V, but the ratio between them remains the same (1:5) and the equation still applies.

Now check the 50kΩ and 500kΩ ranges, using 47kΩ and 470kΩ external resistors. These should give correct readings (47 on the scale in each case) without further adjustment of VR1. If not, check wiring—particularly correct connections on the rotary switch, and also that R10 really was out of circuit when you set the 5kΩ range!

Now put a 4.7MΩ resistor across the terminals and switch to the 5MΩ range. Adjust VR2 until the meter reads 47. Finally switch to the 500Ω range, with a 470Ω resistor across the terminals; the needle should read 47. If it reads low, reduce the value of R8; if it reads high, increase R8. Some constructors may prefer to use a 100Ω preset in place of R7 and R8 and adjust this to get the correct reading.

Check the internal resistors by closing S2. The needle should read 47 on the 5kΩ and 5MΩ ranges, with no resistors connected externally to the terminals. Battery condition can also be assessed by this.

USING THE METER

Individual components are connected across SK1 and SK2. Components in circuit are tested by first disconnecting any power supply from the circuit and discharging any capacitors. Then the device under test is connected to SK1 and SK2. The distant terminals of any devices which are joined to the device under test are grounded by connecting them to SK3. A number of leads with crocodile clips will be found useful for this.

When measuring resistances, be sure to have S2 open, or there will be false readings on the 5kΩ and 5MΩ ranges.

The internal resistor of the 5MΩ range can be made use of for measuring resistances higher than 5MΩ. The formula for such resistances in series is:


$$\frac{1}{R} = \frac{1}{R_x} + \frac{1}{4.7}$$

Where R is the resistance measured as shown on the scale, R_x is the unknown external resistor, and all values are expressed in megohms. This equation can be rearranged to give:

$$R_x = \frac{4.7 \times R}{4.7 - R}$$

So if R is measured, R_x can be calculated. If scale reading is 46 (normally equivalent to 4.6MΩ on this range), this would indicate a value of $R_x = (4.7 \times 4.6)/(4.7 - 4.6) = 21.62/0.1 = 216\text{M}\Omega$. So by using the internal resistor one can estimate very high resistances, though with reduced accuracy, for with high resistances the difference between 4.7 and R is only a few scale-divisions, which cannot be estimated to a high percentage accuracy. Still, one is no worse off than when measuring high resistances at the crowded end of the scale of an ordinary ohmmeter.

Diodes and transistors can be tested for shorts and open-circuit—often a sufficient means of confirming that a component is useless. Switch to the 5MΩ range for these tests. Terminal SK1 is positive to SK2, and by connecting a diode first one way round then the other it can soon be found if it passes negligible reverse current (equivalent to high resistance—often in excess of f.s.d.). Similarly an npn transistor will conduct from base to emitter and

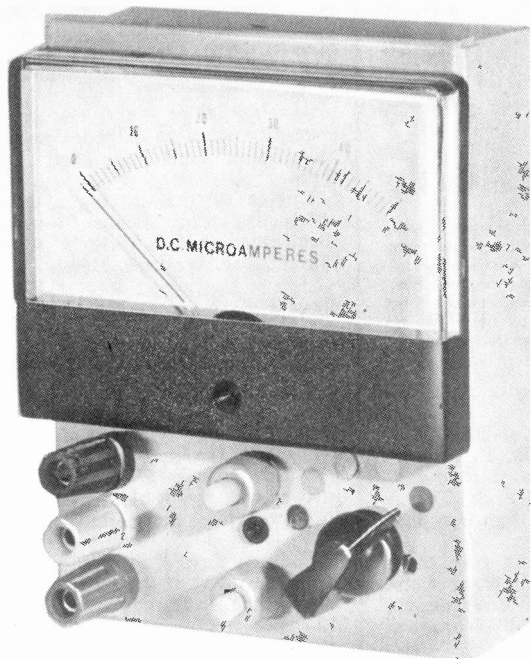

from base to collector, but not in reverse or from collector to emitter. A *pnp* transistor will conduct only from emitter or collector to base. When connected for conduction, the meter will indicate some resistance less than f.s.d. When otherwise connected, a greater resistance (usually greater than f.s.d.) will be shown.

CAPACITORS

To test capacitors, switch to either the $5k\Omega$ range (for capacitors of $1\mu F$ or more) or the $5M\Omega$ range (for capacitors less than $1\mu F$). Close switch S2. Without the capacitor in place, the needle should read 47. When a capacitor is connected across SK1 and SK2, the needle kicks sharply toward zero, then steadily returns to 47. The higher the capacitance the greater the swing, and the longer time taken to return to 47. It is important to discharge the capacitor before testing and re-testing. With electrolytic capacitors observe correct polarity (positive to SK1). Take care not to charge the capacitor unknowingly; if you touch one terminal of the capacitor with one hand, and have the other hand in contact with a lead from the instrument, a current can pass through your body sufficient to charge the capacitor appreciably, and give a false reading—possibly *no* kick, which would be taken to indicate a useless open-circuit capacitor.

It is worth remembering this point too when measuring high resistances. The resistance of the human body from hand to hand is about $1-2M\Omega$. If this is shunted across a high resistor under test a very false reading will be obtained.

Readers may observe that the time taken for the needle to fully return to its starting point (47) is proportional to the capacitance of the capacitor. This could be the basis of a simple and rough way of estimating capacitance. Similar capacitance testing can be done with an ordinary ohmmeter, but usually a barely perceptible kick is obtained below $10,000pF$. With this ohmmeter a useful check can be made on capacitors as low as $30pF$. ★

NEWS BRIEFS

New Loudspeaker

THE application of modern technology to a loudspeaker concept proposed over 30 years ago has resulted in the development of a new loudspeaker construction which promises to overcome many of the mechanical drawbacks associated with normal cone-construction driver units.

The innovator, Mr Josef K. Manger, a German radio retailer, has used modern materials to produce a so-called resistive diaphragm driver which was demonstrated to the I.E.E. and the Technical Press last month using pre-production models and normal disc records.

Whilst all such demonstrations are subjective, this one indicated that the new units will bear close watching in the near future since, to the writer, they seemed to come closer to representing the actual sound experienced when standing in, for example, an orchestra, than anything heard so far.

This is perhaps an exaggerated claim but certainly the units are capable of reproducing a square wave as such which (again to the writer's limited knowledge) no other equipments seem able to do.

Currently the units are to be made in Germany in the near future on a commercial scale and it is understood that Mr Manger is looking for a possible British manufacturer to make here under licence.

World's Best Timekeeper Goes On Show

WHAT is claimed to be the world's most accurate wristwatch will soon be on display at the Science Museum in London. The Omega "Marine Chronometer" has a guaranteed accuracy of within one second per month which is achieved by using a quartz crystal vibrating at $2359296Hz$ as the reference.

A special feature of this watch is that the hour and second hands can be set independently without affecting the accurate timekeeping.

Before each watch is put on the market it is sent to an independent laboratory where a certificate is awarded confirming the watch's performance.

Complete with stainless steel case and bracelet the Marine Chronometer sells for £680.

New Year Award For Radar Executive

THE New Year Honours List included the name of Dr K. Milne who has been awarded the OBE for outstanding work as Research Executive with Plessey Radar.

A recognised authority in microwave antenna research and design, Dr Milne has been responsible for many major projects including advanced radar, satellite communications and navaid systems. He is an active member of the Electronics Research Council and of international committees, contributing to the recognition of Britain's high status in microwave technology.

Ipswich News

A LECTURE entitled "Sound Synthesis for the Amateur" will be given by Douglas Shaw at The School of Engineering Technology, Rope Walk, Ipswich, on February 26 at 7 p.m.

This lecture is part of a Hi Fi course, currently running at the Civic College, but P.E. readers in the Ipswich area who have an interest in sound synthesis are cordially invited to attend by the course tutor, P. B. Broadribb Esq.

P.E. ORION

Good news for P.E. Orion amplifier builders, the manufacturers of the cabinet used in the prototype unit, H.M. Electronics Ltd., have recently informed us that they hope to be able to produce a pre-drilled cabinet with a self-adhesive anodised aluminium front panel as an optional extra.

H.M. Electronics have also informed us that we have quoted the wrong type number for the cabinet in our components list. The correct type number for the case is the GB1 and not GB3 as stated in the article.

Full details and a price list of their complete range of equipment cabinets can be obtained from **H.M. Electronics Ltd., 275a Fulwood Road, Sheffield, S10 3DB.**

We have been informed that some readers have experienced difficulty in obtaining the mains transformer. This transformer, type SL8, can be purchased from **Gardners Transformers Ltd., Christchurch, Hants., BH23 3PN,** for £10.23 including postage and VAT.

Alternatively, the transformer for the P.W. Texan amplifier can be used in the P.E. Orion. This has a lower current rating and will give a slightly reduced output power, but it should be entirely satisfactory for speech and music. This transformer is available from **Henry's Radio Ltd., 303 Edgware Road, London, W2 1BN,** for £5.94 including postage and VAT.

LOUDSPEAKER KIT

Readers who have completed or nearing completion of the P.E. Orion, and are shopping around for a reasonable speaker system that they can build for themselves, may find the range of SEAS hi-fi loudspeaker kit now being marketed by Macel Electronics worth investigating.

Designed for sealed enclosures, there are five kits available, capable of handling outputs ranging from 20W to 70W. The frequency response of the units ranges from 25 to 20,000Hz, according to speakers used and size of enclosure. Each kit includes a tweeter, main driver(s), crossover unit and connecting wire with a din plug. The speaker impedance is 4 to 8 ohms.

A feature of the systems is that each kit contains a recommended enclosure design with full measurements and constructional guidance notes.

Further information and full details of their complete range of SEAS hi-fi loudspeaker kits can be obtained from **Macel Electronics Ltd., P.O. Box 64, 14 High Street, Ipswich, Suffolk.**

DIGITAL LEAF

Suitable inexpensive valves for use with the "Digital Leaf" greenhouse automatic moisture system, described in our January issue, are

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

available from Concordia Automation Components.

Several types are available with $\frac{1}{4}$ in, $\frac{1}{2}$ in, $\frac{3}{4}$ in and 1in B.S.P. connections for mains or low voltage supplies at prices from £6 each. This is approximately half the figure quoted in the article.

Further information on these valves can be obtained from **Concordia Automation Components Ltd., 6 Central Park, Worcester Park, Surrey, KT4 8HZ.**

NEW LITERATURE

Recently formed to market p.c.b. hardware, heat sinks and modules manufactured by Assmann KG, Germany, Dieter Assmann Electronics announce the availability of a new catalogue.

The catalogue contains 50 pages of detailed information covering the whole of the Assmann product line. Dual-in-line sockets, for example, can be supplied with from 8 to 40 pins, including the popular 14- and 16-pin units. Sockets and mounting pads for transistors are also available in most of the popular configurations.

The range additionally includes p.c.b. connectors, and bread boards

SEAS hi-fi loudspeaker kit from Macel Electronics



for experimental and development work. Details of jumper links, terminal pins, u-pins, eyelets and insulated terminals form a complete section in the catalogue. A very broad range of heatsinks is also covered, including extruded and cast aluminium, and staggered finger types.

Copies of the catalogue can be obtained from **Dieter Assmann Electronics Ltd., Victoria Works, Water Lane, Watford, Herts.**

SEMICONDUCTORS


High Speed 741

In many areas of application engineers need a higher slew rate from their operational amplifiers than can be obtained from the everyday 741 chip.

Motorola have provided the answer to this problem with a plug-in alternative designated MC1741-SCPI.

The new device, available ex-stock from Jermyn at a 1-off price of £0.92 each, boasts a slew rate of 10V per microsecond, suiting it to digital-to-analogue converters and amplifiers where bandwidth from d.c. to over 100kHz is important.

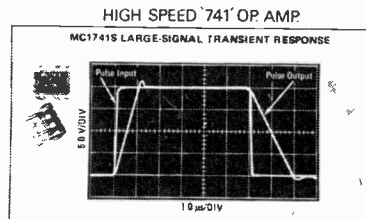Further details available from **Jermyn Industries, Vestry Trading Estate, Sevenoaks, Kent.**



Audio Transistors

Five new complementary pairs of silicon epi-base, epi-collector power transistors designed for a complete voltage range have just been announced by SGS/ATES.

The first pair, BD433 and BD434, have been developed for in-car entertainment applications with power requirements up to 12W. The second and third pairs BD435 and BD436, and BD437 and BD438, are particularly suited to hi-fi audio amplifiers up to the 15/20W range.

All types in the range are suitable for industrial applications such as power drivers, switching circuits and current regulators up to 4A and, of course, for automotive applications such as flashing lights, lamp dimmers and direction indicators.

All the devices are rated at 36W P_{tot} , 4A I_c and an f_t of 3MHz, whilst the V_{ceo} values for pairs are as follows: BD433/34, 22V; BD435/36, 32V; BD437/38, 45V; BD439/40, 60V and BD441/42, 80V.

Further details available from **SGS/ATES (U.K.) Ltd., Planar House, Walton Street, Aylesbury, Bucks.**

NEXT MONTH...




THE PE COMPENSATED PHOTO TIMER

The P.E. compensated photo timer not only provides simple selection of time interval from 0.1s up to 120s with controls designed specifically to suit darkroom conditions, but additionally provides for exposure compensation of mains voltage variation effects on enlarger lamp light output.



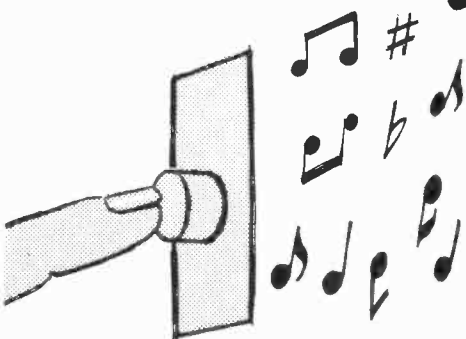STARTLE YOUR FRIENDS WITH THIS MUSICAL DOORBELL



Capable of playing a tune of welcome (or rejection!) dependent on the choice of programme you put in. Integrated circuitry and state-of-the-art logic make for simplicity of construction.

STARTING NEXT MONTH...

INTRODUCTION TO TRANSDUCERS

An important and informative series on Transducers, their operation, types, uses and technical features. Make certain not to miss any of this in-depth study of these important tools in the art of measurement.

TEMPERATURE
HEAT LIGHT WEIGHT
DISTANCE SOUND
FREQUENCY DEPTH

PRACTICAL

ELECTRONICS

APRIL 1975 ISSUE ON SALE MARCH 14, 1975 — PRICE 30p

ELECTRONIC

THERMOSTAT

By R.A. PENFOLD

IN photographic work it is often necessary to keep solutions at a constant temperature during the printing process. The situation is especially critical when it comes to colour printing, where it may be necessary to maintain the temperature of the solutions to within a fraction of a degree.

The normal method of achieving this is to place the dishes containing the photographic chemicals on a thermostatically controlled dish warmer. However, many devices of this type use mechanical thermostats which are far too insensitive for accurate temperature control, and can often only keep the solutions to within a couple of degrees of the required temperature.

PRECISE CONTROL

The device which forms the subject of this article was built to give a much more precise control over a system such as that just described, and has proved to be very successful in use. Exactly how accurately it will maintain a given temperature will depend to a certain extent on the apparatus with which it is employed, and also on the efficiency of the sensor. It should however, be able to maintain a temperature to an accuracy of about plus or minus 0.2 degrees.

It can of course be used for any similar purpose where it is necessary to maintain a liquid at a constant temperature. The range covered by the unit is from slightly below 50°F to a little more than 100°F.

Circuits of this type can be rather complicated, but in this design the utilisation of an i.c. operational amplifier enables a very simple and straightforward circuit to be used.

THE CIRCUIT

A complete circuit diagram of the electronic thermostat is shown in Fig. 1. The unit is designed around the 741C i.c., which is used here as a differential amplifier.

COMPONENTS . . .

Resistors

- R1, R2 5.6Ω (2 off)
- R3 33kΩ
- R4 27kΩ
- R5 10kΩ
- R6 4.7kΩ
- R7 430Ω
- R8 220kΩ
- All ½W 10% carbon

Potentiometer

- VR1 10kΩ linear slider

Capacitors

- C1, C2 220μF 16V elect. (2 off)

Semiconductors

- TR1 BC109
- D1-D4 1N4001 (4 off)
- D5, D6 BZY88 C10 10V 400mW Zener (2 off)
- D7 OA200 or any general purpose silicon diode
- IC1 741C 8-pin d.i.l.

Thermistor

- TH1 VA1066S

Miscellaneous


- SK1 Surface mounting mains socket
- RLA Miniature 12V relay (Omron 1051, 465 Ω Home Radio)
- T1 Mains primary, 9-0-9V 80mA secondary (Osmor MT9, Home Radio)
- S1 Single pole on/off
- FS1 500mA with holder
- 0.1in matrix Veroboard 35 x 15 holes
- 6in x 4in x 2½in aluminium chassis with base plate
- Screened cable, hardware for sensor

The gain of the i.c. is extremely high, and the voltage difference required at the inputs to cause the output to swing fully one way or the other is only a fraction of a millivolt. This tends to give the circuit built-in triggering, as there is such a restricted range of voltages which will give an intermediate state at the output.

At the inputs to the i.c. there is a bridge circuit. One arm of this is formed by R3, VR1, and R4, and the other by R5, R6, TH1. The supply is connected to the input of the bridge.

The output from IC1 is coupled via R8 to TR1, which has the relay in its collector circuit. The contacts of the relay are taken to a mains socket, into which the dish heater is plugged. When the output of IC1 is high (+20V) the relay is energised. R7 is required in order to reduce the supply to a more suitable level to power the relay. Diode D7 is the normal protective diode. Even when the output of the i.c. is low there is an output potential of about two volts. R8 is therefore required to prevent the relay from being permanently held on.

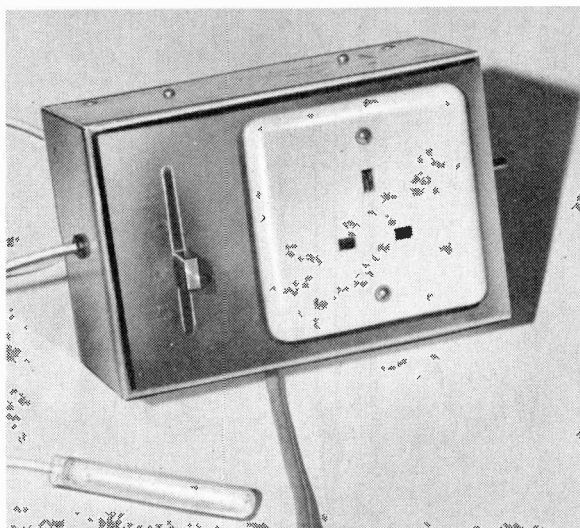
In practice VR1 is marked with a scale calibrated in degrees. If, for example, this is set to 100°F, at the start the liquid will probably be at about room temperature, and considerably less than 100°F. The voltage at the non-inverting input will be high in comparison to that set at the other





input by VR1. The output of IC1 will thus be high and the heater will be turned on. As the liquid warms up the voltage at the non-inverting input will decrease, until eventually when the liquid reaches 100°F, this voltage being equal to that at the other input, will cause the output of IC1 to go low, and the heater to be turned off.

The liquid will now of course begin to cool, but will not be allowed to cool much, as this cooling will be sensed by the thermistor, which will unbalance the input voltages resulting in the heater being turned on again. The circuit will continue to oscillate in this way, thus stabilising the temperature of the liquid.

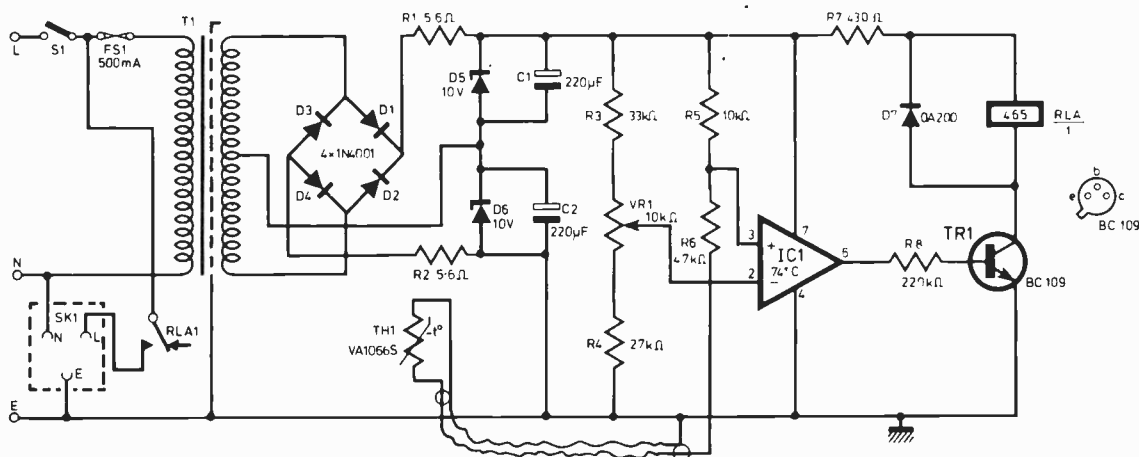A simple stabilised mains power supply is used. This consists of two full wave supplies, each providing 10V, connected in series to give 20V, which is



237

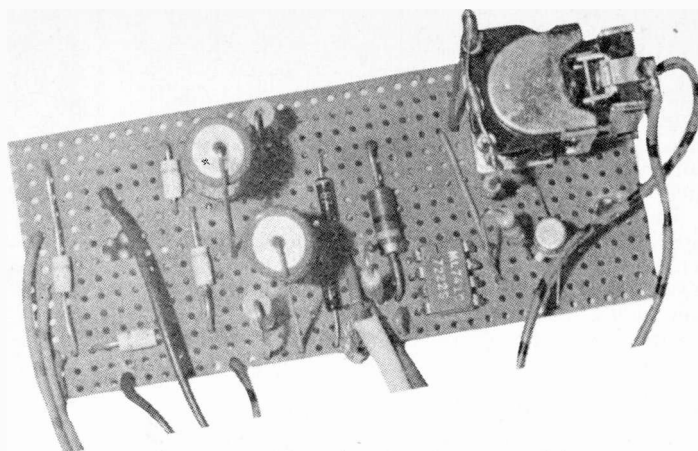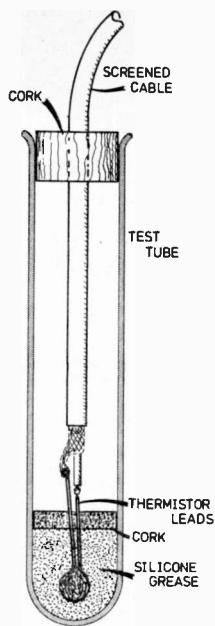

Component board of the Electronic Thermostat

Fig. 2. Construction of the sensor using a small test tube and some silicone grease

adequate for the 741C. D5, and D6 in conjunction with R1 and R2, and the relatively high secondary impedance of T1 give the stabilisation. C1 and C2 provide the necessary smoothing.

SENSOR CONSTRUCTION

The thermistor must be contained in a watertight compartment, and it must also be in good thermal contact with the outer surface of the container. Fig. 2 illustrates the construction of the sensor used with the prototype. The outer casing is a small glass test tube. The thermistor is mounted at the bottom of the tube, and is immersed in silicone grease to ensure a good thermal contact with the test tube.

The small slice of cork above this helps to keep the thermistor firmly in place, and also helps to prevent its leads from shorting together. Also, the silicone grease is rather thick, and needs to be pushed to the bottom of the tube. The slice of cork is very good for this task. Thin microphone cable is used to connect the sensor to the main body of the instrument.

CASE CONSTRUCTION

A suitable case for the unit consists of a 6in × 4in × 2½in aluminium chassis fitted with a base plate. Four rubber cabinet feet are bolted to the base. The general layout of the case can be seen from the photographs. The mains socket is mounted on top of the case on the right hand side. This mounted by two 4BA ½in bolts.

A large part of the socket fits behind the panel, and a large cut out must be made for this to fit through. This is easily made by drilling a string of ¼in holes around the perimeter of the cut out, and then using a ¼in "Abrafile" to join the holes.

The slider potentiometer is mounted on the left of the mains socket, and it is glued into position. The cut out for this can be made in a similar way as that for the mains socket. A nail file can be used to smooth up the edges of the slot.

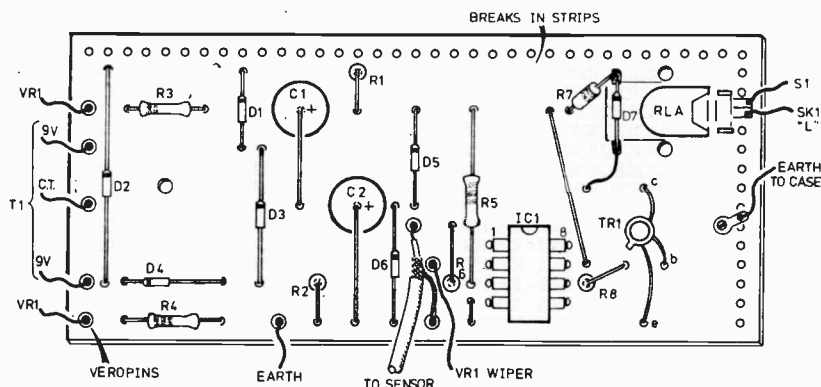


Fig. 3. Layout of components on the Veroboard. The diode D7 is connected directly across the coil contacts of the relay

The on/off switch is mounted on the centre of the right hand side panel. The lead from the sensor enters the case opposite this on the left hand side, and the mains lead enters on the lower edge of the case. The holes for both these leads must be fitted with rubber or p.v.c. grommets.

COMPONENT PANEL

Most of the components, including those of the p.s.u. (except T1), are mounted on a 0.1in matrix Veroboard panel. Fig. 3 shows the layout of this.

The mounting holes for the relay are $\frac{1}{4}$ in diameter. The mounting screws and washers are supplied with the relay. There are two mounting holes for the board, and these are for 6BA clearance. The outer braiding on the lead from the sensor is too large in diameter to go through the holes in the Veroboard, and is therefore taken to a pin.

When completed, the board is mounted on the upper side of the case by two 6BA $\frac{1}{4}$ in bolts. Two stand off insulators are required to hold the board a little way clear of the case.

ADDITIONAL WIRING

T1 is glued to the inside of the case opposite the Veroboard panel. Unfortunately the lead out wires of this are too short to reach the Veroboard panel. The leads from T1 are taken to a miniature three way connector block, and three insulated wires are taken from this to the component panel. The mains input is also taken to one side of a three-way connector block, and from here the connections are made to the various parts of the circuit.

Only the two connections to the relay contacts at the top, and middle of the relay are used, the lower one being ignored. Up to five amps at 250V can be handled by the specified relay.

It is essential that the negative supply is earthed, as if this is not done the relay will not switch over cleanly. For reasons of safety the case must also be earthed. A solder tag on one of the mounting bolts of the component panel is used to make the connection to the case. The two connector blocks can be bolted to the case, but on the prototype these were left supported only by the leads connected to them.

CALIBRATION

A scale is marked along the run of VR1. The various points along this are easily found. If for example it is required to find the setting which corresponds to 100°F, the sensor is placed in some water which has been heated to precisely this temperature. Once the sensor has had time to adjust to the temperature of the water, the slider of VR1 is brought as far down the scale as possible without the relay turning off. This point is then marked 100°F.

The scale is rather broad, as a fairly wide range of temperatures is covered. If absolute accuracy is required, it is advisable to initially use a thermometer to monitor the temperature of the liquid, and then if necessary, small adjustments can be made to the setting of VR1 to bring the temperature to exactly that required. ★

21st London International BOAT SHOW 75

ONCE again the annual International Boat Show has brought forward a variety of new and interesting developments in electronics associated with the sea. One of the most important and significant innovations on display this year was the Lucas Marine safety buoy. The buoy is automatically released from a sinking vessel and remains anchored to the vessel at depths up to 3,000ft. It sends out a distress signal at 121.5 and 243MHz, emits a high intensity flashing light, releases a 50ft floating line with light to act as a rallying point for survivors and releases an automatically inflating four to six man life-raft. Other facilities are also available, such as marker dye and calming oil.

The electronics are powered by lithium batteries which have a recommended replacement life of four years. The transmitted distress signal has been satisfactorily received at a range of 180 miles.

Another new device to aid safety at sea is the G.H.T. Gas Safety Unit. Using solid state gas sensors and electronic control, this unit not only senses the presence of dangerous gases, but turns off the gas at source. The unit is fitted with voltage failure protection and has to be reset once triggered or if the supply fails.

One of the most popular ranges of instruments among the racing yachtsmen, Brookes and Gatehouse, has this year been increased and modified. A new unit, the Halycon—they must run out of names soon—is a repeating compass with dead reckoning indicator providing information on position in two co-ordinates. This year B. and G. have introduced a quartz crystal controlled chronometer and l.e.d. internal lighting for their repeater instruments.

Baron Instruments have introduced a Square Mk. 2 range—re-designed housings and dials. Two versions of the log are available (0-15 knots and 0-35 knots) and three versions of the depth sounder 0-30, 0-60ft/fathoms and 0-10/100 metres.


Decca were showing the 36 mile 110 Radar for the first time; this equipment employs a 4ft scanner and therefore is not likely to be seen on anything but the largest private yachts. This set is basically an improved version of the 101 Radar that has proved itself over the years.

Space Age Electronics were displaying a doppler speedometer with audible output for dingy tuning—the transducer is inserted in the centre board case and an increase in speed increases the frequency of the output. However, at £40 it may not be very popular.

Also from Space Age a portable echo sounder for fishermen; using l.e.d. output it is claimed that fish can be easily recognised. Can be used in a boat or from the river bank.

Finally, two points concerning EMI. The first is rather sad—The Electrascan radar will soon be discontinued, presumably competition from others, the servicing requirements and the general financial situation have all taken their toll. The second item—looking ahead to next year's Boat Show—the CCTV Division of EMI Sound and Vision Equipment Limited, is providing additional security in the form of an automatic closed circuit TV alarm system.

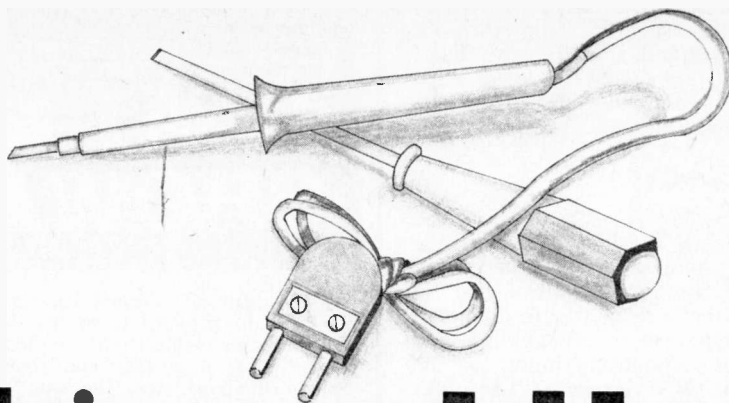The system is in no way intended to inhibit normal movement through the entrances and exits, but it is intended to assist the existing security services to prevent the unauthorised entrances of people into the show halls.



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

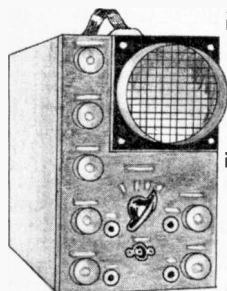

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


2

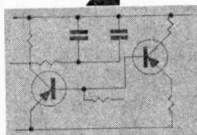

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.


3

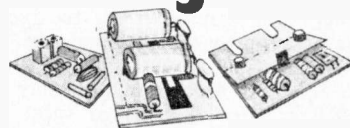

Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

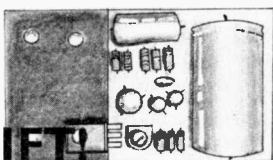

FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Brochure without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EL35

P.O. Box 156, Jersey, Channel Islands.

NAME.....

ADDRESS.....

(Block caps please)

WAA



THE time has come to introduce a few practical projects in the production of taped music. In the coming months it is hoped to bring out some hints on the creative use of the P.E. Minisonic Synthesiser, but for the moment it seems advisable to get into practice with tape manipulation, to perform a short composition and settle on the kind of equipment required to get the best out of the Minisonic—or any other sound source destined to be frozen on tape.

Firstly the equipment. It is generally advisable to have two tape machines available, although both need not necessarily be sophisticated stereo (or quadrasonic) units. Preferably both should be reel-to-reel machines (for ease of editing) though one can get along quite well with one stereo reel-to-reel machine and a cassette deck. In the interest of increased versatility a choice of tape speeds should be available (19, 9.5, and 4.75 cm/s being normal on domestic equipment).

If one or both machines are stereo with track-to-track dubbing (so-called multi-play) one can extend the number of superimposed recordings without unduly affecting the final quality. Personally, however, I tend to ignore this facility and use two stereo machines through a mixer to produce a stereo result.

Basic set-up

The mixer unit need not be an elaborate affair. A very workable battery-powered stereo unit can be built around a couple of 741 op.amps with as many input and output connections as required. For the coming projects, including this month's, I recommend at least eight inputs, individually switchable from left to right channels, and three-plus-three outputs.

Any stereo amplifier will serve in the set-up since it is to be used

only for monitoring purposes; one of the stereo outputs from the mixer will be permanently connected to its Auxiliary, Tape, Radio or Phono socket.

The final piece of equipment for this month's project is a short-wave radio receiver, see Fig. 1.

Method of composing

As a student some years ago I felt the urge to attempt some electronic music, spurred on by the apparent simplicity of the sound material in Stockhausen's "Study II". Without the mass of equipment necessary I had to rack my brains to find an alternative sound source. The problem was partially solved by a domestic four-waveband a.m. radio set. After hours of patient (and enjoyable) knob-twiddling I managed to find a selection of "electronic" sounds which promised to be of use. Armed with a splicing block, razor blade, splicing and leader tape and a four-speed mono tape recorder I spent a fortnight's spare time producing a two-minute piece.

The project outlined below works along these lines, but since stereo is pretty commonplace nowadays I have decided to compose a two-channel work. Those who may only have access to mono machines could still, with a bit of juggling, produce a mono version of it.

PELORIA

I have called my piece "Peloria"* which is laid out in time, the numbers 1 to 20 across the top and bottom of the score referring to equal time intervals chosen by the performer, see Fig. 2.

Each channel has three imprecisely laid out pitch bands—high, medium and low. The dynamic levels are similarly imprecise: *pp*=very soft, *p*=soft, *mf*=moderate level, *f*=loud, *ff*=very loud. The short-wave sound material, chosen by the performer, is shown largely in rectangular blocks, variously shaded; blocks containing horizontal lines indicate a rich or busy sound with no discernible melodic or rhythmic consistency;

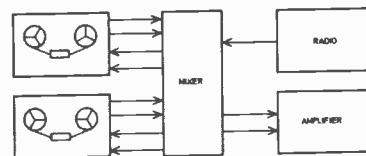


Fig. 1. Simple tape effects set-up

similar vertical narrow bands represent a very short event.

The areas shaded with dots represent fleeting pitches which may be discernibly rhythmic or melodic yet move at great speed. The blocks shaded with short curved lines represent melodic and rhythmic patterns of a moderate-to-quick speed. Horizontal broken lines signify a decrease in level towards silence if placed after continuous lines, an increase if they appear before.

The sound material for "Peloria" is available, from my experience, all year round. I suggest that all the sounds required for the piece be recorded at some length and at all speeds available on your tape machine; this gives sufficient length to cut out unwanted blips and to ensure an increased variety of pitch bands. Decide on the length of your time interval—you may do this roughly with the seconds hand of a watch or more precisely by measured lengths of tape. Those events which require an increase or decrease in level should be re-recorded using the level controls on the mixer.

From the material you now have snip out the measured lengths for channel one, not forgetting the periods of silence. Record the whole of the sequence on to the left-hand channel of your stereo machine. Now edit the tape for channel two, placing leader tape between events; this will allow you to pause during the gaps and come in on time for the final transfer to the right-hand channel of your stereo machine. Absolutely exact synchronisation is not necessary in this piece.

*Peloria: The regularity in a normally irregular flower (Chamber's Twentieth Century Dictionary).

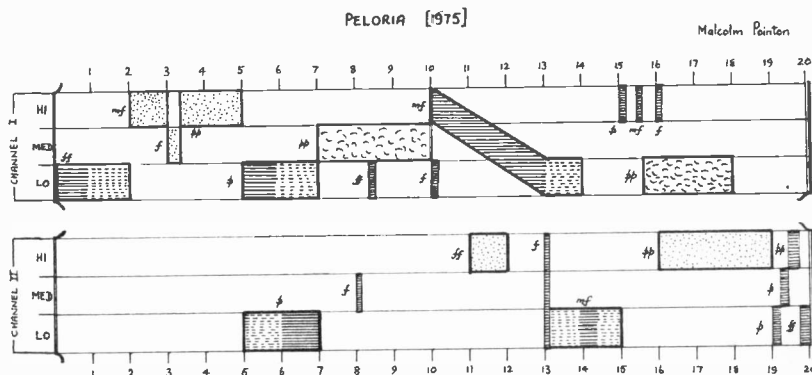


Fig. 2. Mr. Pointon's method of composing electronic music for his piece called "Peloria"

THE Geiger counter described in this article is small enough to be slipped into the pocket and taken out into the country to look for radioactive minerals. Quarries and old mine workings are good hunting grounds, particularly if geologically old rocks are being uncovered. Unfortunately, your search is not likely to be very rewarding in this country.

Nevertheless, the instrument will show that we are being exposed continually to a natural background radiation made up of cosmic rays and the emissions from radioactive materials in the ground and air around us and over which we have very little control. The instrument can also be used to locate sources of radioactivity should these be mislaid in the workshop and laboratory.

The instrument is quite sensitive, it will count by producing a click in an earpiece, a single beta particle (an electron) whose mass is about one million billionth of a kilogram (10^{-30} kg) and which could be moving at about 800 million kilometres per hour!



GEIGER COUNTER

By M. PLANT M.Sc.

The accompanying photographs show one form of the completed Geiger counter with the electronics housed in a plastics slide box. In use the box is held close to the ear, the thumb holding the push-button switch down.

THE GEIGER TUBE

The Geiger counter tube is the part which is sensitive to the atomic radiations which are emitted from radioactive sources and which make up cosmic rays. The type of tube shown in the photographs is fairly common and consists of a central anode surrounded by the cathode. Photos show the kind of tube which has an end window to allow it to respond to alpha particles (the nuclei of helium atoms) and to low energy beta particles, both of which are most easily absorbed by the material through which they pass. The less sensitive tube shown in the model responds to the very penetrating radiation of gamma rays and high energy beta particles.

Geiger tubes (strictly called Geiger-Muller or GM tubes) are available on the government surplus market for a few pounds and are often advertised in the pages of this journal or are available from suppliers of Mullard equipment.

The tube selected should have an operating voltage of about 400V. An important feature of the counts per minute versus voltage across the anode-cathode of a geiger tube is the so-called plateau of operating voltage which is shown in Fig. 1. The sensitivity of the tube increases gradually over this



plateau and it is important to operate the tube within this range of voltage; the midpoint of the plateau is usually chosen and the present instrument can be adjusted to operate the tube at this voltage. Geiger-Muller tubes have commonly a two-pin base requiring a special holder, but some have an octal base although just two of these pins actually make connection to the tube.

THE CIRCUIT

Fig. 2 shows the circuit which consists essentially of three parts, an inverter or d.c.-to-d.c. converter, a voltage doubler, and an amplifier. The inverter and voltage doubler enable a 9V battery to provide up to 500V to operate the GM tube, and the amplifier is required to amplify the voltage pulses obtained across a resistor in series with the tube when the tube responds to the effect of a particle passing through it.

THE INVERTER

The inverter is a simple resistance-coupled oscillator which gives about 250V across the secondary of the 9-0-9V/250V transformer at a frequency of about 40Hz.

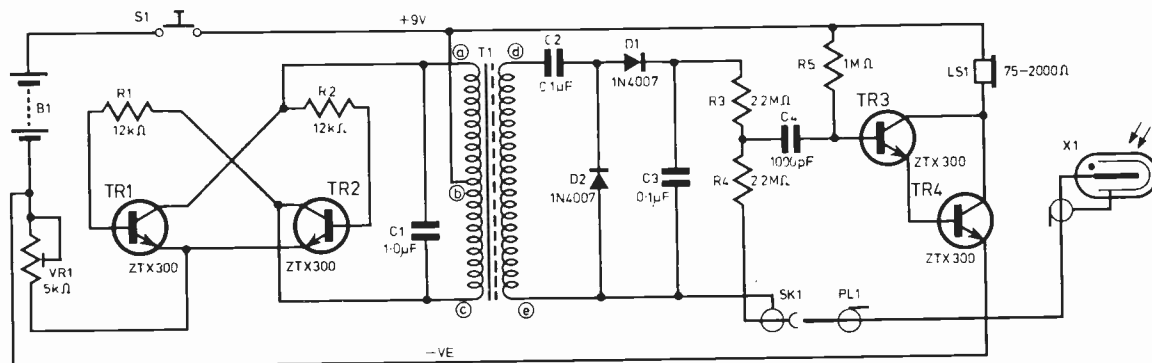


Fig. 2. Circuit diagram of the power supply, GM tube and amplifier

TR1 starts to conduct when the circuit is switched on and current increases in the associated half of the primary winding of the transformer, induces a voltage in the other primary half which rapidly drives TR1 into saturation via the base coupling resistor R1 and thus biases TR2 off.

Flux increases in the core of the transformer until saturation is reached when the positive feedback provided by the induced primary voltage falls to zero. TR1 is returned to the off state and this ends the first half cycle of the period of oscillation. The collapsing flux in the transformer core induces a voltage in the primary winding associated with TR2 to drive it on, so initiating a second similar half-cycle.

Capacitor C1 across the collectors of the transistors eliminates the possibility of high frequency oscillation and makes for reliable starting of the inverter. The actual primary voltage being switched by the two halves of the primary winding of the transformer can be varied by means of the variable resistor VR1 in series with the 9V battery so that the voltage available from the voltage doubler can be varied to suit the characteristics of the tube used.

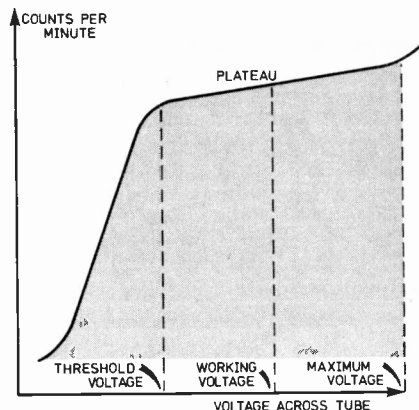


Fig. 1. The characteristic curve of a GM tube

Up to 250V a.c. is available across the secondary winding of the transformer and this is doubled and rectified by the diodes D1 and D2 and the capacitors C2 and C3 to provide about 500 V d.c.

The output from the supply is applied across the GM tube via R3 and R4. The passage of a radioactive particle through the gas filling the tube causes some of the gas to be ionised. Under the high voltage between the anode and cathode, a rapid avalanche of ionisation occurs and ions are collected by the electrodes resulting in a very small current through the external resistors R3 and R4. This pulse of ionisation is short-lived and the tube is quickly ready to respond to another ionising particle passing through it. The voltage change across the external resistors is coupled to a two-transistor amplifier by the coupling capacitor C4 so that a loud click is heard in the earpiece.

ASSEMBLY

A piece of Veroboard was selected for assembling the circuit, the precise dimensions depending on the physical size of the components to hand and the case used. In the present instance the case used in the prototype was a Kodak slide box measuring 108 × 32 × 52mm and the Veroboard measured 46 × 54mm.


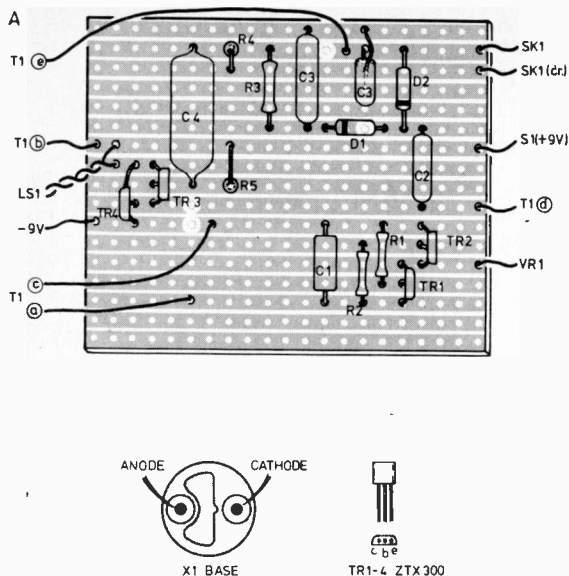


Fig. 3. Component layout and Veroboard cutting details for the counter

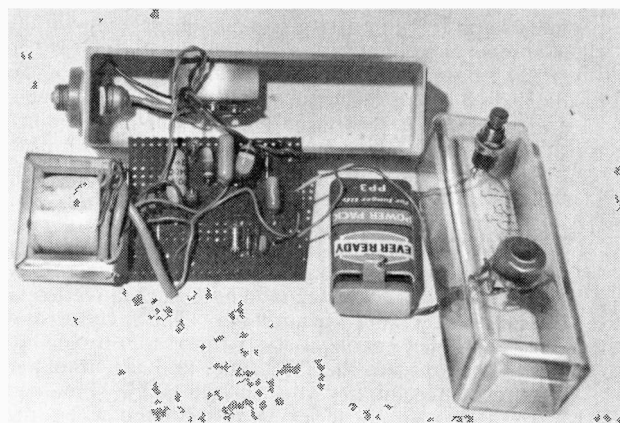

Completed Geiger Counter ready for installing in a photographic slide case

Fig. 3 shows the component layout of the prototype circuit in which C3 is made up of two 0.22 μ F, 250V capacitors connected in series to give, effectively, a 0.1 μ F, 500V capacitor. However, a suitable single capacitor may be obtained for this circuit, although physical size may preclude use. The main precaution to be taken is to ensure that the high voltage cannot be inadvertently connected to the low voltage side of the circuit, otherwise damage to the transistors and C1 may result.

COMPONENTS . . .

Resistors

R1, R2 12k Ω , 2 off
R3, R4 2.2M Ω , 2 off
R5 1M Ω
All $\frac{1}{4}$ W, 10%

Potentiometers

VR1 5k Ω skeleton pre-set

Capacitors

C1 1 μ F, 250V
C2 0.1 μ F, 250V
C3 2 off 0.22 μ F, 250V to make up 0.1 μ F, 500V
C4 1,000pF mica

Semiconductors

TR1, 2, 3 & 4 Silicon npn ZTX300 or similar, 4 off
D1, 2 1N4007, 2 off

Switches

S1 Push-to-make button switch or slide switch

Miscellaneous

T1 Transformer, 9-0-9V primary, 240V secondary. Midget mains type such as Osborn MT9
LS1 Small earphone, 75 Ω or above (to 200 Ω)
X1 Mullard MX168 or similar low voltage type GM tube. Possible sources Henry's Radio, 20th Century Electronics Ltd., New Addington, Croydon, Surrey
B1 9V, PP3 or PP6 suits
Tube holder; co-ax cable; co-ax plug and socket; Veroboard; wire; solder; suitable box.

SETTING-UP

After assembly and before connecting the Geiger tube, switch on the circuit and listen for a faint low frequency hum coming from the earpiece which indicates that the inverter is working. Rotate the high-voltage-adjust variable resistor VR1 and the hum should change in intensity and frequency slightly.


Next, use a high impedance voltmeter to measure the voltage available at the socket for the GM tube and adjust this voltage to that required to drive the tube. Sometimes this voltage is marked on the side of the tube.

If the voltage is not marked and you are unsure of the correct operating voltage, connect the tube and increase the voltage slowly by means of VR1 until the tube begins to respond to the background radiation and clicks are heard. Increase the voltage by about 20V and then leave VR1 alone. The counting rate due to the background depends upon your locality, the operating voltage of the tube and the volume of the gas in the tube as well as its construction.

Using a gamma-ray sensitive tube, a background count rate of about 45 clicks per minute should be obtained.

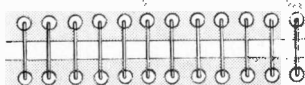Bring up a luminous watch or clock face to the tube and the count rate will increase. The Geiger counter is now ready for use. From time to time it will be necessary to adjust VR1 to compensate for the fall with use of the terminal voltage of the battery. Never operate the tube at too high a voltage so that it breaks into continuous discharge for this will decrease its useful life markedly.





INDUSTRY NOTEBOOK

By Nexus

SMALL IS BEAUTIFUL

From time to time I have been criticised for writing too often about the smaller enterprises in the electronics industry. But there's a lot to be said in favour of the homely neighbourhood store compared with the supermarket. Both have their role to play in our complex world. The same with electronics where there is still plenty of room for the small man in among the giants. And it is still demonstrable that for sheer profitability in the electronics industry the optimum size of the workforce is about 300 people. This is the maximum size where the boss still knows everyone and everyone knows the boss. Where people know what's going on, feel appreciated, have some job satisfaction.

It's the sort of size, too, where a company is still flexible. Reaction times are less and response is quicker. Product lines can be switched quickly to meet changing conditions. There is no multi-million pound investment in a single product line that might, and often does, go sour when brought to the market place.

A good example of what I mean is Brandenburg Ltd. which celebrated its 21st anniversary recently. It's a comfortable little unit employing 160 people in a 25,000ft² plant at Thornton Heath.

Turnover is running at over £1 million with £100,000 going for export. The company makes high voltage power supplies. Buy one of those super Cambridge 'Stereoscan' scanning electron microscopes and you'll find the high voltage supply made by Brandenburg.

The lethal punch in Rentokil electronic fly-killers comes from another Brandenburg unit and radar displays, photocopiers, nuclear physics,

all are grist to the Brandenburg mill for EHT assemblies. Anything up to 100,000 volts—more if a "special" is required.

BUT GROWTH NECESSARY

Having said all that, it still has to be admitted that growth remains a prime business objective, even with companies like Brandenburg. Nearly all managing directors are dedicated to growth as a desirable end in itself. The challenge is to keep growth profitable. With present rates of inflation it is natural that turnover should increase by, say, 20 per cent a year from the same volume of business, but if running cost increases are in excess of 20 per cent then the company is slipping behind. So you need greater efficiency.

GDS Sales Ltd., the Slough-based component distributors, have now implemented a computerised inventory management and order processing system based on an IBM 3/10 with disk file and video display terminals. The system is the result of over a year of planning and it really does its job. It gives a quicker order turnaround for the customer but, equally important, it spins off all the management information needed for true efficiency, especially in stricter control of the £400,000-worth of components stored in the main warehouse. GDS, in one of the most hotly competitive areas of electronics, has doubled turnover in two years and is keeping ahead of the game. In the same period the company has opened distributor operations, though as yet on a smaller scale, in Holland, Switzerland and Denmark.

TOP SECRET

High-flying Rascal Electronics Group is still showing the rest how to conduct a profitable world-wide business. Last published figures show increased turnover at £34.62 million and almost £3 million profit. And 1975, despite the prevailing gloom, is again forecast as a record year. Rascal chairman Ernest Harrison is one of the most forthright men in the industry. But even he keeps mum over what Rascal is up to in the speech privacy market. Last year a new company was formed called Rascal-Datcom based in Salisbury. It is manufacturing equipment for speech scrambling—all rather hush-hush and we are told only that "the speech privacy market will grow in the next two years".

Harrison is a firm believer in small companies where people are well-motivated. As soon as a Rascal company gets too big for real efficiency it is split and a new company formed. There are acquisitions, too, such as British Physical Laboratories who recently joined the Group.

THE BIG LEAGUE

Of course you've got to be big and have huge resources to cope with projects of great magnitude. Satellites, for example.

This year sees Marconi getting its teeth into MAROTS, the European marine communications satellite due for launch in the Autumn of 1977. Marconi is prime contractor for the satellite payload with a contract price of £11 million.

Hawker Siddeley Dynamics has a budget of £9 million for the spacecraft. And MAROTS itself is only the experimental and pre-operational unit paving the way for a more advanced system.

British Aircraft Corporation has a £1.25 million contract for satellite sub-systems for the ISEE-B in the International Sun Explorer Satellite System. All these satellite contracts have been placed through the European Space Research Organisation.

BAC will also be busy this year working through the backlog of orders for the Rapier low-level air defence missile in which quite a number of electronics companies are engaged on sub-contracts. BAC took orders last year for a staggering £100 million of Rapier systems, the bulk of them from the Middle East. Total Rapier sales are now well over £200 million.

NORTH SEA ELECTRONICS

And whatever the dividends from North Sea oil in the years ahead, there's certainly plenty of business there today. The Post Office, for example, is spending a cool £8 million on quadruple diversity troposcatter systems out to the rigs operated by the Total, Mobil and Occidental Groups. Marconi gets £1.5 million of the work for the shore terminals. Marconi is also supplying huge quantities of other equipment including the privately owned troposcatter links run by BP and Phillips Petroleum.

Nobody has yet worked out the cost of defending the rigs once they become operational. Certainly there will be a need for patrol vessels and aircraft fitted with radar, sonar and communications. It's a whole new world of opportunity for the electronics industry.

Just in case anyone gets the idea that the giants can only move slowly, let me recount a story out of the £200 million a year turnover Pye of Cambridge Group. Pye TVT did a rush job for Australia to get colour TV outside broadcast vans delivered in time for the opening of the colour service on March 1, 1975. By working round the clock a twelve week installation and testing procedure was telescoped to four weeks.

NEW LOW PRICES!

Sinclair Scientific kit

(Was £19.95 - save £5!)

£14.95
(INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range - features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

sin and arcsin,
cos and arccos,
tan and arctan,
automatic squaring and doubling,
log₁₀, antilog₁₀, giving quick access to x^y (including square and other roots),
plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer - they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

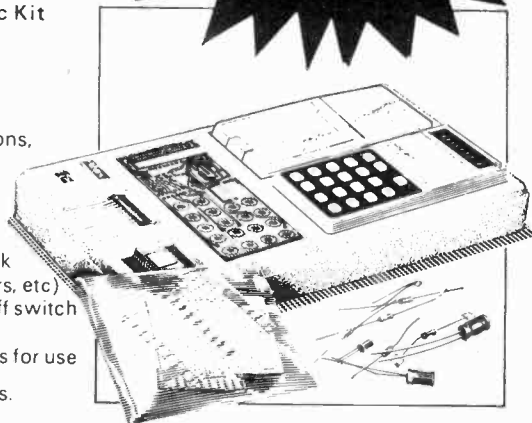

Features of the Sinclair Scientific



● **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

● **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.

● **200-decade range**
10⁻⁹⁹ to 10⁺⁹⁹

● **Reverse Polish logic** Post-fixed operators allow chain calculations of unlimited length - eliminate need for an = button.

● **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

● **Genuinely pocketable**
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.

NEW LOW PRICES!

Sinclair Cambridge kit

(Was £14.95—save £5!)

Now only
£9.95
(INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below — then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this

money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question.

All parts are tested and checked before despatch — and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £14.95 inc. VAT

Price built £21.55 inc. VAT.

Cambridge

Price in kit form £9.95 inc. VAT.

Price built £13.99 inc. VAT.

Features of the Sinclair Cambridge



- Uniquely handy package.
4 1/3" x 2" x 1 1/16", weight 3 1/2 oz.
- Standard keyboard.
All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, x, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £10.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
FREEPOST St Ives,
Huntingdon, Cambs. PE17 4BR

Please send me

- ☐ Sinclair Scientific kit at £14.95
☐ Sinclair Scientific built at £21.55
☐ Sinclair Cambridge kit at £9.95
☐ Sinclair Cambridge built at £13.99

All prices include 8% VAT.

*I enclose a cheque for £.....,
made out to Sinclair Radionics Ltd,
and crossed.

*Please debit my *Barclaycard/
Access account. Account number

--	--	--	--	--	--	--	--	--	--

*Delete as required.

Signed _____

Name _____

Address _____

Please print. FREEPOST — no stamp
needed.

sinclair

Sinclair Radionics Ltd,
FREEPOST St. Ives,
Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

PATENTS REVIEW...

BANISHING THE STEREO SEAT

Domestic stereo systems suffer from the disadvantage that a good stereo image is obtainable only at that part of the room where the axes of the two speakers intersect. Omni-directional speakers are less critical over listening position, but are unable to produce a truly firm stereo image anywhere in the world. In BP 1 368 070 Andrei Vladimirovich Borisenko, of Leningrad, has a proposal which could well enable a good solid stereo image to be obtained over a wide area of a listening room.

As the inventor points out, image localisation depends on the intensity of sound heard from each loudspeaker and the time at which it arrives at the listener's ears. As the listener varies his position in a room, so both the relative level heard at each ear and the relative arrival time sensed at each ear also varies. The proposal is to use acoustic focusing devices to ensure that the intensity and arrival time of sounds heard by a listener are effectively constant over a wide area of the listening room.

As in conventional systems, two loudspeaker cabinets are used, each with three types of transducer (woofer, tweeter and mid-range) are used. But two mid-range units are arranged in each cabinet as a horizontal pair and they beam their sound into the room via a laminar acoustic lens. This takes the form of a number of vertical parallel plates, see Fig. 1.

BP 1 368 070

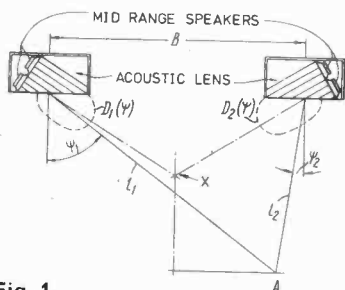


Fig. 1.

The plates are made from wood or plastic, are arranged vertically, and are of varying length. When the listener stands at position X the plates have virtually no influence or effect on the sound waves from the mid-range speakers. But as the listener moves away from the position X towards one side, the nearest speaker's plates both diminish the level of sound to that ear and delay it in dependence on how close and thus how far off the axis of the plates he is standing.

Obviously, the dimensions and angling of the plates will be critical and the patent suggests that, with the speakers 2.4 metres apart, each should have between six and eight plates, set at 40 degrees to a straight line drawn between the speakers.

PHASE CONVERSION

Single phase supplies may be converted into multi-phase supplies either by using a single phase motor driving a multi-phase alternator or by phase shifting the single phase supply in advance and retard by passive networks.

In BP 1 362 195 Raymond Russell of Newcastle-upon-Tyne claims that accurate phase shift results may be obtained from simpler passive networks, than those usually recommended. He suggests taking as a starting point the observation that a single phase supply can be regarded as an unbalanced three phase system.

In Fig. 1 three identical arms are arranged in delta configuration. Each arm has a resistor R and a capacitive impedance Z_C . The reactive component X_C of the impedance Z_C is such that current leads voltage by 60 degrees. A single phase supply is connected across any two of the junction points 1, 2, 3 and the resulting three phase supply is taken off across the three star-connected windings T . The windings are connected between neutral point a and junction points, b, c, d between the resistors R and impedance Z_C .

The inventor specifies that it is essential to arrange for R to be equal in magnitude to the 60 degree capacitive impedance Z_C . A null method of achieving this is described by way of example. The first step is to take three nominally equal capacitors and, by putting trimmers in parallel with the two smallest, match them accurately with parallel resistors they are connected at Z in Fig. 2.

The next step is to provide, from a balanced three phase supply, three voltage outputs, V_A, V_B and V_C . This is achieved by connecting the supply to 1, 2 and 3 via three adjustable load resistors arranged in star configuration, connecting voltmeters across points 1, 2, 3 and 3, 1 and adjusting the resistors to balance the system. Voltmeters V can then be located between a and b, c and d , and null deflections obtained with trimmers, see Fig. 2.

It is claimed that a very high order of accuracy can be achieved.

BP 1 362 195

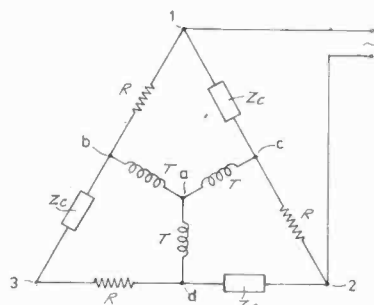


Fig. 1.

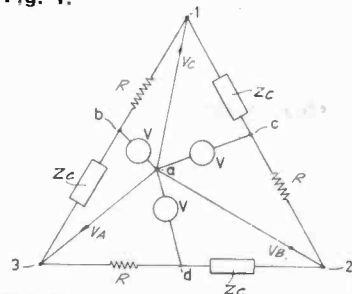


Fig. 2.

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 25p each

Readout —

A SELECTION FROM OUR POSTBAG

Readers requiring a reply to any letter must include a stamped addressed envelope. We regret that we cannot answer any technical queries on the telephone.

"Wee Morag"

Sir—With regard to Mr Parfitt's letter January issue, I was astounded to discover that "wee Morag" from the local hamburger stall has at last made good, and is serving Boolean Breakfasts, incognito, in a Croydon hotel.

I met the lady under much the same unfortunate circumstances. I had occasion to ask her for "one hamburger with onion, and one without". Imagine my chagrin when I was served with one salt and one pepper, one tomato ketchup and one bill for 45p, but no hamburger and certainly no onion.

I questioned Morag, inquiring as to the whereabouts of the food, only to be told, that, according to Boolean Algebra "hamburger and onion and hamburger and no onion, equals nothing", and was shown a truth table to verify that remarkable statement. The column of zeros at the end of the analysis somewhat overcame me. I must confess, and I was therefore too perplexed to see through the deception. Had I been less staggered, I would have pointed out that a hamburger is neither true nor false; it is instead merely present or absent; and that Boole is correct when his A's and B's are logical statements, and wrong when they are hamburgers and onions (or for that matter, eggs and bacon).

Alistair C. Thompson,
Lanarkshire.

On the table

Sir—The fallacy lies in the use of $A + A.B = A$ to describe Mr Parfitt's breakfast, see *Readout*, January issue. This equation is good only when A and B are independent events.

The breakfast choice was "egg or egg and bacon". The "egg and bacon" is really "bacon if and only if egg and bacon together", which is

not $A.B$ (in Mr Parfitt's notation) but $B \equiv A.B$. Thus we have to consider two breakfasts (mutually exclusive)

Egg (A) or
Egg and bacon ($B \equiv A.B$)
in an enclosure or relationship.

Mr M. J. Hughes dealt with this in "Logic Tutor", Part 5 (P.E. Sept. 1973) and gives the equation

$$Q = AB + \bar{B}\bar{A}$$

with truth table

A	B	Q
0	0	0
1	0	1
0	1	1
1	1	0

No one can say that some P.E. readers are guilty of not doing their homework.

C. F. Tozer,
Dorset.

Misconception

Sir—There is a very simple answer to Mr Parfitt's problem (*Readout*, January 1975).

By applying his own brand of mathematical analysis, he should have seen that he had only to walk out of the hotel or walk out and pay his bill. He would then argue that both courses of action are equivalent to the first, and he would never notice that he had paid his bill in full.

To be more serious, the apparent paradox comes from a misconception of the nature of Boolean variables. In the expression: $A + (A.B) = A$, "A" and "B" are statements which may be "true" or "false". The expression should be read "If A, or both A and B are true, then A is true."

When written in this manner the validity of the expression is patently obvious.

The paradox of the "Boolean bed and breakfast" arises because Mr Parfitt has thought of Boolean variables as objects instead of as statements.

I hope this letter may serve to clarify the thoughts of any non-mathematically-minded P.E. readers, especially those who run hotels, and have found unexpected losses on their December balance sheets.

J. Dickson,
Rochester, Kent.

Bacon and eggs

Sir,—One of the wonderful attractions of mathematics is how easily confusion can arise. Confusion is wonderful because it is the opposite to "Blue Peter": it can be resolved only by going into it more deeply, providing great pleasure and satisfaction.

In mathematics many different algebras use the same symbols for different meanings, + and . vary according to whether they are applied to numbers, vectors, matrices, sets, truth statements, switching circuits or whatever. Mathematicians deliberately introduce this joyous confusion in order that it should be resolved by *comparing the different algebras*. If this comparison is not done, you may as well have different symbols for each different algebra (as in O-level SET algebra which use $\cup$ and $\cap$ instead, reducing the depth to superficial levels).

If we were in the algebra of numbers, then given

$$A.B + A = A$$

we could deduce $A.B = 0$ by subtracting A from both sides or by adding $-A$ to both sides. But in Boolean algebra, + does not mean number or quantity addition, and subtraction does not exist.

If comparison is not acceptable, the alternative is to put more depth into the Boolean algebra: + meaning "either one or other or both" and "=" also not being straightforward. In the eggs and bacon situation, the algebra should be interpreted as "Given Bacon and Eggs or Eggs, necessarily implies being given Eggs." The nearest to the number-A in Boolean algebra is $\bar{A}$ meaning the opposite of A (no eggs or maybe the rest of the menu).

If $\bar{A}$ is used the $A.B + A = A$ gives $A.A.B + \bar{A}.A = \bar{A}.A$ which gives $0 = 0$

Translated this means that although the study of mathematics, or breakfasts or waitresses or managers can give 1/0 pleasure, staying in hotels always leaves one penniless.

M. Everett.
Saltdean.
Sussex.

P.B. PRODUCTS LTD.

ELECTRONIC · SCIENTIFIC · INSTRUMENTS
57 HIGH STREET · SAFFRON WALDEN · ESSEX CB10 2DP · ENGLAND
Telephone: Saffron Walden 22876 Telex: 817201

FREE RESIST COATED CIRCUIT BOARD

For every order placed for any of the products listed below, each order will receive a piece of fibre glass circuit board, approx. size 6in x 6in, coated with negative resist.

DRILLING MACHINES AND DRILL KITS

Specially designed for engineers, lab workers, jewellers, engravers, sculptors, model makers and hobbyists. These powerful, low power, drilling machines are capable of drilling holes up to 3mm in diameter in any material. They will DRILL, SAW, GRIND, BURR, BRUSH AND POLISH.

Reliant Drill with 3 collets, 9,000 r.p.m. £3-68 (50p).

Reliant Drill Kit, 3 collets, 20 tools £8-34 (97p).

Drill Stand, used horizontally or vertically for drilling, sawing, buffing, or as a miniature lathe for turning small components between centres £8-34 (97p).

MAJOR DRILL KIT for the man with everything. Contains 9,000 r.p.m. super drill, power unit, drill stand, 40 assorted tools, presentation box, normally £34-76 only £27-87 (£3-22).

SOLDERLESS MODULAR BREADBOARDS

These OEC breadboards are used throughout the world for making prototype and production working circuits. The patented contact allows components to be inserted over and over again without soldering.

S DEC. Discrete components only. Normally £1-98 only £1-32 (25p).

T DEC. Station for one integrated circuit normally £3-63 only £2-43 (39p).

U DEC. A. Discrete and I.C. components normally £3-99 only £2-67 (40p).

Each Dec. is boxed and has instructions, carriers, plugs, coloured leads are also available.

COPPER CLAD GLASS-FIBRE CIRCUIT BOARD

$\frac{1}{16}$ in Single sided normally 85p per sq. ft. only 55p per sq. ft. (29p).

$\frac{1}{16}$ in Double sided normally 93p per sq. ft. only 60p per sq. ft. (30p).

$\frac{1}{16}$ in Single sided normally £1-52 per sq. ft. only 75p per sq. ft. (31p).

$\frac{1}{16}$ in Double sided normally £1-60 per sq. ft. only 80p per sq. ft. (31p).

RESIST COATED CIRCUIT BOARD

Positive or negative resist, single or double sided copper clad fibre glass circuit board. State which required.

Size inch	SS	$\frac{1}{16}$ in DS	SS	5/64in or $\frac{1}{16}$ in or $\frac{1}{8}$ in DS	1.00mm or 1.19mm or $\frac{1}{16}$ in paper SS	DS
3 x 4in	6p	7p	10p	12p	8p	9p
6 x 8in	24p	25p	46p	48p	26p	27p
8 x 10in	40p	41p	78p	80p	42p	43p
12 x 12in	72p	73p	98p	£1-00	74p	75p

Please add 8% VAT and 20p postage to all above orders.

Example positive or negative coated 4 x 3in 12p each + VAT and post. 5 x 5in 25p each + VAT and post. Please quote if positive or negative coated and size. Ferric chloride 5 litre etchant mix £1-50 (35p). Temperature controlled, air agitated etching tank £85-00 (£8-96). Please add to the sum shown in brackets after the price to cover the cost of post and VAT.

SPARKRITE Mk II

Electronic Ignition... Better on all points



Because you keep your points!


The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly — with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleaner plugs — they last 5 times longer without attention. ● Faster acceleration. ● Faster top speeds. ● Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

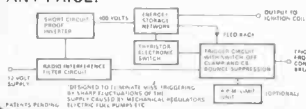WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite Mk II — full capacitive discharge electronic system — not just a transistorised inductive discharge booster.

PRICES

D.I.Y. Kit only £10-93 incl. VAT and P & P

Ready Built Unit £13-86 incl. VAT and P & P

(Both to fit all cars with coil/distributor ignition up to 8 cylinders).

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES

(Dept PE 2) 82 Bath Street

Walsall WS1 3DE Phone 33652

Please supply

Sparkrite Mk. 2 D.I.Y. Kit(s) at £10-93 each incl. VAT and P & P (Will make pos. or neg. earth) ☐

Sparkrite Ready Built Neg. Earth Unit(s) at £13-86 each incl. VAT and P & P ☐

Sparkrite Ready Built Positive Earth Unit(s) at £13-86 each incl. VAT and P & P ☐

NAME _____

ADDRESS _____

I enclose cheque/P.O. for £ _____
 Send SAE for brochure.

PHONOSONICS

**SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET**

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A must for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11.49
8 channel component set (excl. thyristors)	£20.32
Power supply component set	£4.78
PCB for 4 frequency channels	£2.50
PCB for power supply and 8 lamp drivers	£1.25

P.E. CCTV CAMERA Details in List

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work, or for home-movie shows.

Component set, incl. PCB £2.95

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:	
Set of resistors, capacitors and presets	£5.96
Stereo printed circuit board	£1.28
Pre-Amplifier:	
Set of resistors, capacitors, potentiometers and switches—	
Standard Tolerance Set	£10.57
Superior Tolerance Set	£18.04
Stereo PCB (as Published)	£2.20
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4.58
Printed circuit board	72p

HI-FI TAPE LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter)	£22.85
Mono component set (excl. panel meter)	£13.31
Power supply component set	£3.72
Stereo main PCB	£2.50
Stereo sub-assembly PCB	86p

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB)	£2.30
Regulated power supply (including PCB)	£3.71

PROJECT Q4 (P.W. Oct. 73/Jan. 74)

Multi-system Quadraphonic Decoder.

Decoder component set	£13.74
Power supply components	£3.22
Printed circuit board	£2.80

SEMICONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB

£8.56

REVERBERATION UNIT (P.W. Nov./Dec. 72)

A high-quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit)
Printed circuit board

£6.44
£1.40

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB)

£2.20

PHASING CONTROL UNIT (P.E. Oct. 74)

(for use with above Phasing Unit)
Component set (including PCB)

£3.50

P.E. SOUND SYNTHESISER

The well-acclaimed and highly versatile Synthesiser published in P.E. Feb. 1973 to Feb. 1974.

Component sets and printed circuit boards. List shows full details including discounts.

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

Component set £3.41
Printed circuit board £1.10

RHYTHM GENERATOR (P.E. Mar./Apr. 74)

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures. See list for discount.

Tempo, Timing and Logic Circuit

Component set (excl. switches)
Double-sided PCB for above

£17.25

£2.30

Mixer, Pre-amp and Effects Circuits

Component set
Printed circuit board

£12.70

£2.67

Monitor Amplifier

Component set and PCB
Power Supply

£3.10

£5.85

ULTRASONIC TRANSMITTER-RECEIVER

A highly sensitive and long range "invisible beam" detection circuit with numerous applications.

Component set with PCBs, but excluding transducers

£4.40

P.E. RONDO

PCB details in List

POWER SLAVES

PCB details in List.

P.E. ELECTRONIC PIANO HOME INTERCOM

Details in List.

PHOTOPRINT PROCESS CONTROL

(P.E. Jan./Feb. 72)

For colour and B. & W. an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter)
Printed circuit board

£8.85
£1.60

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)

Dual-purpose dark-room unit with good accuracy.

Component set with PCB, but excluding meter £4.00

WIND AND RAIN UNIT (P.E. Oct. 73)

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB

£2.40

PCB LAYOUT AND
CIRCUIT DIAGRAMS
SUPPLIED WITH ALL
PCBs DESIGNED BY
PHONOSONICS

LIST

Send S.A.E. for free list
giving fuller details of
kits, PCBs, and other
components

P. & P.
Add 18p to all orders

VAT
Add 8% (or current
rate if different) to
total order cost in-
cluding P. & P.

OVERSEAS

P. & P. will be charged at cost.
VAT does not currently apply. List
gives fuller details including kit
weights. Charge for list: Europe
10p, other countries 20p.

**COLOUR CODE
IDENTIFICATION
SUPPLIED WITH MOST
KITS AND AS PART OF
LIST**

Semiconductors				Integrated Circuits				Zeners				Electrolytic Capacitors (uF/V)				Polyester (uF)				Tantalum (uF/V)			
AC128	20p	BFY50	22p	2N3702	12p	709 8-pin DIL	40p	3.3V 400mW	12p	0 47/63V	8p	47/63	7p	470/40	20p	0 01	3p	0 1/35	12p				
AC176	20p	BFY51	22p	2N3703	12p	709 TOS	40p	3.9V 400mW	12p	1 5/63V	8p	100/40	8p	500/64	40p	0 015	3p	0 22/35	12p				
BC107	13p	BSY95A	22p	2N3704	12p	723 TOS	95p	5.1V 400mW	15p	2 2/63V	8p	100/25	8p	680/25	20p	0 022	3p	0 47/35	12p				
BC108	13p			2N3819	35p	741 8-pin DIL	40p	5.6V 1/3W	20p	4 7/63	8p	100/40	8p	680/40	25p	0 033	3p	1 0/35	12p				
BC109	13p			2N4060	12p	747 14-pin DIL	115p	5.2V 400mW	15p	6 8/40	8p	100/25	8p	1000/16	25p	0 047	3p	1 5/35	12p				
BC147	12p			2N4871	36p	748 TOS	40p	5.1V 400mW	15p	10/25	8p	100/40	8p	1000/16	25p	0 1	4p	4 7/35	12p				
BC148	12p			2N5245	51p	748 8-pin DIL	63p	11V 1W	25p	15/63	8p	100/63	13p	1000/16	25p	0 15	5p	10/25	16p				
BC149	12p			2N5777	45p	748 14-pin DIL	83p	12V 400mW	15p	22/25	8p	150/63	13p	1000/25	30p	0 22	5p	10/25	16p				
BC157	13p					7400	40p	18V 400mW	15p	33/63	8p	220/16	7p	2200/40	63p	0 33	7p	15/6 3	16p				
BC158	13p					7402	20p	20V 400mW	15p	47/10	8p	220/16	7p	2200/40	63p	0 47	8p	22/16	16p				
BC159	13p					7410	20p	20V 1/3W	20p	33/63	8p	220/16	7p	2200/40	63p	0 68	11p	47/6 3	16p				
BC182L	12p					7417	44p	27V 400mW	15p	47/10	8p	220/16	7p	2200/40	63p	1 0	14p	47/16V	25p				
BC184	12p					7443	44p			47/25	8p	220/16	7p	2200/40	63p	2 2	24p	100/3	16p				
BC204	14p					7489	7p																
BC209C	14p					7489	7p																
BC212L	15p					7489	7p																
BC213	15p					7489	7p																
BC478	22p					7489	7p																
BCY71	22p					7489	7p																
BF178	40p					7489	7p																

**PHONOSONICS, DEPT. PE33, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY**

Practical Electronics March 1975

251

TRANSISTORS AC107 0-16 BC159 0-13 C111E 0-55 76217 0-30 AC126 0-13 BC171 0-16 CV5441 0-27 V405A 0-25 AC127 0-13 BC172 0-16 CV7464 0-10 V10-50 0-40 AC128 0-12 BC173 0-16 CV7594 0-25 Y25 0-10 AC138 0-20 BC184 0-16 CV7648 0-30 Z116 0-75 AC141 0-20 BC208 0-12 CV8762 0-40 ZTX107 0-12 AC142 0-20 BC209 0-13 MD533 0-30 ZTX302 0-17 AC153 0-22 BC212 0-14 ME102 0-12 ZTX502 0-17 AC176 0-15 BC331 0-30 NK7162 0-25 2G126 0-21 AC176 MP BC336 0-15 NK7164 0-25 2G306 0-44 AC128 0-25 BC337 0-15 NK7212 0-20 2G345A 0-18 AC178 0-25 BC211 0-28 NK7221 0-17 2G402 0-25 AC177 0-28 BD131 0-40 NK7224 0-15 2N526 0-46 AC199 0-22 BD132 0-40 NK7270 0-15 2N697 0-15 AC199 0-22 BD132 0-40 NK7270 0-15 2N697 0-15 AC199 0-22 BD132 0-40 NK7270 0-15 2N697 0-15 AC199 0-22 BD132 0-40 NK7270 0-15 2N697 0-15 AD161 0-38 BD139 0-60 OC28 0-50 2N753 0-55 AD162 0-38 BD140 0-60 OC35 0-46 2N1304 0-19 AD161 MP BF167 0-24 OC36 0-55 2N1305 0-19 AD162 0-38 BF194 0-12 OC45 0-14 2N1309 0-25 AF115 0-26 BF196 0-15 OC70 0-11 2N1754 0-20 AF116 0-26 BF197 0-16 OC71 0-11 2N2484 0-30 AF178 0-50 BF274 0-39 OC72 0-15 2N2926 0-14 AS552 0-22 BF279 0-30 OC81 0-17 2N3055 0-50 BC107 0-09 BF845 0-33 OC201 0-30 2N3702 0-12 BC108 0-09 BFY50 0-20 OC445K 0-25 2N3703 0-12 BC109 0-09 BFY51 0-20 SGS26920 0-15 2N3704 0-14 BC142 0-30 BFY52 0-20 SGS26942 0-14 2N3710 0-10 BC143 0-30 BFY81 0-65 SGS26949 0-15 2N3711 0-10 BC147 0-10 BS338 0-20 SGS27022 0-18 2N3713 0-20 BC148 0-10 BS339 0-20 SU203 0-65 2N4047 0-25 BC149 0-10 BS340 0-31 TK100 0-75 2S322 0-46 BC157 0-11 BS541 0-31 TIS90M 0-33 2S712 0-46 BC158 0-11 C111 0-50 TIS91M 0-33 2S745 0-46									
TESTED S.C.R.s 50 PIV 3A TO-66 CASE 0-25 100 PIV 3A TO-66 CASE 0-25 200 PIV 3A TO-66 CASE 0-30 400 PIV 3A TO-66 CASE 0-40 600 PIV 3A TO-66 CASE 0-50 800 PIV 3A TO-66 CASE 0-60 ZENER DIODES CV7204 11V STUD TYPE 0-60 THYRISTOR BT 109 CON BRI 0-75 OPTOELECTRONICS ORP 12 0-48 OCP 71 0-48									
LOGIC I.C.s TYPE MC330 0-15 MC946 0-14 MC332 0-15 MC948 0-15 MC333 0-15 MC952 0-15 MC944 0-16 MC9093 0-40 MC945 0-30 MC9097 0-40 74 SERIES I.C.s SN741 0-45 SN7400 0-18 SN7400 0-18 SN7405 0-18 SN7401 0-18 SN7406 0-39 SN7402 0-18 SN7490N 0-74									
BONANZA 1 MILLION CAPACITORS WE CANNOT NAME THE WELL KNOWN MAKER DUE TO THE LOW PRICE. THEY ARE OF THE VERY LATEST DESIGN AND TYPE 100 MIXED VALUES AND TYPES VALUED AT OVER £5 YOURS FOR ONLY £1.50 NO MORE TO PAY (WHAT A BARGAIN) Electrolytics 5 µF at 40V, 100µF at 63V, 680µF at 16V etc Polyester 1500pF at 400V, 0.0015µF at 400V, 0.0086µF at 400V Minutaire Metallized Film 0.22nF at 250V, 47nF at 250V etc Ceramic Plate 82pF at 100V, 2200pF at 40V, 4700pF at 40V etc etc etc etc etc etc etc etc etc etc									
SPECIAL OFFER I.C.s BULK PURCHASE BRAND NEW 14 PIN DECADE COUNTER SN7490 2 FOR ONLY £1.00 SPECIAL OFFER BULK PURCHASE BRAND NEW BC 337 TRANSISTORS NPN TO 84 case 20 FOR £1.00									
SPECIAL OFFER RESISTORS CARBON FILM CR 25 TYPE 1m2 2m2 10% 10 120 470K 5% etc etc etc 200 MIXED FOR ONLY £1.00 SPECIAL OFFER DIODES IN4148 BRAND NEW 40 FOR ONLY £1.00 SPECIAL OFFER 1.C 1TT 7CA270C ONLY £3.00									
MAINS TRANSFORMER 240V INPUT 12V 8A 25V 1 1A 30V 1 5A C CORE £2.50 P & P 25p. PAPET TAPE MOTOR 220V 50Hz £2.50 P & P 25p. AMPLIFIER 5V 500MW 0.95p. P & P 5p. P. A. R. BISTABLE RELAY LATCHING 24V DC 4 C/O CONTACTS 0.65p. RELAY KEYSWITCH 24V 1 POLE 2 WAY NEW AND BOXED 0.55p. RELAY T.M.C. MINIATURE 3.300 ohms 2 POLE 4 WAY 0.55p. TELEPHONE DIALS BRAND NEW £1.00 EACH P. & P. FREE ELECTROLYTICS 0.1µF 250V 8p. 25µF 50V 8p. 40µF 16V 4p. 16-16µF 500V CAN TYPE 35p. 32-32µF 450V CAN TYPE 35p. CAPACITORS 0.047µF 400V 8p. 125µF 10V 7p. 100µF 10V 8p. FREE OFFER ONE J PACK OF YOUR OWN CHOICE WITH ALL ORDERS VALUED AT £5.00 AND OVER PLEASE ADD 10% TO ALL TOTAL ORDERS FOR POST AND PACKAGE.									
MAIL ORDER DEPT. ONLY (Callers by appointment) J.E.T. ELECTRONICS 90a Mawney Road, Romford, Essex RM7 7DA Telephone: Romford 61486 SPECIAL OFFERS ARE AVAILABLE ONLY WHILE STOCK LASTS									

PC ETCHING KIT
Contains 1lb ferric chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner, dish for etching and instructions. £3.30.

RESISTORS AND CAPACITORS
500 assd. resistors £1-40, 2500 £5, 15 different trimmers, air-spaced and compression up to 1250F £1.

VEROBOARD
100 sq ins assorted sizes and pitches, about 8 bits £1-10.

8 PIN DIL 741's
FULL SPEC. OF COURSE
10+26p 25+23p
100+21p 250+20p

FERRIC CHLORIDE
Anhydrous technical quality in 1lb double sealed pack, 1lb 80p, 3lb £1-65, 10lb £4-45, 100lb £35.

P.O. AMPLIFIER UNIT
Contained in steel case 5 1/2 x 5 1/2 x 2 1/2 inches. 2 x GET1 16 transistors on heat sinks, 3 pot cores, 2 30V zeners, 4 audio transformers, 1% R's & C's. With circuit £1.


SEMICONDUCTORS
All new full spec devices: AC127 AC128 AC176 AC177 AC187 AC188 all 20p; BC107, 8, 9 10p; 723C 75p; 741C 35p; IN194 4p; IN4001 6p; IN4004 8p; IN4007 12p; 800V 1 1/2 10p; 400mW zeners 10p; 400V 6A triac £1.

7lb BARGAIN PARCELS
Hundreds of new components—pots, resistors, capacitors, switches.
All prices include VAT and postage. See list, enquiries.
Computers, equipment and components always wanted for cash.

GREENWELD ELECTRONICS (PE3)
Head office, mail-order dept. Wholesale/Retail shop: 51 SHIRLEY PARK RD., SOUTHAMPTON SO1 4FX. Tel. (0703) 772501. Also callers welcome at 21 Deptford Broadway SE8. Tel. 01-692 2009 and 38 Lower Addiscombe Rd., Croydon. Tel. 01-688 2950.

Dimmit

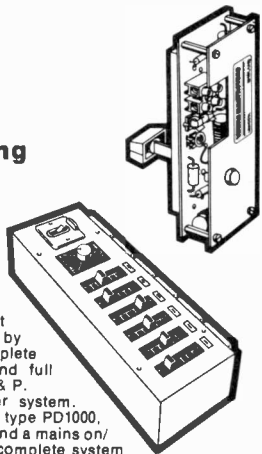range of light dimmers and lighting control systems



Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppressed, 60mm slider range, size 12 x 5 x 4cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studio, etc. Complete with scale plate, fixing screws and full instructions. £7.25 inc. VAT and P. & P.

Illustrated is the DD61 dimmer system. Contains: six 1000W slider dimmers type PD1000, six outlet sockets, a master control and a mains on/off switch. Size 59 x 22 x 12cm. A complete system in one unit for stage or disco lighting, etc. Other systems available with 1000W or 2000W dimmers with 2-pre-set and master controls.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for industrial heating applications, etc. Rotary and slider control versions. Ratings: 1000W; 2000W; 3000W; 110V and 240V.


Model SL800 sound to light converter. Modulates the light in time with sound. Built in microphone. Just place unit near any sound source—radio, hi-fi, TV, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800W. Complete with full instructions.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Personal callers welcome, visit our showroom for a demonstration of any of the modules or systems.

YOUNG ELECTRONICS LTD.


184 Royal College Street, London NW1 9NN. Tel. 01-267 0201

SUPERSOUND 13 HI-FI MONO AMPLIFIER

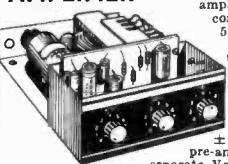

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power out-put transistors push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz ± 3 dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/240V. PRICE £12.50. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

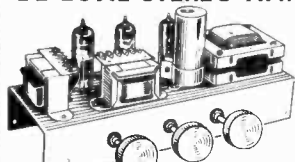

A.C. mains 200-240 v. U.S.A. 115 v. heavy duty fully insulated fully insulated mains transformer with full wave rectification giving a negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £10.75. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 5 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. Price £5.20. P. & P. 35p.

VYNAIR & REKINE SPEAKERS & CABINET FABRICS ap. 54 in. wide. Our price £1.30 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully insulated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohm. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. P. & P. 40p. BARGAIN PRICE £4.20

FEW ONLY. High grade mains transformer with grain orientated lamination. Primary 200/240. Secondary 15.5 volts at 0.6 amps and 6.6 volts at 0.3 amps. Size 2 1/2" long x 2 1/2" wide x 2 1/2" deep overall. £1.35 plus 25p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10 15-20-25-30-35-40-60v. half wave at 1 amp. or 10-10-10 20-20-20 30-30-30v. at 2 amps full wave. Size 3 1/2" long x 3 1/2" wide x 3 1/2" deep. Price £2.60. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pro. 200/240V. Sec. 9-0-9 at 500 mA. £1.25. P. & P. 25p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.40. P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.00. P. & P. 35p.

3 VOLT RELAY. 100 mA single pole normally closed. 2 for 60p. P. & P. 15p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-20KHz. Gain 20dB. Solid state amplification size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price £1.20. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.


8 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. **Diode Equivalents** 90p. **Transistor Equivalents** £1. **Transistor Characteristics** £1.30. **POST FREE** All three together £3.

NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1. Post Free. 8 pole 3 way 2 bank low loss Yaxley type switches 11" sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday. Prices and specifications correct at time of press. Subject to alteration without notice

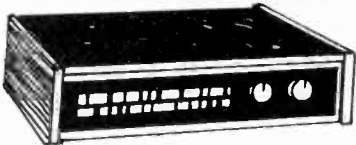HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-grain, low noise IF stages. Automatic frequency control to 'lock on' station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide x 8 1/2" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £23.00. Post and Packing 50p.

STEREO-DECODER SIZE 2" x 3" x 1 1/2"

Ready built. Pre-aligned and tested. Sens. 20-5600V for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5 plus 10p P. & P. Stereo beacon light if required 40p extra.

LATEST HI SENSITIVITY UNI-DIRECTIONAL SLIM-LINE CONDENSER MICROPHONE as used by many professionals. Very low acoustic feedback. Available in Hi impedance or low impedance. State which required. £13.50. P. & P. 25p.

LATEST AGS GP81/18C mono compatible cartridge with 10 stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.75. P. & P. 15p.

SONOTONE 97AHC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.78. P. & P. 15p.

LATEST RONETTE T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £1.60. P. & P. 15p. **LATEST RONETTE T/C MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7 1/2" wide x 3 1/2" deep x 6 1/2" high. Ready built and tested. PRICE £5.50. P. & P. 50p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. PRICE £6.70. P. & P. 60p.

HI-FI LOUDSPEAKER SYSTEM MK.II

Beautifully made simulated teak finish enclosure now with most attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover (approx). AVAILABLE IN NOMINAL 4 ohm, 8 ohm or 16 ohm impedance (state which). **OUR PRICE £9.50 each. Carr. 90p.**

Cabinet Available Separately £5.00. Carr. 90p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.00. Carr. 75p.

LOUDSPEAKER BARGAINS

5in. 3 ohm £1.25. P. & P. 15p. 7 x 4in. 3 ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 5in. 3 ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £2.50. P. & P. 30p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £4.65. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms, £1.25 + 20p. P. & P.

BRAND NEW. Bakera Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFiux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.50. 35w. £8.50. P. & P. 40p.

"POLY PLANAR" WATER-PROOF, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send 8 A.E. for details. Only £6.50 each. P. & P. 34p. **NOW ALSO AVAILABLE** 8in. 10W r.m.s. 20W peak 40Hz-20,000Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. £4.32. P. & P. 25p.

SPECIAL BARGAIN OFFER!

Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £28.00 + p. & p. 60p.

HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response ± 3 dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: ± 3 dB 12-15,000 Hz. Bass boost approx. to ± 12 dB. Treble cut approx. to -16 dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large 8 A.E. **AMPLIFIER KIT** £12.95 P. & P. 30p **POWER PACK KIT** £4.32 P. & P. 40p **CABINET** £4.32 P. & P. 40p (Post Free if all units purchased at same time) Full after sales service

Also available ready built and tested £28.00. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II. Designed for Hi-Fi reproduction of records. A.C. Mains operated. Ready built on plated vvy gauge metal chassis. 7 1/2" w. x 4 1/2" d. x 4 1/2" h. Incorporates ECC83, EL84, 280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £6.50. P. & P. 45p. **HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £5.50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.50. P. & P. 25p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.50. P. & P. 25p.

PRICES INCLUDE VAT

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTE APPROPRIATELY. P. & P. OVERSEAS ORDERS CHARGED EXTRA.

THE NEW NELSON-JONES FM TUNER



PUSH-BUTTON VARICAP DIODE TUNING (6 Position)

('WW' JUNE '73)

Exclusive Designer Approved Kits

What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:-

- MOSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

- PHASE LOCKED** Stereo decoder with Stereo mute, see below
- LED** fine tuning indicators.
- PUSH BUTTON** tuning (with AFC disable) over the FM band (88-104)
- IC STABILISED** and S/C protected power supply.
- CABINET** double veneered against warp.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting 0.75uV. Image rejection -70dB.I.F. Rejection -85 dB.


Basic tuner module prices start as low as £12.31, with complete kits starting at £26.95 (mono) + P.P. 65p, and of course all components are available separately.

Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

PORTUS AND HAYWOOD PHASE LOCKED DECODER (W.W. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED.

PLEASE NOTE. Existing tuners are readily convertible and kits/parts are available for this purpose.

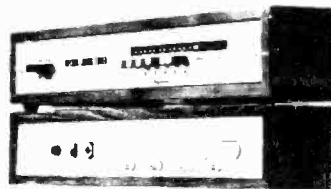TEXAN AMPLIFIER. We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at £30.78 plus P.P. 65p including Teak Sleeve.



NEW LOW COST STEREO TUNER Available as basic or complete kits

Basic stereo tuner £15 post free.
Basic mono tuner £12 post free.
6 position push button units with integrated pots £2-92.



No alignment required. Mullard LP1186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with Interstation Mute, restricted range AFC, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

TYP. SPECIFICATION
2uV for 30dB S/N
Image rejection 40dB
IF rejection 65dB

VAT at 8% is included in all prices

PRICE Complete stereo kit £28.42
Complete mono kit £24.19
P. & P. 65p

INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106



TRAMPLUS

ELECTRONICS LTD
58-60 GROVE ROAD,
WINDSOR, BERKS.

FAST SERVICE.

SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

CATALOGUE/LIST FREE SEND S.A.E.

Digital Displays



- MINITRON 3015F
- 0-9DP £1.15 ea
- LED 0.3" digit
- 0-9DP £1.49 ea
- JUMBO LED 0.6"
- 0-9DP £2.25 ea
- LIQUID CRYSTAL
- 6 digit £18

LEDS 14P.

- MINI PIN SOURCE OR RED DIFFUSE
- LEDS. 209 STYLE. NO CLIP. 14P ea
- TIL209 RED LED & CLIP 17P ea
- BIG 1" RED LED & CLIP 18P ea
- ORANGE & GREEN LEADS:
- MINI 25P ea. BIG & CLIP 33P ea
- PS12 PHOTO IC/amp/switch £1.

DIGITAL CLOCK

- MOS INTEGRATED CIRCUITS.
- AYS1224 4 DIGIT CLOCK supplied with 14pin socket & data £4.25
- MM5311/14 6 DIGIT CLOCK with 28 pin socket & data £7.50
- 3DIGIT DVM AYS3500 £7.50
- 4DIGIT COUNTER/DRIVER £7.50

CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.
As used in imported types costing £100. Only requires a case & electronics. Heads supplied. Send for data 15p.

IC's & Semiconductors

- 702 OPA 69p
- 703 RF/IF 28p
- 709 TO99 21p
- 709 DIL 14 29p
- 710 DIL 14 36p
- 720 Radio £1.39
- 723 Regulator 67p
- 741 TO99 29p
- 741 DIL8 31p
- 741 DIL14 31p
- 747 Dual 741 89p
- 748 DIL 8 36p
- 1505 IC A/D Converter £7
- 7805 1A5V £1.59
- 7808 1A8V £1.69
- 7812 1A12V £1.69
- 7815 1A15V £1.69
- 76009 6W AF 75p
- 76013 6W AF £1.39
- 8038 Sig Gen £3
- CA3046 69p
- LM301 OPA 49p
- LM307 OPA 49p
- LM308 HiBoPa 95p
- LM309K Reg. £2.29
- LM371 RF/IF £2
- LM372N AF/IF £2
- LM373 13
- LM377 2x2H £2.69
- LM380 2W AF 99p
- LM381 2xpre. £2
- LM382 amp £2
- LM3900 4xOPA 69p
- MC1303 £1.20
- MC1306 49p
- MC1310 & LED £2.69
- MC1312 SQuamp £2.50
- MC1330 69p
- MC1339 11
- MC1350 55p
- MC1351 71p
- MC1352 71p
- MC1357 11
- MC1358 11
- MC1375 £1.25
- MFC4000 1W AF 35p
- MFC4060 54p
- MFC6030 52p
- MFC6040 90p
- MFC8010 £1.10
- MFC8040 11
- NE531 35V/us £2
- NE536 FET OPA £2
- NE540 Driver £1
- NE546 AM Rx £1.50
- NE550 2v ref 79p
- NE555 TIMER 67p
- NE556 Dual £1.50
- NE560 PLL £3.15
- NE561 PLL £3.15
- NE562 PLL £3.19
- NE565 PLL £2.69
- NE566 Gen £2.49
- NE567 code £2.69
- SN72709 709 29p
- SN72741 741 31p
- SN72748 748 36p
- SN76131 £1.20
- SN76660 FMIF £1
- SN76611 IF £1.25
- TAD 100 & IF £2
- 2N400E 13
- 2N402T £1.75
- 2N403 Servo £2.50
- 2N414 AM Rx £1.09
- 7400 etc gates 16p
- 7413 schmitt 31p
- 7447 driver £1.09
- 7470/72 32p
- 7473/74/76 39p
- 7475 48p
- 7490 Counter 63p
- 7492 Counter 69p
- 74121 mono 45p
- 74141 driver 83p

Full range in Cat...

SPECIAL OFFERS

- 741 29p MFC4000 35p
- 555 67p 2N414 £1.09
- BC107, BC108, BC109 9p ea
- 2N3055 39p Three for £1
- 115W/TO3 or 90W plastic
- 2N3819E 16p 2N3053 17p
- BFY50/51/52/53 all 18p
- 1A50Vrect 4p ea IN914 4p

Price each:-

- AC127/128 16p
- AC187/188 19p
- AD161/162 35p
- BC107/8/9 9p
- BC132/4/7 18p
- BC147/8/9 10p
- BC157/8/9 12p
- BC167/8/9 12p
- BC177/8/9 18p
- BC182/3/4 11p
- BC212/3/4 12p
- BCY70/1/2 15p
- BD131/2 39p
- BFY50/1/2 18p
- BFY53 17p
- BSX20 12p
- MJE2955 95p
- MJE3055 62p
- MPU131put 49p
- OA91 8p
- TIP29A 48p
- TIP30A 57p
- TIP31A 61p
- TIP32A 73p
- TIP41A 78p
- TIP42A 89p
- BZY88 400mW 2ENERS 9p
- BRIDGE RECT 1A 50V 20p
- GAS SENSOR £2
- GAS " KIT £5
- TIP2955 90p
- TIP3055 55p
- TIS43 UJT 25p
- IN4004 4p
- IN4001 6p
- IN4148/914 4p
- 2N697 13p
- 2N706/8 10p
- 2N2646 49p
- 2N2904/5 20p
- 2N2926 90p
- 2N3053 17p
- 2N3055 39p
- 2N3614 49p
- 2N3702/3 9p
- 2N3704/5 10p
- 2N3706/7 9p
- 2N3708/9 8p
- 2N3710/11 9p
- 2N3563/64 16p
- 2N3566/67 16p
- 2N3568 16p
- 2N3641/2 16p
- 2N3819E 16p
- 2N3832E 17p
- 2N3904/6 14p
- 2N4249 16p
- TAG 1/400 55P
- 1C107D1 SCR 4A/400V 55p
- SC146D TRIAC 10A 400V 75p

vero

NEW LOW PRICES!

- VERO PINSx36 25p.
- COPPER CLAD VEROBORARD 0.1"
- 21x5" 27p. 21x31" 24p. 31x31" 27p.
- 31x5" 29p. 31x17" £1.50
- DIL IC's: BOARDS 6x14" £1.50
- 24 way edge connector 60p
- 36way 90p. PLAIN 31"x17" £1
- FACE CUTTER 43p. FEC ETICANT

DALopen69p

- PRINTED CIRCUIT BOARD KIT £1.69
- COPPER BOARD 6x4" 40p.
- DESOLDER BRAID reel 59p
- HEATSINKS
- 5E/TO5 & 18E/TO18 5p ea.
- TV4 12p. TV3/TO3 16p. 4Y1/TO3 29p.

CAPACITORS

- 22pF to 0.1uF 4p ea. ELECTROLYTIC
- 25V 2/10/50/100uF 6p. 1000uF 20p
- PRESETS VERT: 5p. RESISTORS 5p 11p

POTS ABor EGIN

- ROTARY: 12p. SWITCH 13p. DUAL 38p.
- SLIDERS: SINGLE 26p. DOUBLE 48p.
- SWITCHES: SPST 18p. DPDT 25p.
- MINI 1": SPST 39p. PUSH 39p.
- BENCH POWER SUPPLY 3-12V £5.
- DIN PLUGS all 13p ea. Sockets 9p
- TRANSFORMERS 1A 6/12V £1.34
- BHA 0002 MODULE 15WATT AMP £5
- EAL000 4W AF MODULE £2.49
- 8W/12V FLUORESCENT LIGHT £3.


Oil sockets

- PROFESSIONAL GOLD PLATED & GREY NYLON.
- 8, 14 or 16 PIN
- ONLY 15p each.


CUSTOM CABINETS

331 High Street, Rochester, Kent. Tel: Medway (0634) 404199

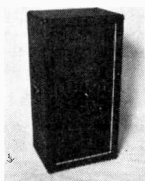
SPEAKER CABINETS IN KIT FORM REPRESENT **HUGE SAVINGS**



2' x 12" Cabinet

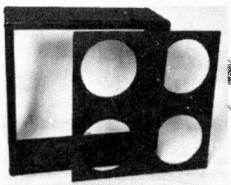

4' x 12" Cabinet

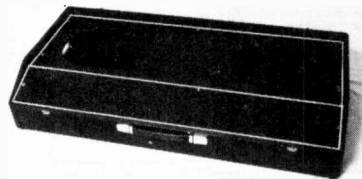

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!

Kits are available in all specifications and all the kits contain everything you need as follows:-


- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!

PRICE & TYPE LIST


Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£21.45	£13.75
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£26.95	£19.25
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£33.00	£23.65
1 x 18"	31" x 31" x 13" x 3/4"	£26.95	£19.25
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£23.10	£14.85

SPECIAL ANNOUNCEMENT

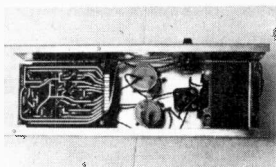Owing to difficulties in obtaining raw materials and labour we apologise for any inconvenience caused to our customers.



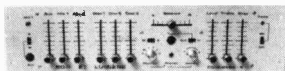- * 100w RMS slave amp for Disco
- * 100w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £42.00 complete




- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00



- ERC 100w power amplifier
- * Electrolytic capacitors and second generation ICs
- * Fully protected against short or open circuit
- * Less than 0.1% distortion at all powers
- * Rise time 4μs-stability-
Unconditional Price £66.50

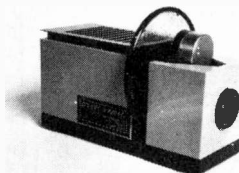ALL OUR PRICES INCLUDE VAT AND UK DELIVERY



Disco imp projector 150 watt tungsten
unbeatable price
Includes liquid wheel and postage
Normally sold between £24—£27.50

OUR PRICE £19.75

TRADE AND EXPORT ENQUIRIES WELCOME

12in LONG PERSISTENCE CRT. Full spec. Price £8.50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £25. P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBLULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £8.75. P. & P. 25p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £8.85 each. P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each. P. & P. 5p.

Large quantity of good quality components—**NO PASSING TRADE**—so we offer 3lb of **ELECTRONIC GOODIES** for £1.50. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic, 1 off 4 pole, 2 way, etc.). 50p. P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft. no tiny pieces. 50p. P. & P. 20p.

CAPACITOR PACK—50 brand new components, only 50p. P. & P. 20p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic, 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 10p.

PHOTOCELL equ. OCP71. 13p each. **MULLARD OCP70.** 10p each.

DELIVERED TO YOUR DOOR. 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. **FOR ONLY £4.**

MODERN TELEPHONES. Type 706. Two-tone grey. £3.75 each. Two-tone green £3.75 each. Black £3.75 each. P. & P. 35p.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 35p.

HANDSETS. Complete with 2 inserts and lead. 75p each. P. & P. 37p.

DIALS. ONLY 75p each. P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors.

etc.—No 2 boards the same. No short leaded transistor computer boards. £1.75, post paid.

BEEHIVE TRIMMER 330 pF. Brand new. Only 1-9 13p each. P. & P. 15p. 10-99 10p each. P. & P. 25p. 100-999 7p each. P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each. Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p. P. & P. 10p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—or build your own. Send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMead LTD

7/9 ARTHUR ROAD, READING, BERKS.
(near Tech. College) Tel. Reading 582605/65916



GIRO NO. 331 7056. Access accepted.
C.V.O. only. P. & P. 10p on orders below £5
Discount: £10-10%, £20-15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net
10E12 ¼W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net
25E12 ¼W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net
5E12 ½W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.80 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 33p, 0.068µF, 0.1µF, 41p, 0.15µF, 41p, 0.22µF, 51p, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 33p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 33p, 0.047µF, 0.068µF, 0.1µF, 41p, 0.15µF, 61p, 0.22µF, 81p, 0.33µF, 12p, 0.47µF, 14p.
160V, 0.01µF, 0.015µF, 0.022µF, 33p, 0.047µF, 0.068µF, 33p, 0.1µF, 41p, 0.15µF, 51p, 0.22µF, 51p, 0.33µF, 61p, 0.47µF, 81p, 0.68µF, 12p, 1µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 21p each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 50V
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 41p.

RESISTORS
CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%
W. Type Range 1-99 100-499 500-999 1000+ Size mm

CF 12-1M	1	0.75	0.60	0.55	2.4x7.5
CF 22-2M2	1	0.75	0.60	0.55	3.9x10.5
CF 22-1M	1	0.75	0.60	0.55	5.5x16
MF 10-2M7	2	1.54	1.32	1.1	3x7
MF 10-2M2	2	1.43	1.21	0.99	4.2x10.8
MF 10-10M	3	1.98	1.81	1.65	6.6x13
MF 10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (Price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS
MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each.

B. H. COMPONENT FACTORS LTD.

(P.E.), LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD,
BEDS. Tel.: Leighton Buzzard 2316 (Srd. Code 05253).
CATALOGUE No. 3, 20p.

Miniature	Mullard	Electrolytics	VEROBOARD	0.1	0.15
1.0µF 63V	61p	68µF 16V	21 x 5"	36p	36p
1.5µF 63V	61p	68µF 63V	21 x 3 1/2"	33p	25p
2.2µF 63V	61p	100µF 10V	32 x 5"	42p	46p
3.3µF 63V	61p	100µF 25V	32 x 3 1/2"	36p	36p
4.7µF 40V	61p	100µF 63V	21 x 1"	9p	9p
4.7µF 63V	61p	150µF 63V	21 x 5" (Plain)	—	19p
6.8µF 63V	61p	150µF 63V	21 x 3 1/2" (Plain)	—	16p
8.0µF 40V	61p	220µF 6.4V	5 x 3 1/2" (Plain)	—	29p
10µF 16V	61p	220µF 10V	Insertion tool	73p	73p
10µF 25V	61p	220µF 16V	Track Cutter	56p	56p
10µF 63V	61p	220µF 63V	Pins, Pkt. 25	22p	22p
15µF 16V	61p	330µF 16V			
15µF 63V	61p	330µF 63V			
22µF 40V	61p	470µF 6.4V			
22µF 25V	61p	470µF 10V			
33µF 10V	61p	680µF 16V			
33µF 16V	61p	680µF 16V			
33µF 40V	61p	1000µF 16V			
33µF 63V	61p	1000µF 25V			
47µF 10V	61p	1500µF 6.4V			
47µF 25V	61p	1500µF 16V			
47µF 63V	8p	2200µF 10V			
		3300µF 6.4V			

POTENTIOMETERS	DIODES	PLUGS	ELECTROLYTIC CAPACITORS
Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 16p Dual Gang 46p. Log single with switch 26p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.	IN4001 61p IN4002 71p IN4003 9p IN4004 9p IN4005 12p IN4006 14p IN914 1p IN916 7p BA106 10p OA5 42p OA47 9p OA81 11p OA200 8p	Din 2 Pin 12p 3 Pin 13p 5 Pin 180° 16p Sed. Jack 20p 2.5mm Jack 13p Phone 6p Din 2 Pin 10p 3 Pin 10p 5 Pin 180° 12p Sed. Jack 15p 2.5mm Jack 13p Phone 6p	(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/25, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/10, 8p, 2000/25, 30p, 2000/100, 93p, 2500/25, 38p, 2500/50, 61p, 5000/25, 65p, 5000/50, £1.08. HI-VOLT: 4/350, 14p, 8/350, 19p, 100/100, 20p, 16/350, 22p, 16/450, 23p, 32/350, 33p, 50/250, 20p, 100/250, 30p. METALLISED PAPER CAPACITORS 250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 71p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 71p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 34p.

PLEASE NOTE OUR NEW ADDRESS.
OUR NEW ELECTRONICS CENTRE
IS NOW OPEN

NEW KIT
5E12 ½W Metal Film.
5 each value 10 Ω-1M,
total of 305 **£3.25**

MULTIMETER U4323
22 Ranges plus AF/IF Oscillator 20,000 Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5 Ω—1M Ω in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 465KHz (A.M.) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.30 net P. & P. 25p.



U4323

MULTIMETER U4341
27 Ranges plus Transistor Tester 16,700 Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Idc—0.3—300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges. Accuracy—dc—2½%, ac—4% of F.S.D.
Hfe—10—350 in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.30 net P. & P. 30p.



U4341

MULTIMETER U4324
34 Ranges. High sensitivity. 20,000 Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Idc—0.3—3A in 5 ranges.
Resistance—25 Ω—5M Ω in 5 ranges.
Accuracy—dc and R—2½% of F.S.D. ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £9.95 net P. & P. 25p.



U4324

MULTIMETER U4313
33 Ranges. Knife edge with mirror scale. 20,000 Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ranges.
Idc—0.6—1500mA in 6 ranges.
Idc—0.6—1500mA in 6 ranges.
Resistance—1K Ω—1M Ω in 4 ranges. db scale—10 to +12db.
Accuracy—dc—1½%, ac—2½%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £13.40 net P. & P. 30p.



U4313

NEW CAPACITOR KITS
C280 Kit—PC Mounting polyester 250V. 5 of each value: 0.01 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47µF. £1.30 net.
C296 Kit—Tubular polyester, 400V. 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47µF. £1.30 net.
Ceramic Kit—square plaquette 50V. 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0.1µF. £1.30 net.
250V Paper Kit—Tubular metal case. 3 of each value: 0.05, 0.1, 0.25, 0.5, 1µF. 90p net.
500V Paper Kit—Tubular metal case. 3 of each value: 0.025, 0.05, 0.1, 0.25, 0.5µF. 90p net.
1000V Paper Kit—Tubular metal case. 3 of each value: 0.01, 0.025, 0.05, 0.1µF. £1.10 net.

S-DeC	£2.14	MULTIMETER U435
T-DeC	£3.92	32 ranges. High sensitivity. 20,000 Ω/Volt.
µDeC "A"	£4.30	Vdc—75mV—1000V in 8 ranges
µDeC "B"	£7.53	Vdc—2.5—1000V in 7 ranges
2 DeC	£4.72	Idc—0.001—3A in 6 ranges
		Idc—0.005—2.5A in 5 ranges
		Resistance—3-300K in 3 ranges
		Capacitance scales 0-0.5µF
		Accuracy—dc and R—2½% of F.S.D. ac and C—4% of F.S.D.
		Size—205 x 110 x 84mm.
		Complete with steel carrying case, test leads and battery.
		PRICE £9.45 net P. & P. 25p.



ANTEX
CCN240 £2.43
CN240 £2.01
X25 £2.01

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT
VARIABLE 0-260V All Types
SHROUDED TYPE
 200 watt (1 amp) £9.00
 0.5 KVA (2½ amp) (MAX) £10.00
 1 KVA (5 amp) (MAX) £14.70
 2 KVA (10 amp) (MAX) £28.10
 3 KVA (15 amp) (MAX) £31.25
 4 KVA (20 amp) (MAX) £72.50
 37.5 amp (MAX) £102.50
CARRIAGE AND PACKING EXTRA
OPEN TYPE 1 amp (panel mount) £9.00



L.T. TRANSFORMERS

0, 10, 17, 18 Volt at 10 amp. £7.90, Post 60p.
 0, 6, 12 Volt at 20 amp. £9, Post 60p.
 0, 12, 24 Volt at 10 amp. £9.20, Post 60p.
 0, 6, 12, 17, 18, 20 Volt at 20 amp. £10.40, Post 60p.
 Other types to order at short notice — Phone your enquiries.

AUTO TRANSFORMERS

Step up step down
 0-115/200/220/240 Volts.
 At 75 watt £2.64, Post 36p.
 150 watt £3.18, Post 36p.
 300 watt £6.20, Post 50p.
 500 watt £9.20, Post 65p.
 1000 watt £12.00, Post 80p.

300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2. Post 20p. (Total incl. VAT and Post £2.38).



VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp. contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.



COIN MECHANISM (Ex London Transport)

Unit containing selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 60p.

230/250 VOLT A.C. SOLENOID

Approximately 1½ lb pull. Size of feet 11" x 1 1/2". Price £1.00, Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb pull 1 inch travel. Two x approx. 1 lb pull 1 inch travel. 6 x approx. 4oz. pull 1 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50. Post 60p. **ABSOLUTE BARGAIN.**

'STC' 6" RED ALARM BELL

24/48 volt D.C. Brand New. Price £4. Post 50p.



'GENTS' 6" ALARM BELL

200/250V AC/DC. Brand New. Price £5. Post 60p.

INSULATION TESTERS

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.



600 WATT DIMMER SWITCH
 Easily fitted. Fully guaranteed by makers. Will control up to 600V of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.



All Mail Orders—Callers—Ample Parking
Dept. PE3, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT

Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30, Post 30p.

INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.

Approx. 1/2 output of Hy-Light. Price £14.00, Post 50p.

HY-LIGHT STROBE MK III

For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £14. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light. ONLY £22. Post 75p.

ROBUST, FULLY VENTILATED METAL CASE, For Hy-Light Kit including reflector £5.75.

Post 25p.

Super Hy-Light case including reflector £8. Post 60p.

7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 55p. Post 15p.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £20.50. Post 50p.



6 INCH COLOUR WHEEL

As used for Disco lighting effects, etc. Price £4.50. Post 30p.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast is essential. Price of matched ballast and bulb £16. Post £1. Spare bulb £7. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt. Price £5.50, Post 30p. (4ft to Personal callers only). 2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin. MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube. £1.70. Post 25p. (9in and 12in measures approx.)

U.D.I. SINGLE CHANNEL

750 WATT MANUAL/AUTO DIMMER

750W Solid State Fader, with three functions. Manual fade: Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three-position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15. Post 30p.

POWER RHEOSTATS !!!

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/150/500/1k/ohm. £1.70. Post 10p.
 50 WATT 1/5/10/25/50/100/250/500/1.5k/ohm £2.10. Post 10p.
 100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/ohm £3.30. Post 15p.
 Black Silver, Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia. brass bush. Ideal for above 22p each.

TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS 10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146E 10 amp, 500 PIV, £1.00. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.



All prices are subject to 8% VAT. (8p in the £)

To all orders add 8% VAT to total value of goods including carriage packaging.

SERVICE TRADING CO.

LED READOUTS

7 series, L/H d.p. one-third high character. 14 pin D.I.L. Available in RED or GREEN. Price £1.65. Post 10p. 4 for £6. Post paid.



RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-8	2 c/o	70p
Working	58	5-9	6 c/o	80p
d.c. volts	185	8-12	6M	60p*
Col. 3	308	9-18	2 c/o	70p
Contracts	308	9-14	4 c/o	75p*
Col. (4)	430	15-24	4 c/o	80p
Price	700	16-24	4M 2B	60p*
	700	16-24	4 c/o	80p*
HD =	2,500	31-43	2 c/o HD	60p*
Heavy duty	2,500	36-45	6M	60p*
	9,000	40-70	2 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 35p. Post 10p.

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 10p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 10p.

24 VOLT D.C. 3 c/o 75p. Post 10p.

2 HD c/o 700 ohm coil. 75p. Post 10p.

4 c/o 300 ohm coil. 85p. Post 10p.

100 VOLT A.C. 2 c/o sealed type, octal base

75p. Post 10p.

ENCLOSED TYPE RELAYS

24 VOLT A.C. 3 h.d. c/o. 65p. Post 10p.

24 VOLT A.C. Mfg. by ITT. 2 h.d. c/o contacts.

55p. Post 10p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C.

10 amp h.d. c/o contacts. Price 75p. Post 10p.

Octal plug in base 15p extra.

230/240 VOLT A.C. RELAY, Mfg. by Arrow 2 h.d.

15 amp c/o contacts. Amp connectors. Price £1.

Post 10p.

220/240 VOLT A.C. RELAY

3 c/o 5 amp contacts. Sealed. £1.25. Post 10p.

11-pin base 15p extra.

CLARE-ELLIOTT TYPE RP7641 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o.

70p post paid.

110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.

Many others from stock—phone for details.

VERY SPECIAL OFFER

MINIATURE ROLLER MICRO

SWITCH. 5 amp. c/o contacts.

NEW. Price 10 for £1.50. Post 10p.

(Min. order 10). As above less roller/

lever) 20 for £2. Post 10p. (Min. order 20).

Qitto press to make, 20 for £1.50. Post 10p.

Qitto press to break, 20 for £1.50. Post 10p.



230/240 VOLT A.C. MINIATURE MOTOR.

20 R.P.M. Price £1. Post 10p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in.

Reversible 1/70th h.p. cycle 0-38

amp. (Type 2) 28 r.p.m. torque 20

lb. in Reversible 1/80th h.p. cycle 0-28 amp.

The above two precision made U.S.A. motors are

offered in 'as new' condition. Input voltage of motor

115v A.C. Supplied complete with transformer for

230/240V A.C. input.

Price, either type £6.25. Post 50p or less trans-

former £3.75. Post 40p.



'FRACMO' 240 VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

33 r.p.m. 30 lb. ins. Reversible.

Fitted with mounting feet.

Brand New. £14. Post 60p. (Total price incl. VAT

£15.77).



230V FAN ASSEMBLY

Continuously rated, removable

aluminium blades. Price £1.

Post 20p.



PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd.

Heavy Duty continuously rated,

smooth running. 230/240V a.c.

motor. Size: 16 x 14cm (case

only). OAL 15cm. Aperture

6 x 6cm. £6.50. Post 50p.



230/240 VOLT A.C. EXTRACTOR FAN KIT

Comprising of impeller, continuously

rated motor, motor housing and fixings

as illustrated. Price £1.75. Post 25p.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET

LONDON WC2H 7JJ

Phone 01-437 0576

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can be applied to give d.c. to winding for a maximum holding torque of 300oz/in with 35V at 0.35A through winding. For a.c. (synchronous) operation at 120V, 50Hz. Speed 60r.p.m. at 60Hz, 72r.p.m. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia. 4in. body length 4in. spindle length 2 1/2in x 1/4in dia. Weight 6 1/2lb. BRAND NEW in maker's packing. Offered at less than half maker's price.

OUR PRICE ONLY £15. P. & P. £1

MAGNETIC DEVICES SOLENOID

240V a.c. 50 P.C. rated 18lb pull, 1 1/2in travel push or pull. Shackle both ends, length overall 4in plus 3in travel arm x 2 1/2in x 3 1/2in high. Brand new £5.25 plus 60p P. & P. or ex-equipment £3 plus 60p P. & P.

CARTER ELECTRIC

Similar to above with alloy gear case, 60r.p.m. This item is ex-equipment but perfect. £1.95. P. & P. 30p.

SHADED POLE MAINS MOTOR

A quality shaded pole motor. Open frame, 3in high x 2 1/2in x 2in. Spindle 1in x 1/4in, 1.420r.p.m. £1.95. P. & P. 20p.

"LABGEAR ELIMINAC"

P.S.U. 200-250V, 40/60Hz. Alternative outputs fully variable (variac incorporated). Output 1, 12V at 5A d.c. fully smoothed. Output 2, 12V at 8A d.c. with ripple content. Output 3, 20V at 10A a.c. 2 1/2in x 2 1/2in flush 0.20V d.c. m/c motor. In attractive grey hammer finish case. In maker's carton. £27.50. Carr. & Pkg. £1.50.

SPECIAL OFFER LIGHT DEPENDENT RESISTORS

Matched pairs Pioneer Type 174 similar to OPR 12. Resistance 1kΩ to 4kΩ. Dia. 1/2in with 1/2in flanges. £1.50 for two pair (minimum) 10 or more pairs 50p. per pair incl. P. & P.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1in through hinged elbow. Bracket incorporates 2 fixing screws. Length of arm, 2 1/2in 240V a.c. Pull at coil is approximately 11lb. £1. FREE P. & P. Special quote for quantities.



SOLENOIDS by WESTOOL

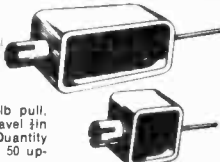240 a.c. type, MM6 3lb pull, 2 1/2in x 1 1/2in x 1 1/2in. Travel 1in 90p each. P. & P. 10p. 240 a.c. type MM4, 2lb pull, 1 1/2in x 1 1/2in x 1 1/2in. Travel 1in 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 a.c. 28r.p.m. NEW HIGH TORQUE, approx. overall size: 3 1/2in x 3 1/2in x 2 1/2in = spindle 1/2in dia. as illustrated. £2.70 plus 30p P. & P. 110r.p.m. with pressed steel gear case (similar to above but slightly smaller). £2.70 plus 30p P. & P.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3A at 120V, 1 1/4A at 240V. Size: (approx.) 1 1/2in long x 1/2in dia. Ideal for burglar alarms, security systems, etc. and wherever non-mechanical switching is required. 10 for £2.10; P. & P. 15p. 50 for £8.80; 100 for £15.50. FREE P. & P. over 10.




AMPEX 7.5V D.C. MOTOR

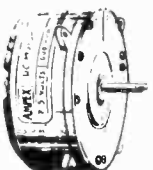

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500mA. Draws 60mA on run. 600r.p.m. ± speed adjustment. Internal AF/RF suppression. 1/2in dia. x 1 1/2in spindle motor 3in dia. x 1 1/2in. Original cost £16.50. OUR PRICE £4.25. P. & P. 25p. Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

FAN/BLOWER

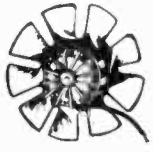

Precision built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60mA on run. Size: 5 1/2in dia. x 2 1/2in deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3 plus 40p P. & P.

ALL PRICES INCLUDE VAT

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH

COMPONENTS LTD.

315/317 EDGWARE ROAD
LONDON, W.2

Tel: 01-723 5667, 01-402 5580

★ ELECTRONIC PIANO KIT ★ SYNTHESISER KIT ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145.29. ★ Console organ with 5 octave keyboard, £250.93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £680. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £960. ★ W/W Sound Synthesiser Kit, £130. ★ W/W Touch Sensitive Electronic Piano, £100.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

Elvins Electronic Musical Instruments

12 Brett Road, Hackney, London E8 1JP (Tel. 01-986 8455);
8 Putney Bridge Road, London SW18 1HU (Tel. 01-870 4949);
40a/42a Dalston Lane, Dalston Junction, London E8 (Tel 01-249 5624).

Business hours: Open 10 a.m. to 7 p.m. Monday to Saturday. Closed all day Thursday. Open 10 a.m. to 1 p.m. Sunday.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB35, P.O. BOX 156, JERSEY

NAME: _____

ADDRESS: _____

BLOCK CAPS please

Marshall's

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Everything you need is in our
New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Popular Semiconductors

2N456	0-80	2N2907	0-22	2N4061	0-11
2N456A	0-85	2N2907A	0-24	2N4062	0-11
2N457A	1-20	2N2924	0-14	2N4126	0-20
2N490	3-16	2N2925	0-17	2N4289	0-34
2N491	3-58	2N2926		2N4919	0-84
2N492	3-99	Green	0-12	2N4920	0-99
2N493	4-20	Yellow	0-11	2N4921	0-73
2N696	0-22	Orange	0-11	2N4922	0-84
2N697	0-16	2N3053	0-25	2N4923	0-83
2N698	0-40	2N3054	0-60	2N5172	0-12
2N699	0-45	2N3055	0-75	2N5174	0-22
2N706	0-14	2N3900	0-26	2N5175	0-26
2N706A	0-16	2N3991	0-23	2N5176	0-32
2N708	0-17	2N3991A	0-29	2N5190	0-92
2N709	0-42	2N3992	0-13	2N5191	0-95
2N711	0-50	2N3993	0-13	2N5192	1-24
2N718	0-20	2N3994	0-17	2N5193	1-46
2N718A	0-28	2N3402	0-18	2N5245	0-43
2N720	0-50	2N3403	0-19	2N5457	0-49
2N721	0-55	2N3440	0-59	2N5458	0-46
2N914	0-22	2N3441	0-59	2N5459	0-49
2N916	0-28	2N3442	1-59	40361	0-48
2N918	0-32	2N3541	0-17	40362	0-51
2N929	0-30	2N3415	0-21	40363	0-88
2N1302	0-19	2N3416	0-34	40389	0-46
2N1303	0-19	2N3417	0-24	40394	0-56
2N1304	0-24	2N3638	0-15	40395	0-65
2N1305	0-24	2N3638A	0-15	40406	0-44
2N1306	0-31	2N3639	0-27	40407	0-16
2N1307	0-22	2N3641	0-17	40408	0-50
2N1308	0-40	2N3702	0-12	40409	0-52
2N1309	0-36	2N3703	0-13	40410	0-52
2N1671	1-44	2N3704	0-14	40411	2-00
2N1671A	1-54	2N3705	0-12	40414	3-55
2N1671B	1-72	2N3706	0-12	40430	0-85
2N1671C	4-32	2N3707	0-13	40583	0-23
2N1711	0-45	2N3708	0-10	40601	0-67
2N1907	5-50	2N3709	0-11	40602	0-46
2N2102	0-50	2N3710	0-12	40603	0-53
2N2147	0-78	2N3711	0-11	40604	0-56
2N2148	0-94	2N3712	0-96	40636	1-10
2N2160	0-90	2N3713	1-20	40669	1-06
2N2192	0-40	2N3714	1-33	40673	0-73
2N2192A	0-40	2N3715	1-30	40673	0-73
2N2193	0-58	2N3716	1-80	AC107	0-51
2N2193A	0-61	2N3717	2-20	AC113	0-16
2N2194	0-73	2N3718	1-20	AC117	0-20
2N2194A	0-30	2N3719	3-20	AC126	0-20
2N2218A	0-22	2N3720	2-06	AC127	0-20
2N2219	0-24	2N3721	2-40	AC128	0-20
2N2219A	0-26	2N3721	2-35	AC151V	0-25
2N2220	0-25	2N3722	2-69	AC152V	0-17
2N2221	0-18	2N3723	2-40	AC153	0-25
2N2221A	0-21	2N3724	0-37	AC153K	0-30
2N2222	0-20	2N3820	0-64	AC154	0-20
2N2222A	0-25	2N3821	0-78	AC154K	0-23
2N2368	0-25	2N3900	0-28	AC167K	0-33
2N2369	0-37	2N3901	0-32	AC188K	0-34
2N2369A	0-41	2N3903	0-24	AC188	0-24
2N2646	0-55	2N3904	0-27	AC197	0-27
2N2647	1-12	2N3905	0-24	AC20	0-22
2N2904	0-24	2N3906	0-27	AC21	0-26
2N2904A	0-24	2N3906	0-27	AC21	0-26
2N2905	0-24	2N4037	0-63	AC28	0-20
2N2905A	0-26	2N4038	0-42	AC30	0-58
2N2906	0-19	2N4059	0-09	AD142	0-59
2N2906A	0-21	2N4060	0-11	AD143	0-60
				AD149	1-20

AD150	1-15	BC171	0-13	BD135	0-43
AD161	0-50	BC172	0-11	BD136	0-55
AD162	0-50	BC182	0-12	BD137	0-63
AD161A	1-20	BY182L	0-12	BD138	0-71
AD162A	1-20	BC183	0-12	BD139	0-87
AD161B	1-20	BC184	0-13	BD140	0-25
AD162B	0-25	BC184L	0-13	BF115	0-25
AD161C	0-25	BC186	0-25	BF116	0-25
AD162C	0-25	BC186	0-25	BF117	0-43
AD161D	0-55	BC187	0-27	BF119	0-58
AD162D	0-55	BC187	0-27	BF121	0-25
AD161E	0-30	BC207	0-12	BF123	0-27
AD162E	0-30	BC208	0-11	BF125	0-25
AD161F	0-28	BC212K	0-16	BF126	0-25
AD162F	0-28	BC212L	0-16	BF152	0-21
AD161G	0-25	BC214L	0-16	BF154	0-23
AD162G	0-25	BC214L	0-16	BF158	0-23
AD161H	0-25	BC237	0-13	BF159	0-27
AD162H	0-25	BC238	0-13	BF160	0-23
AD161I	0-55	BC239	0-13	BF161	0-42
AD162I	0-55	BC239	0-13	BF163	0-32
AD161J	0-58	BC252	0-18	BF166	0-32
AD162J	0-58	BC252	0-18	BF167	0-24
AD161K	0-58	BC253	0-23	BF173	0-21
AD162K	0-58	BC257	0-14	BF177	0-29
AD161L	0-58	BC258	0-13	BF178	0-35
AD162L	0-58	BC258	0-13	BF179	0-43
AD161M	0-72	BC259	0-14	BF180	0-35
AD162M	0-72	BC259	0-14	BF181	0-34
AD161N	0-54	BC261	0-20	BF182	0-40
AD162N	0-54	BC261	0-20	BF183	0-40
AD161O	0-54	BC263	0-23	BF184	0-30
AD162O	0-54	BC263	0-23	BF185	0-30
AD161P	0-70	BC300	0-36	BF194	0-12
AD162P	0-70	BC301	0-34	BF195	0-13
BC107	0-16	BC301	0-34	BF196	0-15
BC108	0-15	BC302	0-29	BF197	0-18
BC109	0-19	BC303	0-54	BF198	0-18
BC110	0-13	BC307	0-11	BF199	0-18
BC111	0-13	BC307A	0-10	BF200A	0-40
BC115	0-17	BC308	0-12	BF225J	0-19
BC116	0-16	BC308A	0-09	BF237	0-22
BC116A	0-18	BC308A	0-12	BF238	0-22
BC117	0-21	BC308B	0-09	BF247	0-48
BC118	0-11	BC309	0-10	BF248	0-31
BC119	0-29	BC309A	0-10	BF249	0-31
BC121	0-23	BC309B	0-10	BF254	0-16
BC122	0-23	BC327	0-21	BF255	0-17
BC125	0-25	BC237	0-19	BF256	0-59
BC132	0-30	BC337	0-19	BF257	0-59
BC134	0-13	BC338	0-19	BF258	0-59
BC135	0-13	BC339	0-19	BF259	0-55
BC136	0-17	BC340	0-64	BF261A	2-30
BC137	0-17	BC341	0-15	BF262	0-92
BC138	0-24	BC342	0-15	BF263	0-92
BC139	0-24	BC343	0-45	BF264	0-92
BC140	0-34	BC344	0-45	BF265	0-92
BC141	0-29	BC345	0-21	BF266	0-92
BC142	0-23	BC346	0-21	BF267	0-92
BC143	0-25	BC347	0-12	BF268	0-92
BC144	0-25	BC348	0-12	BF269	0-92
BC147	0-12	BC358	0-28	BF270	0-92
BC148	0-13	BC359	0-22	BF271	0-92
BC149	0-12	BC370	0-17	BF272	0-92
BC150	0-18	BC371	0-27	BF273	0-92
BC151	0-18	BC372	0-17	BF274	0-92
BC154	0-18	BC373	0-34	BF275	0-92
BC155	0-18	BC374	0-21	BF276	0-92
BC158	0-13	BC378	0-22	BF277	0-92
BC159	0-14	BC387	0-47	BF278	0-92
BC160	0-37	BD115	1-05	BF279	0-92
BC167B	0-13	BD116	1-06	BF280	0-92
BC168B	0-13	BD121	1-05	BF281	0-92
BC169B	0-13	BD123	0-82	BF282	0-92
BC169B	0-13	BD124	0-67	BF283	0-92
BC169C	0-13	BD131	0-40	BF284	0-92
BC170A	0-11	BD132	0-50	BF285	0-92

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

TYPE B 3-BANK UNIT

Has two brackets to accept P/C Board. Transformers. Also has holes in ends for Potentiometers, Jack Socket, Cable, etc. Ideal for making Sound to Light and Strobes. Base Cover included. Less Lamps, only

£6.50

inc. VAT, P. & P. 40p

SOUND TO LIGHT

Three channel, using Type B unit. Ideal for small disco's and home entertainment. Complete with Lamps. Ready wired.

£25

inc. VAT, P. & P. 40p

STROBE UNIT

Using Type B unit. Adjustable frequency. Single knob control. Complete with Lamps, just plug into mains—that's it.

£25

complete, inc. VAT, P. & P. 40p

100 WATT SPOT LAMPS

Red, Pink, Green, Yellow, Blue, Violet, Clear, Only

80p

each Minimum 3 Lamps = £2.40 inc. VAT, P. & P. 25p pf

TRAFALGAR SUPPLIES

Dept H.T. · Standish Street · Burnley · Lancs



ONLY
£1.50
inc. VAT
Less Lamp
Plus 25p P. & P.
each

SCOOP!! CALCULATOR I.C.



XE 202 FULL 4 FUNCTION + CONSTANT CALCULATOR CHIP **£2.95** +VAT

For only £2.95 you get a brand new, tested full four function calculator chip, with the following features:

- 8 DIGIT DISPLAY CAPABILITY
- FULLY FLOATING DECIMAL POINT
- ALGEBRAIC LOGIC DATA ENTRY
- KEYED CONSTANT ON ALL FOUR FUNCTIONS
- TRAILING ZERO SUPPRESSION
- DIRECT SEGMENT DRIVE

ENORMOUS EXPONENT RANGE: 10^{-20} to 10^{+79}

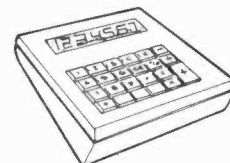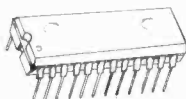SINGLE 'STROBE' LINE FOR SIMPLE KEYBOARD CONSTRUCTION




THURLBY

ELECTRONICS

By the addition of a display and a few discrete components you can construct a powerful machine capable of handling advanced calculations. The XE202 is supplied with full circuit diagrams and wiring details covering the use of different types of displays and keyboards (including a low cost single digit display and rapidly constructed stylus keyboard), and with instructions for realising the full computing powers of this chip to calculate advanced functions such as roots, sines, logs, etc.

ALSO AVAILABLE AT SPECIAL PRICES FOR PURCHASERS OF THE XE202 CHIP:

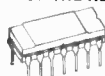Specially designed display driving interface chip at **£0.75**



8 digit magnified LED display at **£3.95**



Full money back guarantee.
Cash with order. Postage and packing 20p per order.
Please add 8% VAT to total order value.

TO
THURLBY ELECTRONICS,
Church Farm House,
Church End,
Over,
Cams. CB4 5NH

PLEASE SUPPLY _____

FOR WHICH I ENCLOSE CASH/CHEQUE/PO FOR

£ _____ INCLUDING VAT & POSTAGE


NAME _____

ADDRESS _____

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO & MONO

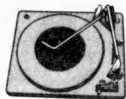Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in.



Above motor board 3 1/2 in. Below motor board 2 1/2 in. with STEREO and MONO XTAL £7.95 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Rexine covered. Large front grille. Lift-up Lid. Chrome fittings. Approx. size 17 1/2 x 15 1/2 x 7 1/2 in. Few only in red and black rexine. £4.50 Post 50p Motor board cut for Garrard deck

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono £4.95 compatible cartridge. Post 25p



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop. Stereo/mono cartridge. Baseplate. Size 11 1/2 x 8 1/2 in. Turntable. Size 7 in diameter. A.C. mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

£5.50 Post 25p

SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Size 12 1/2 x 14 1/2 x 7 1/2 in. £6.50 Post 45p

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 3 1/2 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls.



Attractive Teak finish Weight 13 lb.

Bargain Price £25 85p Carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES

Single pole two-way surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4.50. Brand new and fully guaranteed. OUR PRICE £2.20 Post 25p



BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2 1/2 in sides 6 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 90p; 16 x 10 in 90p; 18 x 11 in 90p; 20 x 12 in 90p; 1430 x 717 in 9

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£5-75 THE PAIR, Post 45p. (Available separately. Woofer £4-25; Tweeter £1-00)

Comprising a fine example of a Woofer 10½ x 6½ in with a massive Ceramic Magnet, 440z Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3½ in square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps
SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN DESIGN. TEAK WOOD FINISH.



£10-50
Post 75p

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5 in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price **£2-95** Post 25p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

10 in round **£4-50**.

£3-75

TEAK VENEER HI-FI SPEAKER CABINETS


Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in
For 12 in. dia. or **£10-50** Post 75p

MODEL "B". 16 x 10 x 7 in
For 13 x 8 in. or **£6-60** Post 45p

MODEL "4C". 30 x 20 x 12 in.
Refr. cabinet will accept 1-12 in. bass unit, 1-5 in. mid range, 1-3 in. tweeter. Teak finish. Grooved front.

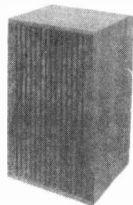£18-50 Carr. 22
LOUDSPEAKER CABINET
WADDING 18 in wide, 20p ft.



DECCA DOME TWEETER


3½ in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3-30**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated.

£4-50

STEREO VERSION OF ABOVE £5-95.
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated.

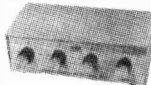THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£3-75** Post 20p



WAFER HEATING ELEMENTS

THIN OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse factory (available in manufacturing quantities). Approx size 10½ x 9½ x ¼ in. Operating voltage 200/250V a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Connector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR £1-50)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £8-50



30-14,500 c/s, 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10-95**

please state 3 or 8 or 15 ohms.

BAKER

"BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25"

12 in 25 watt
3, 8 or 15 ohms.

£7-75

GROUP "35"

12 in 35 watt
3, 8 or 15 ohms.

£8-50

GROUP "50"

15 in. 50 watt
8 or 15 ohms.

£17-80

50 watt 12 in VERSION **£12-95**

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E.



£49 Carr. £1-00

NEW MODEL MAJOR 50 WATT

4 inputs, 2 way mixing, £39-95. Carr. £1. Ideal disco amp

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. **£69**

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered ½ in thick wood cabinet. Size 18½ in x 18½ in x 8½ in. Weight 28 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6½ in Woofer. £7-50. Carr. 85p. Rosewood Version £8-50. Carr. 85p. Baffle could be cut for larger speaker.



SPECIAL OFFER 95p. Post 25p.
100 Ohm 20 watt Rheostat 2½ in dia. Ceramic Former.
Screw Terminals ½ in. dia. spindle.

R.C.S. STEREO DECODER

British made. Ready aligned and tested. Complete with instructions. Size 3 in x 2 in. **£4-95**

WEYRAD COILS

P50/2CC	40p	RA2W	85p
P50/1AC	80p	OPT1	85p
P50/3CC	40p	LFDT4	65p
PCA1	85p	Twin gang	£1-10



DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle 1½ x 7/32 in, size 3½ in x 3 in. As illustrated. 240V a.c. mains. **£2-25** Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2½ x 2½ x 2½ in. **£1-00** Post 25p

BAKER HI-FI SPEAKERS

HIGH QUALITY—BRITISH MADE

REAGENT

12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000 gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£7-75

DE-LUXE Mk II

12 in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000 gauss
Useful response 25-16,000cps
8 or 15 ohm models.

£9-75

SUPERB

12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohm models.

£13-80

AUDITORIUM

12 in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs, Ideal for Hi-Fi and Discoteques.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-18,000cps
8 or 15 ohm models.

£12-95

AUDITORIUM

15 in 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discoteques, Electronic instruments and the home.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohm models.

£17-80

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 65p.

CUSTOMERS FREE CAR PARK

OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.

11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

Spec: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing
Bracket and 5m plus 25p
Control Switch. £7.50 P & P.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

MINIATURE RELAYS

Brand new range of British made relays, size: 1 1/2in x 1in x 3/4in. All two changeovers with 250V 1.5A contacts and suitable for fitting on 0.1m veroboard.
Type Volts Current Ohms
27/1A 12V 17mA 700 Ω
21/1A 12V 28mA 430 Ω 1/30
12/1A 6V 33mA 185 each
200/250V Mains Relay
Heavy duty contacts 2,500 ohm coil. All new and unused D.P.D.T. mains relays 50p, Carr. free. Special quantity £40 per 100 off.

MIDGET MAINS TRANSFORMER

Varnish Impregnated
Size 40mm x 36mm x 31mm
PRI 240V
Sec 3-0-3 100mA
Sec 6-0-6 100mA
Sec 9-0-9 100mA
Sec 12-0-12 100mA
Sec 20-0-20 100mA
£1.23 10p P & P.

CRESCENT BUBBLE LIGHT SHOW

This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 16ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, £15; Wheel, £5; Total £20. Plus 75p carr.

7in x 4in LOUDSPEAKER
A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 9012 to 12KHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. eq. wtd. 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp. Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY
Is supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £25, carr. 75p. Send B.A.E. for further details on this or our ready built amplifiers.

12-0-12V 500MA

240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £12.20.

18V 500MA

240V primary. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price £1 each.

BARGAIN BOX

Loud buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or Morse code practise buzzer. Approx. size: 2 1/2in x 6 1/2in x 1 1/2in. OUR PRICE 50p

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 45mm 51p; 1006, 150mm x 75mm x 47mm 66p; 1007, 184mm x 124mm x 60mm 96p; 1021, 106mm x 74mm x 45mm (sloping front) 50p.

BARGAIN BOARDS

Components galore for the experimenter. Ex-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards £1.

2in. PANEL METERS

Size 59mm x 46mm

0-50 μ A—ME6	0-100mA—ME13
0-100 μ A—ME7	0-500mA—ME14
0-500 μ A—ME8	0-1A—ME15
0-1mA—ME9	0-50V a.c.—ME16
0-6mA—ME10	0-300V a.c.—ME17
0-10mA—ME11	5 meter—ME18
0-50mA—ME12	V.U. meter—ME19

£3 each. 10p P & P.

POWER PACKS

PP1 Switched 3-6-7-9V 400mA Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, £5-25 each.

PP2 Switched 6-7-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, £5-25 each.

PP3 Car converter. From 12V Pos. or Neg. to 6-7-9V. Easy to fit and transistor regulated, £3-90.

3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)

£18-50 plus 38p P & P.

MINI LOUDSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P & P. on each L.S.

U.K. CARRIAGE

15p UNLESS
OTHERWISE STATED

VAT

8% VAT TO BE ADDED
TO ALL ORDERS

SEND 20p FOR A

CRESCENT
CATALOGUE

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
07	20	1 8	7-0 x 6-0 x 6-0	2-55 38
149	60	3 12	9-9 x 7-7 x 8-6	3-98 45
150	100	5 8	9-9 x 8-9 x 8-6	4-45 45
151	200	8 0	12-1 x 9-3 x 10-2	7-39 53
152	250	13 12	12-1 x 11-8 x 10-2	8-93 73
153	350	15 0	14-0 x 10-8 x 11-8	10-80 73
154	500	19 8	14-0 x 13-4 x 11-8	12-41 91
155	750	29 0	17-2 x 14-0 x 14-0	18-65 *
156	1000	38 0	17-2 x 16-6 x 14-0	26-50 *
157	1500	46 0	21-6 x 13-4 x 18-1	30-23 *
158	2000	60 0	21-6 x 15-3 x 18-1	33-70 *

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P
113	20	1 0	5-8 x 5-1 x 4-5	0-115-210-240	1-52 30
64	75	2 4	7-0 x 6-7 x 6-1	0-115-210-240	2-64 38
66	150	3 4	8-9 x 7-7 x 7-7	0-115-210-240-240	3-25 45
66	300	6 4	9-9 x 9-6 x 8-6	"	5-29 53
67	500	12 8	12-1 x 11-2 x 10-2	"	8-02 67
84	1000	19 8	14-0 x 13-4 x 14-3	"	12-44 91
93	1500	30 4	14-0 x 15-9 x 14-3	"	16-65 *
95	2000	32 0	17-2 x 16-6 x 14-0	"	22-00 *
73	3000	40 0	21-6 x 13-4 x 18-1	"	31-90 *

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets, 20VA £2-85, P & P 38p. 500VA £9-50, P & P 80p. 1000VA £15-92, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Windings	P & P
111	0.5	0.25	4-8 x 2-9 x 3-5	0-12V at 0-25A x 2	1-24 33
213	1-0	0-5	6-1 x 5-8 x 4-8	0-12V at 0-5A x 2	1-58 30
71	2	1	7-0 x 6-4 x 6-1	0-12V at 1A x 2	2-09 38
18	4	2	8-3 x 7-7 x 7-0	0-12V at 2A x 2	2-60 38
70	6	3	8-8 x 8-0 x 7-7	0-12V at 3A x 2	3-75 45
108	8	4	9-9 x 8-9 x 8-6	0-12V at 4A x 2	4-15 45
72	10	5	9-9 x 9-6 x 8-6	0-12V at 5A x 2	4-67 53
116	12	6	12-1 x 8-8 x 10-2	0-12V at 6A x 2	5-02 53
17	16	8	12-1 x 9-9 x 10-2	0-12V at 8A x 2	6-62 60
115	20	10	14-0 x 9-6 x 11-8	0-12V at 10A x 2	9-45 73
187	30	15	14-0 x 12-1 x 11-8	0-12V at 15A x 2	12-29 85
226	60	30	17-2 x 15-3 x 14-0	0-12V at 30A x 2	15-30 *

30 VOLT RANGE

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0-5	1 4	6-1 x 5-8 x 4-8	0-12-15-20-24-30V	1-65 30
79	1-0	2 4	7-0 x 6-7 x 6-1	"	2-18 38
3	2-0	3 4	8-9 x 7-7 x 7-7	"	3-18 38
20	3-0	4 8	9-9 x 8-3 x 8-6	"	4-12 45
21	4-0	6 4	9-9 x 9-6 x 8-6	"	4-67 53
5	5-0	8 12	12-1 x 8-8 x 10-2	"	5-02 53
117	6-0	8 0	12-1 x 9-3 x 10-2	"	6-51 60
88	8-0	12 0	12-1 x 11-8 x 10-2	"	9-00 67
89	10-0	13 12	14-0 x 12-7 x 11-8	"	8-97 73

50 VOLT RANGE

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0-5	1 12	7-0 x 6-4 x 6-1	0-19-25-33-40-50V	2-35 30
103	1-0	2 12	8-3 x 7-4 x 7-0	"	3-08 38
104	2-0	5 8	7-9 x 8-9 x 8-6	"	4-26 45
105	3-0	6 12	9-9 x 10-2 x 8-6	"	5-28 53
106	4-0	10 0	12-1 x 10-5 x 10-2	"	6-91 67
107	6-0	12 0	14-0 x 10-2 x 11-8	"	11-00 67
118	8-0	18 0	14-0 x 12-7 x 11-8	"	11-80 85
119	10-0	25 0	17-2 x 12-7 x 14-0	"	15-45 *

60 VOLT RANGE

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0-5	2 4	7-0 x 6-7 x 6-1	0-24-30-40-48-60V	2-12 38
126	1-0	3 4	8-9 x 7-7 x 7-7	"	3-10 38
127	2-0	6 4	9-9 x 9-6 x 8-6	"	4-62 45
125	3-0	8 12	12-1 x 9-9 x 10-2	"	6-84 60
123	4-0	13 12	12-1 x 11-8 x 10-2	"	7-96 67
40	5-0	12 00	14-0 x 10-2 x 11-8	"	8-87 73
120	6-0	15 8	14-0 x 12-1 x 11-8	"	10-27 85
121	8-0	25 00	14-0 x 14-7 x 11-8	"	13-64 *
122	10-0	25 0	17-2 x 12-7 x 14-0	"	15-93 *
189	12-0	29 00	17-2 x 14-0 x 14-0	"	18-16 *

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P
238	200	2	2-8 x 2-6 x 2-0	3-0-3	1-40 10
212	1A, 1A	1	6-1 x 5-8 x 4-8	0-6, 0-6	1-67 30
13	100	4	3-9 x 2-6 x 2-9	9-0-9	1-28 13
235	330, 330	4	4-8 x 2-9 x 3-5	0-9, 0-9	1-42 19
207	500, 500	1 00	6-1 x 5-4 x 4-8	0-8-9, 0-8-9	1-75 30
208	1A, 1A	1 12	7-0 x 6-4 x 6-1	0-8-9, 0-8-9	3-00 38
236	200, 200	4	4-8 x 2-9 x 3-5	0-15, 0-15	1-30 19
214	300, 300	1	6-1 x 5-8 x 4-8	0-20, 0-20	1-76 30
221	700 (d.c.)	1 8	7-0 x 6-1 x 6-1	20-12, 0-12-20	1-98 38
206	1A, 1A	2 12	8-3 x 7-7 x 7-0	0-15-20, 0-15-20	3-15 38
203	500, 500	2	4-8 x 7-0 x 7-0	0-15-27, 0-15-27	2-73 38
204	1A, 1A	3	8-9 x 7-7 x 7-7	0-15-27, 0-15-27	3-50 38

*Carriage via B.R.S.

PLEASE ADD 8% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST

CHROMASONIC electronics

Dept. 2. 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

RECTIFIERS

V	1A	3A	6A
50	IN4001 6p	IN5400 15p	
100	IN4002 7p	IN5401 16p	
200	IN4003 9p	IN5402 17p	8YZ13 58p
400	IN4004 9p	IN5404 22p	8YZ12 66p
600	IN4005 11p	IN5406 26p	8YZ11 73p
800	IN4006 13p	IN5407 28p	8YZ10 85p
1000	IN4007 16p	IN5408 31p	

BRIDGES

V	1A	2A	6A
50	8YX61 - 50	£3.21	
100	8YX61 - 100	£3.48	
200	8YX61 - 200	£3.76	
400	8YX61 - 400	£4.29	
600	8YX62 - 600	£4.29	
1000			

TRIACS

25v	2N6068 45p
50v	2N6069 52p
100v	2N6070 58p
200v	2N6071 63p
400v	2N6073 68p
600v	2N6075 £1.49

SOLDERING



DIN CONNECTORS

Pins	Plugs	Sockets	Line Couplers
2	9p	7p	11p
3	10p	7p	11p
4	11p	7p	11p
5 (180)	11p	8p	11p
5 (240)	11p	8p	11p
6	11p	9p	11p
7	13p	9p	11p


4mm.



Transistor covers

TO 3	10p
TO 66	10p

HEAT SINKS

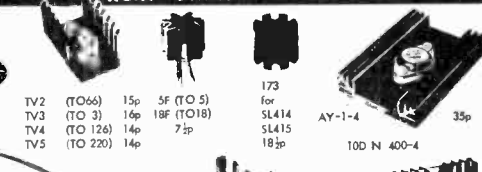

CO-AXIAL

Plug - Screened	11p
Plastic	9p
Sockets	
Chassis	10p
Surface	11p
Coupler	25p

PHONO

Sockets	
1 way	5p
2 way	7p
3 way	7p
4 way	8p
Plugs:	
Plastic Moulded	7p
Chrome Screened	12p
Coupler screened	15p

JACK

Plugs	Sockets
2.5mm *	20p 12p
3.5mm *	20p 12p
standard *	25p 15p
stereo *	27p 21p
side entry standard	48p

AUDIO I.C.'S

A brand New Audio I.C. Leaflet with
Circuits and pin connections for
ALL the I.C.'s listed below
FREE with orders over
£1.00 or 10p
without

I.C. SOCKETS

U1 (TB800)	16p
U1 (TB8105)	16p
U2 (TB810AS)	16p
U2 (TCA940)	16p
U3 (TDA2020)	35p

I.C. PIN SOCKETS

I.C. pins in strips of 100.
Just strip off what you need.
65p per strip

P.C. CONNECTORS



MAINS TRANSFORMERS

secondaries

6-0-6v, 100mA	97p	20-0-20v 1A	£4.55
9-0-9v, 100mA	97p	24-0-24v 1A	£2.48
12-0-12v, 100mA	97p	28-0-28 1A	£6.18
18-0-18v, 200mA	plus	0-24v 40mA	97p

RENDAR INSTA-POWER

safe; inexpensive;
quick A.C. mains
connector. A 13
amp plug top
containing snap
connectors
£1.75

SWITCHES

High Quality 250v 1A	Rotary 2A Mains Switches
S.P.S.T. 25p	35p
D.P.D.T. 45p	
Render Subminiature Toggle S.P.D.T. 48p	Bulgin push-to-make 25p
Slide D.P.D.T. 12p	
	Ergo Dig Switches
	1 pole 8 way 99p
	2 pole 4 way 85p
	4 pole 2 way £1.24
	Lorlin Water Switches 27p
	1 pole 12 way; 4 pole 2 way
	3 pole 4 way; 4 pole 3 way

POWER OUTPUT WATTS	Supply Volts	Load Ohms	Style	Power I.C.	Price	Pre-Amplifier	Supply Volts	Style
0.25	9	16	C	MFC40008	78p	Dual Low Noise	+24	A
0.5	9	8	E	MC13069	86p	Dual Low Noise	+14	A
1	9	8	F	TAA300	£1.76	Dual Pre-Amp	+13	A
2	12	8	G	TAA820	74p	Dual Low Noise	+12	A
2	18	8	A	LM380	£1.08	Dual Low Noise	+15	A
2 1/2 + 2 1/2	18	8	A	LM377	£2.91	General		
3	18	8	J	SL414	£1.72	D.C. Controlled attenuator		
5	24	16	J	SL415	£2.24	3 stage G.P. amp.		
5	24	8	H	TBA800	95p	Tape Pre-Amp		
7	16	4	H	TBA8105	£1.07	Bi-Fet		
7	16	4	K	TBA810AS	£1.07	Hear/Aid Amp 1.3v		
10	20	4	M	TCA940	£1.94	PPL stereo decoder (i)		
15	30	3	O	BHA0002	£2.60	4 channel SQ " (ii)		
35 driver	25	8	F	NE540L	£1.08	4 " pre-amp (ii)		
20	15	4	N	TDA2020	T8A	CBS SQ Logic (ii)		

(i) & (ii) Separate leaflets available free only with purchases over £1

VAT INCLUSIVE PRICES AT 8%

OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
P&P On U.K. Orders 15p Overseas Orders at Cost



Phoenix Electronics (Portsmouth) Ltd.

139-141 Havant Road,
Drayton, Portsmouth, Hants

PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

THIS MONTH'S BARGAIN OFFER!

Rectifier kit. 4 each 1N4148, AA144, 1N4004, 1N4006, 1N5402, 1N5406, SCR 0.6A/200V, Bridge 1A/400V, Triac 2.5A/100V, plus 4 voltages of 400mW Zeners—catalogue value £10.60. Bargain pack PEP/4A—£6.50.


Please send your catalogue—free!

Name

Address

PEP/1A

NEW PE SCORPIO Mk. 2

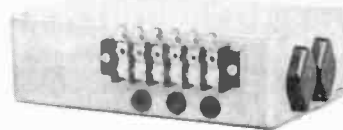

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board. —Uses original plugs, points and coil.—No special parts or extras required. (Case size: 7 1/2 in x 4 1/4 in x 2 1/2 in)

* All components available separately.—S.A.E. with enquiries.

* Construction manual available separately 25p.

Cost £11.78 incl. carr. and ins. or ready built and tested £14.49

Conversion kit from Mk. 1 to Mk. 2. For constructors already possessing Mk. 1 Kits.—Miniature P.C. assembly £1 incl. carr. and ins. With full conversion instructions.

PLEASE ADD VAT TO ALL U.K. ORDERS

(Carriage at cost outside U.K. — Export enquiries welcome.)

DABAR ELECTRONIC PRODUCTS

98 LICHFIELD STREET

WALSALL, Staffs WS1 1UZ



TTL I.C.s 7400 14p 7442 75p 7476 37p 7401 15p 7447 95p 7486 41p 7402 15p 7448 90p 7489 340p 7404 18p 7450 22p 7490 45p 7408 20p 7454 22p 7492 68p 7410 15p 7460 22p 7493 48p 7413 30p 7470 30p 74107 45p 7414 72p 7472 30p 74121 34p 7416 33p 7473 36p 74122 76p 7420 15p 7474 34p 74123 110p 7430 15p 7475 52p 74141 85p					5314 Clock Chip 24 pin DIL 650p. Alarm Clock Chip 40 pin DIL (similar MM5316) 750p. 5001 12 Digit Calculator Chip 28 pin DIL 485p. (All above supplied with full data; data separately 25p each + S.A.E.) PC Keyboard (0-9, decimal, 4 function, C, K, keys). Size: 2.36 x 3.76" x 0.45" 400p.					Popular Op Amps ML709 OPA with ext. comp. 28p ML710 Diff. comparator 35p ML741 OPA with int. comp. (8 pin DIL) 25p ML747 Dual 741 70p ML748 OPA with ext. comp. 38p LINEAR ICs CA3046 Transistor Array 55p CA3048 4 independent Amps 230p CA3089 FM IF Amp 200p CA3090 FM Stereo Decoder 400p LM301 OPA with ext. comp. 40p LM307 OPA with int. comp. 50p MC1303 Stereo Pre-amp 150p MC1307 FM Stereo Decoder 120p MC1310 Collet. FM Stereo Dec. 245p MC1312 SQ Quadruphonic Dec. 220p MFC 4000 1/2 Watt Audio Amp. 40p					MFC6040 Electronic Attenuator 80p MFC8070 Zero Voltage Switch 250p TAA570 Limiter Amp 170p TAA570 AM/FM Radio receiver 180p TBA800 5 Watt Audio Amp 100p TBA810 7 Watt Audio Amp 125p TBA820 2 Watt Audio Amps 90p TCA940 10 Watt Audio Amplifier 270p ZN414 Radio receiver 110p NE536 PET OPA 152p NE555 Timer 40p NE556 Dual 555 120p NE560 PLL 285p NE561 PLL with AM Demod 285p NE562 PLL with VCO 285p NE565 Precision PLL 285p NE566 Function Gen 260p NE567 Tone Decoder 250p SG3402N 172p 8038 Voltage Controlled Oscillator 290p Data sheets on above ICs 10p each.														
ACCESSORIES DIL SOCKETS (L.P.) 8 pin 12p, 14 pin 13p, 16 pin 14p. Mica + bushes for TO3 and TO66 8p.					BRIDGE RECTIFIERS 50V 100V 400V 600V 250mA 15p 1 Amp 20p 21p 24p 25p 2 Amp 30p 35p 45p 48p 4 Amp 40p 6 Amp 55p 60p 78p 98p					SCR-THYRISTORS 50V 100V 400V 600V 1 Amp 42p 45p 60p 78p 3 Amp 43p 49p 78p 100p 7 Amp 80p 84p 115p 16 Amp 82p 98p Other CT106D 45p, 2N3525 91p, 2N4444 185p					TRIACS 100V 400V 500V 3 Amp 85p 99p 120p 6 Amp 88p 120p 150p 10 Amp 107p 154p 185p 16 Amp 145p 180p 205p Other 40430 90p, 40486 85p, 40669 95p DIAC ST2 for use with above triacs 21p.					VOLTAGE REGULATORS 723 1 Amp Plastic TO-220 14 pin DIL 55p 7805 5V 140p MFC4060 70p 7812 12V 140p 7815 15V 140p 7818 18V 140p 7824 24V 140p									
AC126/7 11p BC212 11p OC70/1/2 11p 2N221/2 20p MJE340 45p AC128 11p BC213 10p OC71 12p 2N2369 14p UJTS 35p AC176 11p BC124 13p OC81/2 12p 2N2484 30p TIS43 25p AC187 12p BD115 55p OC83/4 28p 2N2905 18p 2N2160 70p AC188 11p BD124 75p TIP2955 70p 2N2926RB 8p 2N2646 35p AD149 43p BD131 42p TIP41A 68p 2N2926G 8p 2N4871 31p AD161 36p BD132 45p TIP42A 76p 2N2926G 8p 2N4871 31p AD162 36p BF115 22p ZTX300 14p 2N3053 18p AF114/5 13p BF167 23p ZTX304 24p 2N3055 40p FETS AF116/7 13p BF173 25p ZTX500 15p 2N3442 140p BF244 36p AF139 41p BF184 22p ZTX504 50p 2N3702/3 11p MPF102/3 31p BF239 44p BF194 11p 2N696 15p 2N3704/5 11p MPF104/5 31p BC107/8 9p BFR39/40 28p 2N697 13p 2N3706/7 11p 2N3819 20p BC109 10p BFR41 22p 2N698 30p 2N3708/9 9p 2N3820 57p BC147/8 7p BFX29/30 30p 2N706 12p 2N3772 16p 2N3823 60p BC149 8p BFX50/1/2 15p 2N708 18p 2N3773 220p 2N5457 31p BC157 13p BRY39 34p 2N930 12p 2N3903/4 11p 2N5458 31p BC158 12p MJE2055 95p 2N1131/2 18p 2N4058 15p 2N5459 31p BC159 14p MJE3055 65p 2N1302/3 17p 2N4060 15p 2N5459 31p BC169C 12p OC26 47p 2N1304/5 21p 2N5191 95p MOSFETS BC177 18p OC28 55p 2N1306/7 28p 2N5194 85p 40673 50p BC178 17p OC35 48p 2N1308/9 28p 2N2904 20p 40841 75p BC179 18p OC36 52p 2N1613 20p 2N3054 45p 3N128 75p BC182/3 10p OC41/2 15p 2N1711 20p 40361 36p 3N140 85p BC184 11p OC44/5 11p 2N2219 20p 40362 38p 3N141 75p					C-MOS ICs CD4001AE 37p CD4011AE 37p CD4012AE 37p CD4013AE 67p CD4016AE 90p CD4017AE 183p CD4023AE 37p CD4024AE 148p CD4025AE 37p CD4027AE 108p CD4030AE 82p CD4046AE 225p CD4047AE 154p					OPTO-ELECTRONICS LDR ORP12 50p, ORP60 60p; Trans. OCPT1 55p, 2N5777 45p; LEDS TIL209 (Red) 16p, Green/ Yellow 35p. Seven Segment Displays Filament LIT 704 0.354in DIL 120p All LED MAN-3M 0.127in PCB 100p MAN-4 0.191in DIL 180p Reflective Bar LED LIT 707 0.33in DIL 135p LIT 747 0.63in DIL 250p 3 Digit Readouts Blislor Lens 0.127in DIL 250p Red Lens Filter 0.127in DIL 185p					RECTIFIER DIODES 500mA BY100 15p 1 Amp BY126 12p BY127 12p 1N4001 5p 1N4004 6p 1N4007 7p 1-5 Amp PL4004 10p 3 Amp PL7004 20p 5 Amp BYZ10 50p BYZ11 50p BYZ12 50p BYZ13 50p					SIGNAL DIODES BA100 10p OA47 8p OA70 8p OA79 7p OA81 7p OA91 6p OA95 7p OA200 6p OA202 7p IN914 4p IN916 6p IN4148 4p					ZENER DIODES 3-3V to 33V 400mW 9p 1-3W 27p 1-5W 27p 10W 55p Other Diodes TUNNEL AEY11 50p VARIACAP BB103 15p BB104 30p BB105 30p				

Minimum order £2.
All prices exclusive of VAT.
P. & P. 15p.

All goods brand new
MAIL ORDER ONLY

TECHNOMATIC LTD.

54 Sandhurst Road, London NW9. Tel. 01-204 4333

The big three from Wireless World

WIRELESS WORLD ANNUAL 1975



The first ever Wireless World Annual contains pages of features covering all aspects of electronics and communications, including new and established techniques both practical and theoretical. Content includes constructional projects for a general purpose audio oscillator and a small boat echo sounder. There is a reference section packed with useful information.

HIGH FIDELITY DESIGNS

In response to demand for reprints of Wireless World constructional projects, we have collected fifteen of the most popular designs in one book. It covers tape, disc, radio, amplifiers, speakers and headphones. Where necessary, specifications have been updated to incorporate new components which have become available.

HI-FI YEAR BOOK 1975

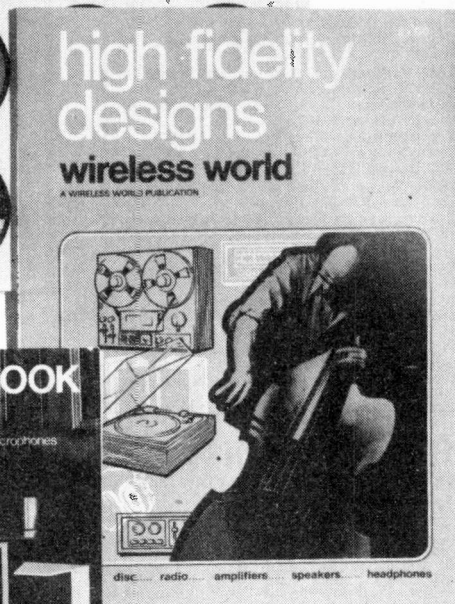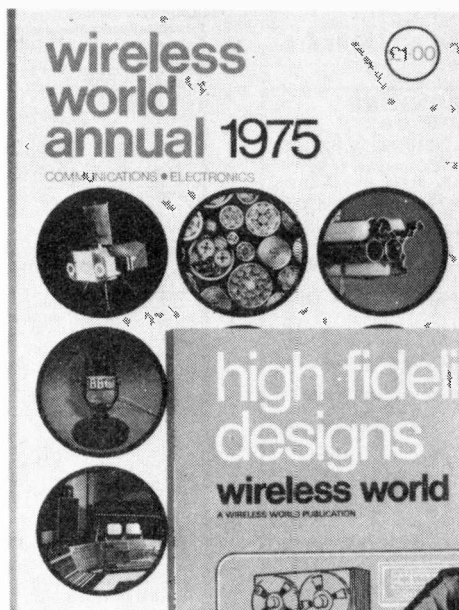This is the book that tells you everything you need to know about the hi-fi equipment on the market. Separate illustrated sections cover every major category, together giving prices and specifications of over 2,000 products. And it's got a directory of dealers/manufacturers – plus a host of articles on the latest hi-fi developments and their application.



**ALSO
AVAILABLE
AT LEADING
BOOKSTALLS**

To: General Sales Department, Room 11,
Dorset House, Stamford Street, London SE1 9LU

ORDER FORM

Please send me books as indicated below (state number of copies of each):

Wireless World Annual 1975 @ £1.35 each incl.

High Fidelity Designs @ £1.35 each incl.

Hi-Fi Year Book 1975 @ £2.00 each incl.

I enclose remittance value £
(cheques payable to IPC Business Press Ltd.)

Name
(please print)
Address

Regd. in England No. 677128 Regd. office Dorset House, Stamford Street, London SE1 9LU

RATES: 11p per word (minimum 12 words). Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

R.T. SERVICES
(MAIL ORDER ONLY)

(Proprs.: Minicost Trading Ltd.)

53 THE RIDGEWAY, ENFIELD, MIDDX.

299/301 BALLARDS LANE
LONDON N12 8NP (01-445 5188)
MAIL ORDER ONLY. Cash with order.
Orders under £3 plus 15p P. & P.
Add V.A.T. to total

Tel.: WHIRALL 464/465 (STD 0948 72)
(Propra.: Minicost Trading Ltd.)

3 THE RIDGEWAY, ENFIELD, MIDDX.

C.W.O. PLUS P.P. 10p TO
BETA DEVICES,
53 THE RIDGEWAY, ENFIELD, MIDDXX.

(Proprietor: Minicost Trading Ltd.)

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO.**, P.O. Box 5, Frome, Somerset. Immediate cash settlement.

DART ELECTRO SERVICES

124 Oaklands Park, Buckfastleigh, Devon

ELEC. CAPS (ITT) μ F/V

1/100, 2-2/63, 4-7/35, 10 μ F/16, 8p; 10/63, 22/10, 47/25, 100/10, 7p; 100/50, 10p; 470/35, 220/50, 18p; 1000/25, 24p.

L.V. DISCS

0-01/18, 0-22/18, 0-047/12, 6p; 0-1/30, 0-22/6, 7p.

P.S. CAPS 5%

10-680pF, 5p; 1000-10000pF, 8p.

P.E. CAPS 250V

0-01-0-047, 5p; 0-068-0-1, 6p; 0-15-0-22, 8p; 0C33-0-47, 10p; 0-68-1 μ F, 18p.

RESISTORS

0-25W E12CF, 1p; 0-5W E12CF, 1p; 0-5W E24MO, 4p.

ZENERS

400mW, 12p; 1W, 18p.

TRANSISTORS

2N699	45p	AD161.2 MP	95p
2N1613	25p	BC107/8/9	12p
2N3053	21p	OA202	7p
2N3054	50p	1N914	5p
2N3055	55p	1N4001/2	7p
2N3702-7	12p	1N4003/4/5	9p
2N3773	£2.95	1N4006/7	13p
2N3819	40p	1N4148	6p
2N5459	49p		

LIN. I.C.s

μ A709/14	32p	μ A741/8	38p
μ A709/T099	28p	μ A723	7p

Please add 8% VAT and 15p Postage and Packing.

EDUCATIONAL

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on April 21st.

Prospectus from London Electronics College, Dept. A3, 20 Penryn Road, London SW5 9SU. Tel. 01-373 8721.

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians, Radio/TV/Electronics Technicians Telecommunications Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 730, Intertext House, London SW8 4UJ
Or phone 01-622 9911 (All hours)

One of the best ways of taking **A DEGREE IN ELECTRICAL or ELECTRONIC ENGINEERING** and also qualifying to become a **CHARTERED ELECTRICAL ENGINEER** is to join the **NORTH STAFFORDSHIRE POLYTECHNIC** at Beaconside, Stafford.

We can introduce you to industrial firms for your practical training periods. In most cases these contacts lead to permanent staff appointment in industry upon graduation. Advice on course, accommodation and training from:

The Head of the Department of Electrical & Electronic Engineering, Room C16, North Staffordshire Polytechnic, Beaconside, Stafford. Tel.: Stafford 52331.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 580644 for brochure.

SITUATIONS VACANT

ELECTRONIC ENGINEER

required in an expanding electronic services company in the Sultanate of Oman, specialising in commercial/industrial television and radio installations, also the installation and servicing of electronic security systems. Applicants should have a minimum of either Ordinary National Certificate or City & Guilds Final.

Salary £3,500 p.a. nett, free furnished accommodation supplied, limited free utilities, i.e. electricity and water, company car and petrol supplied free, annual paid leave of one month with air fares provided, initial contract period minimum of two years.

Applications should be made to:

P.O. Box 1000, Muscat, Sultanate of Oman

MEN!
£70p.w.
can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

London Computer Operators Training Centre Y33, Oxford Hse. 9-15 Oxford St., W.1. Tel. 01-734 2874

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets, manuals, books on radios, T.V.s, etc. Service sheets **40p** plus S.A.E. Free book lists on request. Back issues of P.W., P.E., E.E., TV available **25p** plus 7p post. S.A.E. with enquiries: B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

SERVICE SHEETS for over 6000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only **30p**, plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue **20p** plus S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429068.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **20p**. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

FOR SALE

FOR SALE back issues 1966-1973. Tel. 0283 67011.

FIBREGLASS SHEET $\frac{1}{8}$ in. thick, high strength and insulation properties, sheets 12 in. x 12 in., **45p** each. Send to: Richards, 15 Linden Lane, Kirby Muxloe, Leicester.

COMPLETE MINT COLLECTION of Practical Electronics in binders with indexes, blue-prints, etc. Offers 01-435 4552.

WANTED


TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

'SCOPE TUBES WANTED, 1 in. type 1CP1 or DH3/91, preferably with bases and screens. Price up to £5 according to age and condition. Cheque or P.O. by return. **BARRY CHILDE**, 370 Charninster Road, Bournemouth, BH8 9RX. Tel. 516565. Closed Mondays.

VINTAGE RADIOS are a fascinating and lucrative hobby. We have sets, literature, etc. from **£2-£100** and urgently need more. Write for details to **VINTAGE RADIO MART**, 26 Bowden Lane, Chapel-en-le-Frith, Stockport, Cheshire.

"RADIO & TV SERVICING" books wanted from 1962 edition onwards. **£2** paid per copy by return post. **BELL'S TELEVISION SERVICES**, 190 Kings Road, Harrogate, Yorks. Tel. (0423) 55885.

MISCELLANEOUS

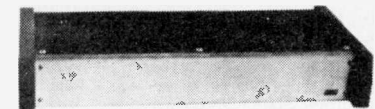

The **PE ORION HI-FI STEREO AMPLIFIER** uses our GB1 Bec cabinet (illustrated in Jan. 1974 Practical Electronics). Special Price to readers of Practical Electronics. £3.60 plus 45p P. & P. Ready Punched with a self-adhesive anodised aluminium front panel. £1.80 extra. Other sizes and types. Send S.A.E. for details. Please add 8% VAT to total amount.

TRADE ENQUIRIES INVITED

H.M. ELECTRONICS

275a Fulwood Road
Broomhill, Sheffield S10 3BD
Tel. 669676

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 44p stamps for catalogue. **RAMAR CONSTRUCTOR SERVICES**, Masons Road, Stratford on Avon, Warwick, CV37 9NF.

12 VOLT 21w/13 watt **FLUORESCENT LIGHTING** (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc. **Guaranteed**

£5.50

inc. VAT and post.
List price £7.42 inc. VAT

SAKOP ELECTRONICS Tel. 53206
23 Nyle Cop. Shrewsbury, Shropshire

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty P.V.C. faced steel. Hundreds of radio, electronic and hi-fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Prompt despatch. Free literature. **BAZELLI**, Department No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster, LA2 6LT.

FLUORESCENT LIGHT KIT

12 v
8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19
Ready built £3-78
Diffuser only 50p extra

inc VAT
post &
packing

ALUMINIUM BOXES

Prices include lid, screws, and V.A.T.
Post and packing 10p extra on all orders.


		by	by	by	high	30p
7	5 1/2"	by	2 1/2"	by	1 1/2"	30p
8	4"	by	4"	by	1 1/2"	30p
9	4"	by	2 1/2"	by	1 1/2"	30p
10	5 1/2"	by	4"	by	1 1/2"	40p
11	4"	by	2 1/2"	by	2"	30p
12	3"	by	2"	by	1"	20p
13	4"	by	4"	by	2"	50p
14	7"	by	5"	by	2 1/2"	80p
15	8"	by	6"	by	3"	80p
16	10"	by	7"	by	3"	90p

Order now to —

ELECTRONIC DESIGN ASSOCIATES
DEPT PE
82 Bath St., Walsall, WS1 3DE. Phone 33652

LOW COST I.C. MOUNTING. 100 I.C. pin sockets 60p. Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports 5p/pair. (P. & P. 5p/order). LED (MLED500) 20p each post free. Quantity rates. **P.K.G. ELECTRONICS**, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

MINI ACCUMULATORS

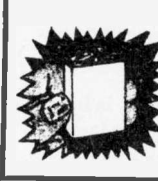

2 volt MULTI-USE
Sealed Lead Acid Rechargeable Cells.

Size **L450**—1 1/4" x 1 1/4" x 0 1/4". 3 for £1.85 inc. P. & P.

Size **GA2**—1 1/2" x 1 1/2" x 0 5/8". 3 for £2.35 inc. P. & P.

GARFIELDS, 269 Rye Lane, London, S.E.15

IC SOCKET PINS for low cost mounting of 8 to 40 pin DILs. 70p (+ 5p VAT) for strip of 100, £1.50 (+ 12p VAT), for 3 x 100, £4 (+ 32p VAT) for 1,000. Instructions supplied—send S.A.E. for sample. 10p P. & P. for orders under £2. **SINTEL**, 53b Aston Street, Oxford. Tel. 0865 43203.

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1lb Reel
10-14	£2.05	£1.15
15-19	£2.15	£1.20
20-24	£2.20	£1.25
25-29	£2.25	£1.30
30-34	£2.35	£1.38
35-40	£2.50	£1.45

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 80p).

SEND 5" x 7" S.A.E. FOR DETAILS TO:

CROFTON ELECTRONICS
124 Colne Road, Twickenham
Middlesex TW2 6QS

THE CHIPS ARE DOWN! AY-5-1224 digital clock chip now £3.95 inc. VAT, post free. Circuit and details S.A.E. **GREENBANK ELECTRONICS**, Dept. 320, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

VALVES, TRANSISTORS, STYLIS. Valves 1930 to 1975. 1,500 types. Many obsolete. List 15p. Transistors list 15p. Stylis list 10p. S.A.E. for quotation. **COX RADIO (SUSSEX) LTD.**, The Parade, East Wittering, Sussex. Tel.: West Wittering 2023.

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists DOZENS of HIGHLY UNUSUAL, LOW-COST BARGAINS, READY-BUILT MODULES.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size)	£2.90
PEOPLE DETECTOR	£3.20
Big-Ear SOUND-CATCHER	£3.20
Mini DREAM LABORATORY	£3.20

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and we'll RUSH you a COPY YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey

(Mail Order U.K. only)

fibre optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate. £8.75.

FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia. 1-14mm. 40p per metre (£3 per 10m).

FIBROFLEX SIZE 4. 2-28mm bundle dia. £1-50 per metre (£12 per 10m).

CROFON 1610. 64-strand plastic light conduit, bundle dia. 1-8mm. O.D. 3-3mm. £1-20 per metre (£8-30 per 10m).

PLASTIC OPTICAL MONOFIBRE. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.

OPTIKIT 103. Contains 2m Crofon 1610 plus 5m each FP20, FP40, FP60 plus polishing compound. A handy pack for the experimenter. £4-70.

LENSES AND REFLECTORS. We stock a range of lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.

OPTIKIT LS. 1 each of 8 lenses. £2-50.

OPTIKIT RRS. 1 each of 5 reflectors. £1-50.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20 x—enhance contrast on cris. LED displays, nixies, instruments, etc. Available in red/amber/green/neutral. 50mm square 80p; 75mm £1-20; 150mm £4.

LINEAR POLARISERS. For light valves, stress analysis, type HX32. Type KN42 is for high temp. use in projectors. Use a pair to make a psychedelic light show. Price as for circular polarisers.

LIGHT SOURCES AND DETECTORS: MV54 Miniature (20mm) Red LED, 20p (10+ 10p); MLED500 T092 Red LED, 20p (10+ 10p); MLED92 Infra-Red Emitter, 30p (10+ 10p); X200-H 3mm Red LED, 20p (10+ 10p); X200-Y or -G Yellow/Green, 30p (10+ 10p); 2N577 High Sensitivity Photodiode Silicon Detector, gain x2,500, 50p (10+ 45p); MRD150 Silicon Phototransistor—high speed, 40p good sensitivity. 70p (10+ 60p).

NEW MLS203. Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24W power. £1-20 (10+ £1-10).

SEOS ULTRASONIC TRANSDUCER. For remote control 40KHz. 1/2R pair, £3-50.

Please add 8% VAT to prices above

Send 9in x 6in S.A.E. for short form list.

FIBRE OPTIC SUPPLIERS

(Dept. PE), P.O. Box 702
London W10 6SL

PRINTED CIRCUIT BOARDS. Manufacturer's offer: PCB's for ALL "P.E. and P.W." projects published after June, 1974, at ONE price, 70p each. Any 5 £2-85. **PRODUCTION SPACE** available for: PCB Production, PCB and Electronic Design to Spec.; electroplating, silk-screening, roller and electro tinning. All art-work and photography undertaken. Send basic circuit, P.C. layout or P.C. master stating quantity required for estimate by return, or phone: **W.K.F. ELECTRONICS**, Dept. P.C., Welbeck Street, Whitwell, Workop, Notts., S80 4TW. Tel.: Whitwell (Derbys.) 665.

LIGHTING MODULES AND KITS CHEAPER STILL!

SAVE POUNDS BY BUYING DIRECT!!

SOUND TO LIGHT: 3 x 11 kW channels with SENSITIVITY, DIMMING and BYPASS controls. Designed to be robust and reliable and simple to build. KIT FORM: £13-99; PRE-BUILT: £15-99. **THEATRE AND DISCO/CLUB DIMMERS OUR SPECIALITY!**

Only written enquiries and Mail Order to:

SELEKTRON

21 Priors Road, Windsor, Berks. SL4 4PD

AERIAL BOOSTERS £3, P. & P. 10p. We make three types of boosters: **L11-VHF radio; L12-VHF 405 TV.** Please state channel numbers. **L45-UHF-625 TV.** S.A.E. leaflets: **LANCASHIRE MAIL ORDER**, 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

SINTEL

Add 10p P. & P. for orders under £2. Data, and circuits where appropriate, supplied with orders, or available separately (44p stamp each).

3 Digit DIP LED calculator display £1-35 + VAT = £1-45
High Quality 0-3in LED 7 seg. display 85p + VAT = £1-02
MK50250N Alarm Clock IC £2-80 + VAT = £3-45

Send for our new simple MK50250N circuit diagrams
Soldercon IC socket pins — 300 pins for £1-50 + VAT = £1-62
1,000 pins for £4-00 + VAT = £4-32

MK50250N + 4 x DL704 0-3in LED's £10-20 + VAT = £11-01
Complete circuits and special prices for MK50250N with LED's
Minitorne or SP352's

SINTEL, 53B ASTON STREET, OXFORD. Tel (0865) 43203

FANTASTIC NEW MICROTEST 80

MEASURES
ONLY

90 x 70 x 18mm



Amazing Value at £11.95
8 fields of measurement
and 40 ranges

Volts d.c. 6 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20kΩ/V)
Volts a.c. 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V (4kΩ/V)
Amp. d.c. 5 ranges: 50μA, 500μA, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250μA, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω, Ω x 1, Ω x 10, Ω x 100 (da 1/10 di Ω fino a 5MΩ)
V Output 5 ranges: 1.5V, 10V, 50V, 250V, 1,000V
Decibels 5 ranges: +6dB, +22dB, +36dB, +50dB, +62dB
Capacity 4 ranges: 25-F, 250μF, 2,500μF, 25,000μF



SUPRETESTER 680 RICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories
1,000 times overload
Circuit board is removable without de-soldering
More ranges than any other meter. Ask for free catalogue.
Accessories Extra
Accessories (extra) available to convert Microtest 80 and Supertester 680R into following SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLT-METER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

£18.50

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0.06-3A-8 Ranges.
A-AC 0.3-3A-5 Ranges.
V-DC 0.6-1200 V-9 Ranges.
V-AC 3-900 V-8 Ranges.
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +120B. Accuracy: ±2.5% DC
±4% AC. Dimensions: 167 x 98 x 63mm.
Only £8.85



ALPHANUMERIC NIXIE TUBES B7971

The Alphabetic NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphabetic NIXIE tube provides many unique benefits including * 170V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footlamberts brightness * Long life with no loss of brightness * Character height 2 1/2 in.
Bases for above 80p each.



Price only 99p each plus 16p P.P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100μs. Character height 0.51, over-all size 1 1/4 in.
Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853st

1-25 £1.00; 25+ 90p; 100+ 80p; 1,000+ price on application.

Add 8% VAT to all items + 35p P. & P.
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

BUILD THE TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best-selling metal locator kit
- Weights only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send a.p.s. for leaflet

Complete kit £9.80 Built, tested and guaranteed £13.75
P. & P. 60p + 78p VAT P. & P. 60p + £1.10 VAT

MINIKITS ELECTRONICS, 69 CLEVELAND ROAD,
LONDON E16 2AN (Mail Order Only)

METER REPAIRS. Ammeters, voltmeters multi-range meters, etc. Send to METER, REPAIRS, 21 Mount Road, Thundersley, Brentlees, Essex, SS7 1HA.

PRINTED CIRCUIT BOARDS. PCB for any PRACTICAL ELECTRONICS and PRACTICAL WIRELESS project, 50p per board. From individual patterns £1 plus 5p per square inch. Add VAT plus 5p P. & P. per board. Mail order only. TEC, 241 Burnt-Oak, Broadway, Middlesex.


BOOKS AND PUBLICATIONS

UFO CHARTS: Daily Flight, 50p; Prediction, 54p; Map, 50p; Propulsion, 55p; "Anti-Gravity", 55p. TV UFO Detection (Reprint), 63p; Circuits: Transistor Optical Detector, 66p; Radiation/Optical, 44p; Microdetectors (Memory, LSI), 80p; Crystal Radiation/Counter-Timer/Stopclock, 85p. PET Multi-meter, £1.70. R. & E., Highlands, Needham Market, Suffolk.

NEW IMPROVED

MAINS INTERCOM

NO BATTERIES
NO WIRES

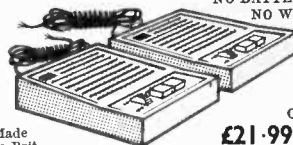

ONLY £21.99 per pair + VAT £1.76

Made to Brit. Safety & Telecom. Standards, Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal-clear communication from room to room. Operates over a 1/2-mile range. On/Off switch, Vol. control. Useful as office intercom, baby alarm, invalids. No G.P.O. licence reqd. Full price ref. if returned in 10 days. 12 months service guarantee. P. & P. 60p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £11.95

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95.
P. & P. 48p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE3)
169 KENSINGTON HIGH STREET, LONDON, W.8

PE MINISONIC

COMPONENT KITS NOW AVAILABLE.
4 1/2p STAMP BRINGS DETAILS.

TRANSISTORS

BC204 11p
BC209C 11p
BC182 10p
BC184 11p
BC212 14p
BC214 16p
BC213 15p
BC213L 15p
ZTX300 15p
ZTX500 17p
2N2484 24p
2N2904 30p
2N2905 27p
2N2219 22p
2N3054 100p

High Voltage

MPSL01 39p
MPSL51 41p
MPSU07 69p
MPSU57 85p
2N3819 46p
2N5459 60p

DIODES

1N5401 21p
1N914 5p
BA148 25p
1S150 12p
1GP7 10p

NOISE DIODES

Z1J 60p
Z1M 120p

RECTIFIERS

REC41A 120p
REC46 255p
REC70 40p
EA100/10 100p
MDA942A/1 210p

VOLTAGE REGULATORS

μA7815 220p
723 180p

ARRAYS

ML3046P 75p
CA3096AE 120p

OP. AMPS

709/8 Dip 39p
710/TOS 39p
741 37p
748 48p
FETMOPA 450p

SPECIAL PURPOSE LINEARS

SG3402N 174p
SG3402T 174p
SG1495D 290p
MFC6040 100p
MFC4000B 70p

T.T.L.

7402N 38p
7410PC 24p
7420N 24p
7430PC 23p
7473N 75p
7475N 75p
7476N 49p
7489N 660p
7493PC 89p
74121J 85p
74122N 80p
74123N 144p
74150N 210p

RESISTORS

2% METAL OXIDE 16p for 5
5% CARBON FILM 9p for 5

MINISONIC P.C.B.

118 x 295mm best quality epoxy-glass, roller tinned. Complete with over-lay details and instructions.

£3.62 inc. VAT and U.K. postage.

V.A.T.

Please add 8% to final total of order

CONSTANTAN WIRE

0-03 ohms/cm as specified for the POWER SLAVES. 20cm lengths 10p

INTRODUCING THE MINISONIC

C20 AUDIO CASSETTE
£1.15 Inc. VAT, P. & P.

MINISONIC COMPONENT KITS

V.C.O. (2 required) £3.85
V.C.F. (1 required) £4.98
ES/V.C.A. (2 required) £5.70
Voltage Ref. £0.57
Ring. Mod. (1 required) £4.14
Noise Gen. (1 required) £1.86
Kbd. Control (1 required) £4.16
HF Osc. and Det. £1.93
Power Amps £2.61

All above prices are for single kits of each type and include VAT, P. & P. Full details are included in lists.

Miscellaneous Items

5 way 180° DIN sockets 27p
5 way 180° DIN plugs 34p
Battery connectors 9p/pair
Hook up wire, 36 colours, 1/2 metre of each 70p
Min. DPDT toggle switch £1.20

VAT should be added to quoted price of miscellaneous items.

SAVE BY PURCHASING A COMPLETE SET OF KITS AS DETAILED TOGETHER WITH SWITCH, BATTERY CONNECTORS, HOOK-UP WIRE AND P.C.B.

Price inc. VAT & U.K. Postage £43

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P. & P. Otherwise please add 10p in the £1.



G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits. ALL ARE BRANDED, FULL SPECIFICATION devices offered at unbeatable prices!

BRAN TUB !!!

- * Resistors—wire-wound and carbon.
- * Capacitors—silver-mica, paper, ceramic, polyester and electrolytic.
- * Controls—volume, pre-set, carbon, wire.
- * Diodes—silicon, germanium, zener.
- * Transistors—silicon, germanium.

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting—TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

And the price that we are asking? Only £1.50 including both postage and VAT!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

	1/99	100/499	500/1000		1/99	100/499	500/1000		1/99	100/499	500/1000
7400	£0-15	£0-125	£0-10	7442	£0-645	£0-537	£0-43	7494	£0-495	£0-412	£0-33
7401	£0-15	£0-125	£0-10	7443	£1-275	£1-082	£0-85	7495	£0-63	£0-525	£0-42
7402	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7496	£0-72	£0-60	£0-48
7403	£0-15	£0-125	£0-10	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-262	£0-21
7404	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-262	£0-21
7405	£0-18	£0-15	£0-12	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-262	£0-21
7406	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-262	£0-21
7407	£0-375	£0-312	£0-25	7448	£0-855	£0-712	£0-57	74122	£0-45	£0-375	£0-30
7408	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-63	£0-525	£0-42
7409	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7410	£0-15	£0-125	£0-10	7453	£0-15	£0-125	£0-10	74151	£0-69	£0-575	£0-46
7412	£0-195	£0-162	£0-13	7454	£0-15	£0-125	£0-10	74153	£0-69	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-69	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74156	£0-69	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7473	£0-315	£0-262	£0-21	74160	£1-005	£0-837	£0-67
7420	£0-15	£0-125	£0-10	7474	£0-315	£0-262	£0-21	74161	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7475	£0-465	£0-387	£0-31	74162	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7476	£0-315	£0-262	£0-21	74163	£1-005	£0-837	£0-67
7426	£0-27	£0-225	£0-18	7480	£0-435	£0-362	£0-29	74166	£1-425	£1-187	£0-95
7427	£0-27	£0-225	£0-18	7482	£0-75	£0-625	£0-50	74174	£1-20	£1-00	£0-80
7430	£0-15	£0-125	£0-10	7483	£0-825	£0-687	£0-55	74175	£0-975	£0-812	£0-65
7432	£0-27	£0-225	£0-18	7485	£1-275	£1-062	£0-85	74192	£1-275	£1-062	£0-85
7437	£0-27	£0-225	£0-18	7486	£0-315	£0-262	£0-21	74193	£1-275	£1-062	£0-85
7438	£0-27	£0-225	£0-18	7490	£0-465	£0-387	£0-31	74198	£2-10	£1-75	£1-40
7440	£0-15	£0-125	£0-10	7492	£0-465	£0-387	£0-31	74199	£2-10	£1-75	£1-40
7441A	£0-825	£0-687	£0-55	7493	£0-465	£0-387	£0-31				

To secure the above prices, all orders for these devices must exceed £10 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW!!!

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray. £1-00
Developer and Etchant 50p
plus postage

FIBRE-GLASS COPPER LAMINATE


Single sided 75p sq.ft
Double sided £1 sq.ft
Cut in any multiple of 6in to a maximum size of 3ft x 4ft

POSTAGE 30p

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

POSTAGE 30p

SYNTHESISER Modules by Dewtron®

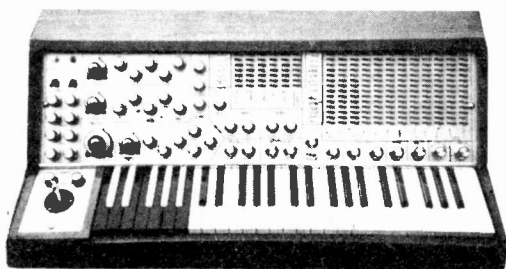

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

P.E. ORION

Complete kit of semiconductors £9.95
High quality printed circuit £2.95

THIS GLASS FIBRE P.C.B. IS ROLLER TINNED AND SCREEN PRINTED WITH COMPONENT LOCATIONS.

FERRANTI semiconductors

BF559	18p	ZTX304	29p	ZTX504	55p	ZS170	14p
BF580	21p	ZTX310	12p	ZTX510	25p	ZS171	16p
BF581	21p	ZTX311	14p	ZTX530	29p	ZS172	22p
BF596	19p	ZTX312	14p	ZTX531	34p	ZS174	26p
BF597	23p	ZTX313	16p	ZTX550	25p	ZS176	33p
BF598	23p	ZTX314	17p	ZTX551	27p	ZS178	58p
ZTX107	12p	ZTX330	21p	2N3055	78p	ZS270	15p
ZTX108	9p	ZTX331	23p			ZS271	22p
ZTX109	14p	ZTX382	15p	* DIODES *		ZS272	25p
ZTX212	14p	ZTX383	19p			ZS274	29p
ZTX213	15p	ZTX384	23p			ZS276	38p
ZTX214	19p	ZTX450	23p			ZS278	61p
ZTX239	16p	ZTX451	25p				
ZTX300	18p	ZTX500	16p			* ZENERS *	
ZTX301	17p	ZTX501	17p			KSO30A 10	
ZTX302	23p	ZTX502	23p			KS180A	28p
ZTX303	18p	ZTX503	18p			BZV19 series	15p

MOTOROLA BD699 £1-10, BD700 £1-22, MJE2955 £1-30, MJE3055 75p.

SIGNETICS UA748CV operational amplifier 55p each.

RCA PRICES SLASHED! CA3090Q stereo decoder only £3-25 each.

ZN414 THE FAMOUS FERRANTI RADIO I.C. Only £1-32 with data.

SCORPIO Mk. II. Complete kit of semiconductors £5-65 (State 6V or 12V).

ALL DEVICES SOLD BY US ARE TOP GRADE, BRAND NEW AND TO FULL MANUFACTURER'S SPECIFICATION. We do not sell seconds or rejects. We are specialists in FERRANTI semiconductors and can supply any device to order.

S.A.E. for quote. Send S.A.E. for our free data sheet and price list for FERRANTI semiconductors.

POSTAGE AND PACKING 10p. FREE ON ORDERS OVER £3
ALL OUR PRICES INCLUDE VAT

DAVIAN ELECTRONICS
PO BOX 38, OLDHAM, LANCs, OL2 6XJ

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to:

ALDERMASTON COLLEGE

Dept. TPE03, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

MECHANICAL	DRAUGHTSMANSHIP	Construction
Society of Engineers—	Institute of Engineering	Surveyors Institute
A.M.S.E. (Mech.)	Designers (A.M.I.F.D.)	L.C.S.I.
Institute of Engineers & Technicians (A.M.I.F.T.)	Draughtsmanship	CITY & GUILD'S
CITY & GUILD'S	Elec. Draughtsmanship	General Building (all branches)
Gen. Mech. Eng.	Architectural	Heating & Vent.
Maintenance Eng.	Draughtsmanship	Inst. Clerk of Works
Welding	Technical Drawing	Site Surveying
Gen. Diesel Eng.		Health Engineering
Sheet Metal Work		Road Construction
Eng. Inspection		Quantities
Eng. Metallurgy		Estimates
		Hydraulics
		Structural Eng.
ELECTRICAL & ELECTRONIC	RADIO & TELE-COMMUNICATIONS	GENERAL
CITY & GUILD'S	CITY & GUILD'S	Agricultural Eng.
Gen. Electrical Engineering	Telecoms	Council of Eng. Institutions
Electrical Installations	Gen. Radio & TV	Farm Science
Electrical Maths	Eng. Radio Amateurs	Plastics
Computer Electronics	Exam Radio Servicing	
Electronic Eng.		
Practical Radio & Electronics (with kit)		
MANAGEMENT & PRODUCTION	AUTOMOBILE & AERONAUTICAL	
Institute of Cost & Management Accountants	Institute of the Motor Industry	
Computer Programming	A.M.I.I.	
Works Mgmt.	CITY & GUILD'S	
Work Study	Auto Eng.	
Gen. Production Eng.	Gen. Auto Eng.	
Estimating & Planning	Motor Mechanics	
Storekeeping	Auto Diesel Eng.	
Management Skills	Garage Mgmt.	
Quality Control	A.F.C. Aero Engineering	
	Exams	
	Gen. Aero Eng.	
	CONSTRUCTIONAL	
	Institute of Building	
	L.I.O.B.	
	A.B.I. Clerk of Works	

Supplementary courses for Nat. Certificates.

G.C.E.
— choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
Dept. TPE03, Reading RG7 4PF

TPE03

NAME
Block Capitals Please
ADDRESS

POST CODE

OTHER SUBJECTS

AGE

Accredited by C.A.C.C.

Member of A.B.C.C.

Henry's Radio

LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT.
LOW PRICES—MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board. Gardners low field transformer. 6-ICs, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15in x 2 1/2in x 6 1/2in mains operated. Free teak sleeve with every kit.

£31.00 (Carriage 50p)

(also built and tested £37.50)



(also built and tested £24.95)

STEREO FM TUNER Features capacity diode tuning lead and tuning meter indicators. stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8in x 2 1/2in x 6 1/2in. Complete kit with teak sleeve

£21.00 (Carriage 50p)

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners—Power Suppliers—Amplifiers

AMPLIFIERS (all single channel unless stated)	
4-300M	9 volt 300MW
4-200	9 volt 250MW
104	9 volt 1 watt
304	9 volt 3 watt
555	12 volt 3 watt
5555ST	12 volt 1 1/2 + 1 1/2 watt
E1208	12 volt 5 watt
608	24 volt 10 watt
410	28 volt 10 watt
620	45 volt 30 watt
240	30/35 volt 15 watt
260	45/50 volt 25 watt
SA6817	24 volt 6 ~ 8

Amplifiers with controls

E1210	12 volt 2 1/2 + 2 1/2 watts 8 ohms	8-25
R500	Mains 5 watts 4-16 ohms	8-25
SAC 14	Mains 7 ~ 7 watts 8 ohms	11-75
SAC30	Mains 15 ~ 15 watts 8 ohms	14-95
CA038	9 volt 1 1/2 + 1 1/2 watts 8 ohms	6-95
CA088	12 volt 3 + 3 watts 8 ohms	10-50

AM/FM MODULES

Mullard LP 1186 FM tuner (front end)	
with data 10 to 7 MHz O.P.	4-85
Mullard LP 1157 AM module	2-50
Mullard LP 1171 AM FM module	4-50
Mullard LP 1179 AM FM front end	4-85
Mullard LP 1185 10 to 7 MHz IF unit with data	4-50

FM & AM TUNERS & DECODERS

FM5231 (TU2) 6 volt FM tuner	7-95
TU13 12 volt version (FM use with Decoder)	7-95
SD4912 Stereo Decoder for TU3 12 volt	7-95
SP62H 6 volt stereo FM tuner	11-95
A1007 9 volt MW-AM tuner	4-80
Sinclair 12 45 volt FM tuner stereo recorder for above	7-45
A1018 9 volt FM tuner in cabinet	13-95
A1005M (S) 9-12 volt Stereo decoder FM for above	7-50
1067 12V Stereo decoder gen. purpose	6-50
Gorier Permeability FM tuner (front end) 10 to 7 MHz O.P.	4-20

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier	6-75
E1300 Cart Tape Mic inputs 9 volt	2-85
E1310 Stereo 3-30 mV mag cart 9 volt	4-75
FF3 Stereo 3 mV tape head 9 volt	4-95
3402 Stereo 5-20 mV Mag cart mains	5-95
EQ25 Mono 3-250 mV Tape/Cart/Play 9 volt	5-95

POWER SUPPLIES MAINS INPUT

(chassis-rest cased)	
470C 6 7 1/2 9V 300MA with ad rs	2-25
P500 9V 500 MA	3-20
HC244R 3 6 7 1/2 9V 400 MA stabilised	5-50
*P11 24V 1A 3 30	3-30
*P15 28V 1A	3-30
*P1080 12V 1A 4 70	7-80
*P1081 45V 0.9A	7-80
P12 4 1/2 12V 0.4-1A	7-15
SE101A 3-6 9 12V 1A stabilised	12-75
P1076 3 1/2 6 7 1/2 9V 12V 1A	4-20
SE800A 1-15 10V 0-4A stabilised	17-50

EMI SPEAKERS

SPECIAL PURCHASE

13in ~ 8in chassis speakers (Carriage 50p each or 50p per 150TC 10 watts 8 ohms twin cone £2-20	5-95
*450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3-85 each	5-10
EW 15 watt 8 ohm with tweeter £5-25	4-95
350 20 watt 8, 15 ohm with tweeter £7-80 each	9-95
* Polished wood cabinet £4-80 carriage 50p each or 50p pair	5-45

UHF TV TUNERS

625 line receiver UHF transistorised (tuner) UK operation. Brand new (Post packing 25p each)	14-75
TYPE C variable tuning £2-50	5-75
TYPE B 4-button push-button (adjustable) £3-50	19-75

PA DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses etc. etc.

FREE stock lists (Ref No 18) on request CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, TEL 01-723 6963

NOW OPEN SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains galore. Goodie bags. Components, etc.

Watch for further developments! EP27 Low Cost Seven Segment Led Digit Height 1in £3.35. P & P 15p. L450 rechargeable battery 2V 400mA hr 50p. P & P 15p.

Philips 12V Fluorescent inverter for RW fluorescent tube. Supplies with instr and tube £3.50. P & P 10p. STC and ITT Miniature Relays 150R 6V 2 p.c.o. 180R 6V 12V 2 p.c.o. 185R 12V 2 p.c.o. 1250R 12V 55V 2 p.c.o. 170R 18 24V 2 p.c.o. 1800R 24V 4 p.c.o. 2500R 18 24V 2 p.c.o. 4000R 24V 2 p.c.o.

BRAND NEW 60V P & P 15p. 10 7 MHz Miniature Ceramic IF Filter 40p per pair. P & P 15p. SLA14 Plessey 3W Power Amp IC £1.65. P & P 15p.

30kHz Ultrasonic Transducers, £5.90. P & P 25p. TAA 960 40kHz amp £1.75. P & P 15p.

TEST EQUIPMENT MULTIMETERS

Carriage 50p.

U4324 20kV V with case	9-25
U435 20kV V with steel case	8-75
U4313 20kV V with steel case	12-50
U4317 20kV V with case	16-50
U4341 33kV V plus transistor	10-50
U4323 20kV V with 1kHz OSC	7-75
IT12 20kV V, slim type	5-95
THL330 L33DXI 2kV V Robust	8-25
TP55N 20kV V (Case £2)	6-25
TP105 2kV V	10-00
U4323 20kV V	11-25
U4341 33kV V	9-95
EP10KN 10kV V	12-50
AF150K 50kV V Deluxe (case £1.90)	22-50
S100TA 100kV V plus transistor tester	

NEW REVOLUTIONARY SUPERTESTER 680R

680R Multi-tester	18-50
TEST AC Multivoltmeter	19-75
*TEST D.C. p.d. meter 440kHz 28mHz	19-50
*TEST 28 Range valve volt-meter	22-50
*TEST 200 R.F. Generator 120kHz	
*TEST 442N 70 SN74155N	18-95
*TEST 220 AF Generator 20Hz 200kHz	19-95
*HM500 in circuit transistor tester	19-50
*C3025 Deluxe meter 1-300mHz	6-95
*T145 Compact transistor tester	14-75
*G3-36 R.C. osc 20Hz-200kHz	19-75
*C3042 SWR Meter	5-75
*C350A Deluxe signal tracer	12-95
*SE400 Mini-tab all in one tester	15-50
C1-5 Scope 500 000kHz (Carriage 50p)	43-00
*C3043 5 CH F.A. meter 1-300mHz	5-75
Resistance sub box (Post. etc.)	2-40
Capacitor 120p	2-10
2A variable transformers (Carriage £1)	6-95
Radio activity counter 0-10r/s	9-97
Mains unit for above (Carriage 50p)	3-75

TAPE HEADS

Marrat KRSP 7 Track High	2-50
Marrat KRSP 18 Track Med	3-50
Marrat KRSP 36 Track Med	5-00
Marrat KRSP 63 Track High	1-75
Marrat Erase Heads for KRSP 7 18 36 XES11	75
Marrat BX12 34 1/2 Track Erase	75
R RPI Record Play & Track B.R.P. Single Track Rec/Play	35
Hagen Type UL290 Erase	1-50
Miniature Stereo Cassette Rec/Play (P & P 15p)	2-25

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load 30 volt max. d.c. operation, complete with data. Price £1-50 each or 2 for £2-85. Printed Circuit Panels 50p.

CALCULATORS

Sinclair Cambridge Kit £13.50	
Sinclair Cambridge (Built) £17.50	
Sinclair Memory £22.50	
Sinclair Scientific £28.95	
Sinclair Scientific Kit £18.50	

VAT 8% EXTRA ON ALL ITEMS

EXTRA DISCOUNTS

Semiconductors—Any one type or mixed SN74 Series IC 12-extra 10%, 25-extra 15%, 100—extra 20%.

74 SERIES AND LINEAR

SN7400N	£ p	SN7485N	£ p	SN74191N	£ p
SN7401N	0.16	SN7486N	1.63	SN74192N	2.00
SN7402N	0.16	SN7489N	3.87	SN74193N	2.00
SN7403N	0.16	SN7490N	0.70	SN74194N	1.30
SN7404N	0.16	SN7491A/N	1.00	SN74195N	1.10
SN7405N	0.16	SN7492N	0.70	SN74196N	1.20
SN7406N	0.42	SN7493N	0.70	SN74197N	1.20
SN7407N	0.42	SN7494N	0.80	SN74198N	2.77
SN7408N	0.28	SN7495N	0.80	SN74199N	2.52
SN7409N	0.28	SN7496N	0.95	ICCA	
SN7410N	0.16	SN7497N	0.87	CA3012	1.32
SN7411N	0.25	SN74100N	1.89	CA3014	1.80
SN7412N	0.30	SN74101N	0.58	CA3018	1.02
SN7413N	0.36	SN74102N	0.53	CA3019	1.12
SN7414N	0.72	SN74107N	0.45	CA3020	1.80
SN7416N	0.36	SN74110N	0.58	CA3022	1.93
SN7417N	0.36	SN74111N	0.88	CA3028A	1.03
SN7420N	0.16	SN74112N	1.67	CA3031	0.85
SN7421N	0.33	SN74118N	0.90	NE5600	5.00
SN7422N	0.25	SN74119N	1.68	NE5618	5.00
SN7423N	0.37	SN74120N	0.95	NE5628	5.00
SN7424N	0.37	SN74121N	0.50	NE5678	3-50
SN7426N	0.32	SN74122N	0.70	Motorola	
SN7427N	0.37	SN74123N	1.00	MC1303L	1-42
SN7428N	0.40	SN74125N	0.65	MC1304P	1-79
SN7430N	0.10	SN74132N	0.90	MC1310P	2-91
SN7432N	0.37	SN74141N	1.26	MC1386CF	0.77
SN7433N	0.37	SN74145N	1.26	MC130CC	0-80
SN7434N	0.37	SN74150N	1.75	MC1400P	0-45
SN7436N	0.37	SN74151N	0.95	MFC4010P	0-55
SN7441N	0.92	SN74154N	2.00	MFC6040P	1.00
SN7442N	0.79	SN74155N	1.30	Others	1-50
SN7443N	1.27	SN74156N	1.60	SN74603N	1-50
SN7444N	1.27	SN74157N	0.95	SN72741P	0-60
SN7445N	1.60	SN74160N	1.38	SN72748P	0-81
SN7446N	1.89	SN74161N	1.38	709C	0-39
SN7447AN	1.60	SN74162N	1.38	723C	0-40
SN7448N	1.27	SN74163N	1.76	728C	0-45
SN7450N	0.16	SN74164N	1.76	747C	1-00
SN7451N	0.16	SN74165N	1.76	748C	0-61
SN7456N	0.16	SN74166N	1.60	LM309K	2-00
SN7457N	0.16	SN74167N	3.00	SN74181N	1-75
SN7460N	0.16	SN74170N	2.52	SN74182N	1-75
SN7461N	0.36	SN74171N	2.52	SN74183N	1-10
SN7472N	0.38	SN74174N	1.57	SN74185N	1-80
SN7473N	0.41	SN74175N	1.10	SN74186N	1-00
SN7474N	0.42	SN74176N	1.26	SN74187N	1-00
SN7475N	0.59	SN74177N	1.26	SN74188N	1-00
SN7476N	0.45	SN74180N	1.26	SN74189N	1-00
SN7480N	0.60	SN74181N	3.95	SN74190N	1-00
SN7481N	1.10	SN74182N	1.26	SN74191N	2-00
SN7482N	0.87	SN74184N	1.80	SN74192N	2-00
SN7483N	1.10	SN74185N	1.80	SN74193N	2-00
SN7484N	1.00	SN74186N	1.80	SN74194N	2-00

COSMOS INTEGRATED CIRCUITS. FULL RANGE IN STOCK

AZ213	0	P	BLY36	£	0	TIP42A	£	0
AC107	0.12	p	BSX20	0	13	TIS43	0	28
AC128	0.15	BU105	0.20	20	V405A	0	22	
AC187	0.21	BY100	0.27	20	ZTX108	0	08	
AC197	0.40	BY127	0.42	12	ZTX300	0	13	
ACY39	0.78	BY213	0.42	12	ZTX302	0	18	
AD149	0.50	C1060	0.54	27	ZTX500	0	18	
AD161	0.44	GET111	0.72	29	ZN697	0	16	
AD162	0.44	GET115	0.72	29	ZN706	0	12	
AD177	0.24	GET880	0.60	20	ZN930	0	18	
AF118	0.57	LM309K	2.00	07	ZN987	0	24	
AF139	0.41	MAT121	0.25	25	ZN1132	0	42	
AF186	0.48	MJE340	0.12	47	ZN1136	0	28	
AF239	0.44	MJE520	0.63	23	ZN1613	0	21	
ASV27	0.33	MJE3055	0.77	21	ZN1671	1	20	
BA115	0.10	MJE2955	1.27	27	ZN2147	0	78	
BA113	0.05	MPF105	3.6	26	ZN2160	0	78	
BC107	0.14	NKT404	0.66	26	ZN2926	0	12	
BC108	0.13	OA5	0.72	26	ZN3053	0	48	
BC109	0.14	OA81	0.18	28	ZN3054	0	48	
BC109C	0.16	OA200	0.08	28	ZN3055	0	45	
BC113	0.15	OA202	0.06	28	ZN3440	0	58	
BC147	0.10	OC28	0.66	26	ZN3442	1	39	
BC148	0.08	OC35	0.55	25	ZN3525	0	50	
BC149	0.10	OC36	0.60	26	ZN3814	0	65	
BC169C	0.15	OC4	0.20	20	ZN3702	0	11	
BC182	0.12	OC45	0.20	20	ZN3714	1	41	
BCY32	1.85	OC72	0.28	28	ZN3777	1	77	
BCY39	1.50	OC77	0.54	28	ZN3790	2	40	
BCY70	1.18	OC81	0.29	29	ZN3819	0	38	
BCY77	0.63	OC93	0.33	33	ZN3886	0	15	
BD124	0.65	OC140	1.14	14	ZN3903	0	15	
BD131	0.65	OC170	0.30	30	ZN4002	0	14	
BD134	0.42	OC200	0.54	24	ZN4126	0	15	
BF115	0.20	OP202	0.20	20	ZN4871	0	34	
BF180	0.10	OP771	1.20	20	ZN5457	0	30	
BF194	0.10	ORP12	0.60	20	ZS303	0	06	
BFK13	0.26	ORP460	0.55	55	40550	0	54	
BFX34	0.20	P3A6A	0.18	18	40361	0	54	
BFX80	0.24	TIL209	1.24	24	41652	0	52	
BFY50	0.21	TIP29A	0.45	45	40408	0	50	
BFY51	0.20	TIP30A	0.57	40	40408	0	50	
BFY64	0.36	TIP31A	0.61	61	40636	3	00	
BFY90	0.31	TIP41A	0.74	74	40430	0	15	

I.C. IDENTICHART

PRESENTED FREE WITH PRACTICAL ELECTRONICS MARCH 1975

TYPE	DESCRIPTION	MAKE
AY-1-0212	Organ master tone generator	GI
AY-1-1313	Priority latching network	GI
AY-1-5050	7 stage divider	GI
AY-1-5051	4 stage divider	GI
AY-1-6721/5	5 stage divider	GI
AY-1-6721/6	6 stage divider	GI
AY-1-1016	16 way multiplexer	GI
AY-5-3507	3 1/2 decade DVM/display driver	GI
AY-5-4007	Quad digit display driver	GI
AY-5-4057	Quad decade counter/store	GI
AY-5-5053	10 bit D/A converter	GI
AY-5-5054	A/D converter	GI

CA3000	DC differential amplifier	RCA
CA3001	Wide band differential amplifier (video)	RCA
CA3002	Video amplifier	RCA
CA3007	A.F. differential amplifier	RCA
CA3008	Operational amplifier	RCA
CA3010	Operational amplifier	RCA
CA3011	FM/IF amplifier	RCA
CA3015	Operational amplifier	RCA
CA3016	Operational amplifier	RCA
CA3018	Transistor array	RCA
CA3019	Diode array	RCA
CA3020	Multipurpose wide band amplifier	RCA
CA3021	Low power wide band amplifier	RCA
CA3026	Dual differential amplifier	RCA
CA3028A	Differential amplifier	RCA
CA3029	Operational amplifier	RCA
CA3030	Operational amplifier	RCA
CA3033	High power operational amplifier	RCA
CA3036	Dual Darlington array	RCA
CA3037	Operational amplifier	RCA
CA3038	Operational amplifier	RCA
CA3039	Diode array	RCA
CA3040	Broadband video amplifier	RCA
CA3041	TV/IF amplifier (sound)	RCA
CA3043	FM/IF system	RCA
CA3045	Transistor array	RCA
CA3046	Transistor array	RCA
CA3047	High power operational amplifier	RCA
CA3048	4 amplifier array	RCA
CA3050	Dual differential Darlington	RCA
CA3051	Dual differential Darlington	RCA
CA3052	Stereo Preamplifier	RCA
CA3053	Differential amplifier	RCA
CA3054	Dual differential amplifier	RCA
CA3058	Zero voltage switch	RCA
CA3059	Zero voltage switch	RCA
CA3062	Photoelectric controller	RCA
CA3064	TV automatic tuning circuit	RCA
CA3079	Zero voltage switch	RCA
CA3081	Npn transistor array	RCA
CA3082	Npn transistor array	RCA
CA3083	Npn transistor array	RCA
CA3084	Pnp transistor array	RCA
CA3085	Voltage regulator (Up to 34V, 100 mA)	RCA
CA3086	Transistor array	RCA
CA3088E	AM receiver subsystem	RCA
CA3089E	FM/IF system	RCA
CA3090Q	Stereo multiplex decoder	RCA
CA3095E	Super-beta transistor array	RCA
CD4000AE	Dual 3-input NOR gate	RCA
CD4001AE	Quad 2-input NOR gate	RCA
CD4002AE	Dual 4-input NOR gate	RCA
CD4006AE	18-stage static shift register	RCA
CD4007AE	Dual complementary pair	RCA
CD4008AE	4-bit full adder	RCA
CD4009AE	Hex buffer/converter	RCA
CD4010AE	Hex buffer/converter	RCA
CD4011AE	Quad 2-input NAND gate	RCA
CD4012AE	Dual 4-input NAND gate	RCA
CD4013AE	Dual D flip-flop	RCA
CD4014AE	8-stage static shift register	RCA
CD4015AE	Dual 4-stage static shift register	RCA
CD4016AE	Quad bilateral switch	RCA
CD4017AE	Decade counter/divider	RCA
CD4018AE	Presetable divide by 'N' counter	RCA
CD4019AE	Quad AND-OR select gate	RCA
CD4020AE	14-stage binary/ripple counter	RCA
CD4021AE	8-stage static shift register	RCA
CD4022AE	Divide by 8 counter/divider	RCA
CD4023AE	Triple 3-input NAND gate	RCA
CD4024AE	7-stage binary counter	RCA
CD4025AE	Triple 3-input NOR gate	RCA
CD4027AE	Dual J-K master-slave flip-flop	RCA
CD4028AE	BCD to decimal decoder	RCA
CD4029AE	Presetable up/down counter	RCA
CD4030AE	Quad exclusive-OR gate	RCA
CD4031AE	64-stage static shift register	RCA
CD4037AE	Triple AND-OR bi-phase pairs	RCA
CD4041AE	Quad true/complement buffer	RCA
CD4042AE	Quad clocked D latch	RCA
CD4043AE	Quad 3 state NOR R/S latch	RCA
CD4044AE	Quad 2 state NAND R/S latch	RCA
CD4045AE	21-stage counter	RCA

TYPE	DESCRIPTION	MAKE
CD4046AE	Micropower phase locked loop	RCA
CD4047AE	Monostable/astable multivibrator	RCA
CD4049AE	Hex buffer/converter	RCA
CD4050AE	Hex buffer/converter	RCA
CD4054AE	Liquid crystal display driver	RCA

DM930	Dual 4 input gate	NS
DM932	Dual 4 input buffer	NS
DM933	Dual 4 input extender	NS
DM935	Hex inverter	NS
DM936	Hex inverter	NS
DM944	Dual 4 input power gate	NS
DM946	RS flip-flop	NS
DM948	RS flip-flop	NS
DM949	Quad 2 input gate	NS
DM957	Quad 2 input power gate	NS
DM961	Dual 4 input gate	NS
DM962	Triple 3 input gate	NS
DM963	Triple 3 input gate	NS
DM7856/DM8856	BCD to 7-segment LED driver	NS
DM7857	BCD to 7-segment LED driver	NS
DM7858/DM8858	BCD to 7-segment LED driver	NS
DM8861	MOS-to-LED 5-segment driver	NS
DM8863	MOS-to-LED 8-digit driver	NS
DM7880/DM8880	7-segment decoder/driver	NS
DM8884A	High voltage cathode decoder/driver	NS
DM8885	MOS to high voltage cathode buffer	NS
DM8887	8-digit Panaplex II anode driver	NS
DM8889	High voltage segment driver	NS

FZH101	Quad 2 input NAND gate	TFN
FZH111	Quad 2 input NAND gate	TFN
FZH121	Dual 5 input NAND gate	TFN
FZH131	Dual 5 input NAND gate	TFN
FZH151	Dual AND/OR gate	TFN
FZH171	Dual 4 input NAND gate	TFN
FZH191	Triple 3 input NAND gate	TFN
FZH201	Hex inverter	TFN
FZH211	Quad 2 input NAND gate	TFN
FZH231	Dual 5 input NAND gate	TFN
FZH241	Dual Schmitt NAND gate	TFN
FZJ101	JK master/slave flip-flop	TFN
FZJ111	JK master/slave flip-flop	TFN
FZJ121	Dual JK master/slave flip-flop	TFN
FZJ131	Quad D latch	TFN
FZJ141	1248 decade counter	TFN
FZJ151	4 bit binary counter	TFN
FZK101	Monostable multivibrator	TFN
FZL101	BCD decimal decoder/driver	TFN

GEL222F1	IW audio amplifier	GE
GEL223F1	Operational amplifier	GE
GEL230F1	High gain operational amplifier	GE
GEL234F1	1W audio amplifier	GE
GEL237F1	2W audio amplifier	GE
GEL239F2	Dual channel audio preamplifier	GE
GEL246S1	5W audio amplifier	GE
GEL263S1	3-5W audio amplifier	GE
GEL266F1	1-5W audio amplifier	GE
GEL277S1	2W dual channel audio amplifier	GE
GEL292	2W sound processor	GE
GEL300F1	Zero voltage switch	GE
GEL301F1	Phase control	GE

LM101	Operational amplifier	NS
LM101A/LM201A	Operational amplifier	NS
LM102	Voltage follower	NS
LM103	Regulator diode	NS
LM104/LM204	Negative regulator	NS
LM105/LM205/LM305	Voltage regulator	NS
LM106/LM206	Voltage comparator/buffer	NS
LM107/LM207	Operational amplifier	NS
LM108/LM208	Operational amplifier	NS
LM108A/LM208A/LM308A	Operational amplifier	NS
LM109/LM209	5-volt regulator	NS
LM110/LM210	Voltage follower	NS
LM111/LM211	Voltage comparator	NS
LM112/LM212	Operational amplifier	NS
LM113	Reference diode	NS
LM307	Operational amplifier	NS
LM308	Operational amplifier	NS
LM309	5-volt regulator	NS
LM310	Voltage follower	NS
LM311	Voltage comparator	NS
LM312	Operational amplifier	NS
LM318	Operational amplifier	NS
LM319	High Speed dual comparator	NS
LM350	Dual peripheral driver	NS
LM363A	Dual MOS sense amplifier	NS
LM376	Voltage regulator	NS
LM377	Dual 2-watt audio amplifier	NS
LM378	4-watt/channel stereo amplifier	NS
LM380	Audio power amplifier (3W)	NS
LM381	Low noise dual preamplifier	NS
LM382	Low noise stereo preamplifier	NS
LM383	5-watt power amplifier	NS
LM1303	Stereo preamplifier	NS

TYPE	DESCRIPTION	MAKE
LM1304	FM multiplex stereo demodulator	NS
LM1305	FM multiplex stereo demodulator	NS
LM1307/LM1307E	FM multiplex stereo demodulator	NS
LM1310/LM1310E	PLL FM stereo demodulator	NS
LM1351	FM detector, limiter and audio amplifier	NS
LM1488	Quad line driver	NS
LM1489/LM1489A	Quad line receiver	NS
LM1514/LM1414	Dual differential voltage comparator	NS
LM1596/LM1496	Balanced modulator-demodulator	NS
LM1558/LM1458	Dual operational amplifier	NS
LM1800	Phase locked FM stereo demodulator	NS
LM1805	TV signal processor	NS
LM1820	AM radio system	NS
LM1841	FM detector and limiter	NS
LM1845	Signal processing system	NS
LM2111	FM detector and limiter	NS
LM2113	FM detector and limiter	NS
LM2900	Quad amplifier	NS

MC1303	Dual stereo preamplifier	Mo
MC1304	FM multiplex stereo demodulator	Mo
MC1305	FM multiplex stereo demodulator	Mo
MC1306	1/2-watt audio amplifier	Mo
MC1307	FM multiplex stereo demodulator	Mo
MC1310	FM stereo demodulator	Mo
MC1311	FM stereo demodulator	Mo
MC1312	Four-channel SO decoder	Mo
MC1313	Four-channel SO decoder	Mo
MC1314	Four-channel audio v.c.a.	Mo
MC1339	Dual low-noise stereo preamplifier	Mo
MC1344	TV signal processor	Mo
MC1349	IF amplifier	Mo
MC1350	IF amplifier	Mo
MC1351	TV sound circuit	Mo
MC1352	TV video IF amplifier	Mo
MC1353	TV video IF amplifier	Mo
MC1410	Video amplifier	Mo
MC1414	Dual differential comparator	Mo
MC1436	Operational amplifier	Mo
MC1437	Operational amplifier	Mo
MC1438	Power booster	Mo
MC1440	Core-memory sense amplifier	Mo
MC1441	Sense amplifier	Mo
MC1444	AC-coupled 4-channel sense amplifier	Mo
MC1445	Wideband amplifier	Mo
MC1446	4-channel, low-threshold sense amplifier	Mo
MC1454	1-watt power amplifier	Mo
MC1455	Timing circuit	Mo
MC1456	Operational amplifier	Mo
MC1456C	Operational amplifier	Mo
MC1458	Dual operational amplifier	Mo
MC1458C	Dual operational amplifier	Mo
MC1460	Positive voltage regulator	Mo
MC1461	Positive voltage regulator	Mo
MC1463	Negative voltage regulator	Mo
MC1466	Voltage and current regulator	Mo
MC1468	Dual 15-volt tracking regulator	Mo
MC1469	Positive voltage regulator	Mo
MC1531	Operational amplifier	Mo
MC1533	Operational amplifier	Mo
MC1535	Dual operational amplifier	Mo
MC1536	Operational amplifier	Mo
MC1537	Operational amplifier	Mo
MC1538	Power Booster	Mo
MC1539	Operational amplifier	Mo
MFC4000B	1/4-watt audio amplifier	Mo
MFC4010A	Wideband amplifier	Mo
MFC4040	Single toggle flip-flop	Mo
MFC4050	Audio driver	Mo
MFC4060A	Voltage regulator	Mo
MFC6010	FM IF amplifier	Mo
MFC6020	Dual toggle flip-flop	Mo
MFC6040	Electronic attenuator	Mo
MFC6050	Dual toggle flip-flop with reset	Mo
MFC6070	Audio power amplifier	Mo
MFC8020A	Class B audio driver	Mo
MFC8021A	Class B audio driver	Mo
MFC8022A	Class B audio driver	Mo
MFC8030	Differential cascode amplifier	Mo
MFC8040	Audio preamplifier	Mo
MFC8070	Zero voltage switch	Mo
MM5311	Digital clock	NS
MM5316	Digital clock	NS
NE501	Video amplifier	Sig
NE510	Dual differential amplifier	Sig
NE515	Differential amplifier	Sig
NE521	Dual differential comparator/sense amplifier	Sig
NE526	Analog voltage comparator	Sig
NE527	High speed voltage comparator	Sig
NE531	Operational amplifier	Sig
NE536	FET input operational amplifier	Sig
NE540	Power driver	Sig
NE546	AM radio receiver subsystem	Sig
NE550	Voltage regulator (2 to 40V, 150mA)	Sig
NE555	Timer	Sig
NE556	Dual timer	Sig

TYPE	DESCRIPTION	MAKE
NE560	Phase locked loop	Sig
NE561	Phase locked loop	Sig
NE562	Phase locked loop	Sig
NE565	Phase locked loop	Sig
NE566	Function generator	Sig
NE592	Video amplifier	Sig
SAH190	12-tone generator for organ	ITT
SG3402N	Ring modulator	SG
SL301	Matched transistor pair	Ple
SL303	Matched transistor triplet	Ple
SL305	Dual matched transistor pairs	Ple
SL312	Matched pair with tail	Ple
SL354	Matched transistor quad	Ple
SL402	2W audio amplifier	Ple
SL403	3W audio amplifier	Ple
SL440	Power control circuit	Ple
SL610	RF amplifier	Ple
SL611	RF amplifier	Ple
SL612	IF amplifier	Ple
SL620	VOGAD	Ple
SL621	AGC generator	Ple
SL622	AF amp/VOGAD/sidetone amplifier	Ple
SL623	AM detector/AGC/SSB demodulator	Ple
SL630	AF amplifier	Ple
SL640	Double balanced modulator	Ple
SL641	Receiver mixer	Ple
SL645	Square law device	Ple
SL701	Operational amplifier	Ple
SL702	Operational amplifier	Ple
SN7400	Quad 2 input NAND gate	TI
SN7401	Quad 2 input NAND gate	TI
SN7402	Quad 2 input NOR gate	TI
SN7403	Quad 2 input NAND gate	TI
SN7404	Hex inverter	TI
SN7405	Hex inverter	TI
SN7407	Hex buffer	TI
SN7408	Quad 2 input AND gate	TI
SN7409	Quad 2 input AND gate	TI
SN7410	Triple 3 input NAND gate	TI
SN7413	Dual 4 input NAND Schmitt	TI
SN7414	Hex inverter Schmitt	TI
SN7420	Dual 4 input NAND gate	TI
SN7425	Dual 4 input NOR gate	TI
SN7430	8 input NAND gate	TI
SN7440	Dual 4 input NAND buffer	TI
SN7442	BCD - decimal decoder	TI
SN7443	Excess 3 to decimal decoder	TI
SN7444	Excess 3 Gray to decimal decoder	TI
SN7445	BCD to decimal decoder/driver	TI
SN7446	BCD to 7 segment decoder/driver	TI
SN7447	BCD to 7 segment decoder/driver	TI
SN7450	Expandable dual 2 wide 2 input gate	TI
SN7451	Dual 2 wide 2 input gate	TI
SN7453	Expandable 4 wide 2 input gate	TI
SN7454	4 wide 2 input gate	TI
SN7460	Dual 4 input expander	TI
SN7470	J-K flip-flop	TI
SN7472	J-K master-slave flip-flop	TI
SN7473	Dual J-K master-slave flip-flop	TI
SN7474	Dual D-edge triggered flip-flop	TI
SN7475	Quad bistable latch	TI
SN7476	Dual J-K master-slave flip-flop	TI
SN7480	Gated full adder	TI
SN7482	2 bit binary full adder	TI
SN7483	4 bit binary full adder	TI
SN7485	4 bit comparator	TI
SN7486	Quad 2 input exclusive OR gate	TI
SN7489	64 bit read/write memory	TI
SN7490	Decade counter	TI
SN7491	8 bit shift register	TI
SN7492	Divide by 12 counter	TI
SN7493	4 bit binary counter	TI
SN7494	4 bit shift register	TI
SN7495	4 bit shift register	TI
SN7496	5 bit shift register	TI
SN74100	Dual quad bistable latch	TI
SN74104	J-K master-slave flip-flop	TI
SN74107	Dual J-K master-slave flip-flop	TI
SN74121	Monostable multivibrator	TI
SN74141	BCD to decimal decoder with Nixie driver	TI
SN74196	Asynchronous decade counter	TI
SN74197	Asynchronous binary counter	TI
SN76001	1W power amplifier	TI
SN76013	5W power amplifier	TI
SN76023	5W power amplifier	TI
SN76115N	Stereo demodulator	TI
STK011	8W audio amplifier	Sa
STK015	13W audio amplifier	Sa
STK016	15W audio amplifier	Sa
STK023	20W audio amplifier	Sa
STK030	25W audio amplifier	Sa
TAA131	Hearing aid amplifier	Sie
TAA151	3-stage a.f. amplifier	Sie
TAA263	10mW a.f. amplifier	Mul
TAA300	1W a.f. amplifier	Mul

TYPE	DESCRIPTION	MAKE
TAA320	MOST I.F. preamplifier	Mul
TAA320A	MOST level sensor	Mul
TAA370	Hearing aid amplifier	Mul
TAA521	Operational amplifier	Sie
TAA550	Voltage stabiliser (31-35V)	Mul
TAA611C	3W audio amplifier	SGS
TAA611F	2W audio amplifier	SGS
TBA231	Dual operational amplifier	SGS
TBA400	Adjustable broadband amplifier	Sie
TBA570	AM/FM receiver	Mul
TBA641A	2W audio amplifier	SGS
TBA700	AM/FM receiver circuit	Phi
TBA800	5W audio amplifier	ITT
TBA810S	7W audio amplifier	SGS
TBA820	2W audio amplifier	SGS
TBA915	500mW audio amplifier	Mul
TCA105	Threshold switch	Sie
TCA120	4W audio amplifier	TFN
TCA160	2W audio amplifier	Mul
TCA220	Triple operational amplifier	Mul
TCA280A	Thyristor trigger module	Mul
TCA290A	Stereo decoder	Mul
TCA315	Operational amplifier	Sie
TCA420A	FM/IF channel	Phi
TCA430N	Quad organ oscillators	ITT
TCA440	AM receiver circuit	Sie
TCA530	Stabiliser for electronic tuning	Phi
TCA671	Npn transistor array	Sie
TCA730	D.C. volume and balance control	Phi
TCA740	D.C. tone control	Phi
TCA750	Voltage regulator	Mul
TCA760	Low power audio amplifier	Phi
TCA830	2W audio amplifier	TFN
TCA940	10W audio amplifier	SGS
TDA1002	Recording and preamplifier	Phi
TDA1004	8W power amplifier	Phi
TDA1005	PLL stereo decoder	Phi
TDA2610	4W audio amplifier	Phi
TDA2630	Touch control	Phi